

EASTERN MEDITERRANEAN  
UNIVERSITY

DEPARTMENT OF ELECTRICAL &  
ELECTRONICS ENGINEERING

EENG341 LAB  
ELECTRONICS I

EXPERIMENT 2  
HALF-WAVE & FULL-  
WAVE RECTIFICATION

Std. No.    Name & Surname:

1	_____	_____
2	_____	_____
3	_____	_____

Group No    : \_\_\_\_\_

Submitted to: \_\_\_\_\_

Date                : \_\_\_\_\_

**Objectives:**

- To recognize a half-wave rectified sinusoidal voltage.
- To understand the term 'mean value' as applied to a rectified waveform.
- To understand the effect of a reservoir capacitor upon the rectified waveform and its mean value.

**Simple Half-Wave Rectification**

Construct the circuit of Fig. 2.1 where V is the voltmeter. Note that the resistor limits the current to a safe value.

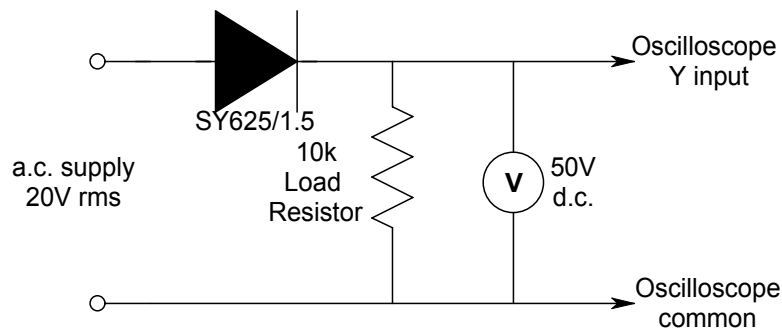


Fig. 2.1. Half-Wave Rectification

- Switch on the oscilloscope and the sinusoidal supply.
- With the oscilloscope d.c. coupled adjust the time-base and the Y amplifier sensitivity to obtain a steady trace of about 4cm vertical and 5ms/cm horizontal.
- ❖ Measure and record time T and peak voltage  $V_{pk}$ :
- ❖ Sketch the waveform and label it to show the periods when the diode is conducting and those when it is not. Time T depends upon the frequency of your power supply.
- ❖ Confirm this.  $V_{pk}$  should be very nearly equal to the peak voltage of the alternating supply.

### Questions

1. Why will  $V_{pk}$  not be exactly equal to the peak value of the supply?

2. How much is the difference between the measured and theoretical mean voltage?

(**Hint:** The mean value of a half-sinusoid can be shown by geometry to be :  $\frac{V_{pk}}{\sqrt{2}}$  .

But at every half-cycle the voltage is zero. The mean value of the waveform, therefore is:

$\frac{V_{pk}}{2\sqrt{2}}$  . Note the mean voltage indicated by the voltmeter, and compare it with  $0.35V_{pk}$ .)

3. The mean voltage you obtain is positive relative to zero. How could you obtain a negative voltage?

(**Hint:** Verify your answer by experiment and sketch the waveform.)

Fig. 2.2.

### The Effect of a Reservoir Capacitor

Very often when rectifying an alternating voltage, we wish to produce a steady direct voltage free from variations of the sort observed in Fig. 2.2. One way of doing this is to connect a capacitor in parallel with the load resistor as in Fig. 2.3.

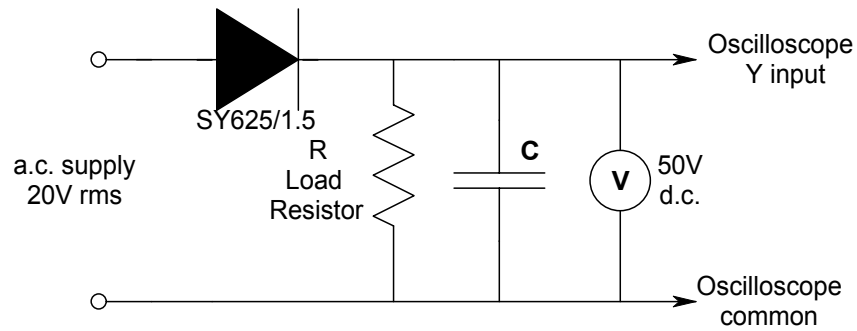


Fig. 2.3. Half-Wave Rectifier with Reservoir Capacitor

- Set  $C=1\mu\text{F}$  and  $R=10\text{k}\Omega$ .
- ❖ Observe the output waveform on the oscilloscope and note the value of the peak-to-peak variations in voltage. Note also the new mean voltage on the voltmeter.

4. Is the new mean voltage greater or less than it was before?

- Now replace the  $1\mu\text{F}$  capacitor by a much larger value of  $22\mu\text{F}$ , and answer the following questions.

5. The variations on the rectified waveform are called **RIPPLE**. Is the ripple now less than it was with the lower value capacitor?

6. Is the mean rectified voltage now greater or less?

### A Bridge Rectifier with Resistive Load

Construct the circuit of Fig. 2.4. Note that the resistor limits the current to a safe value.

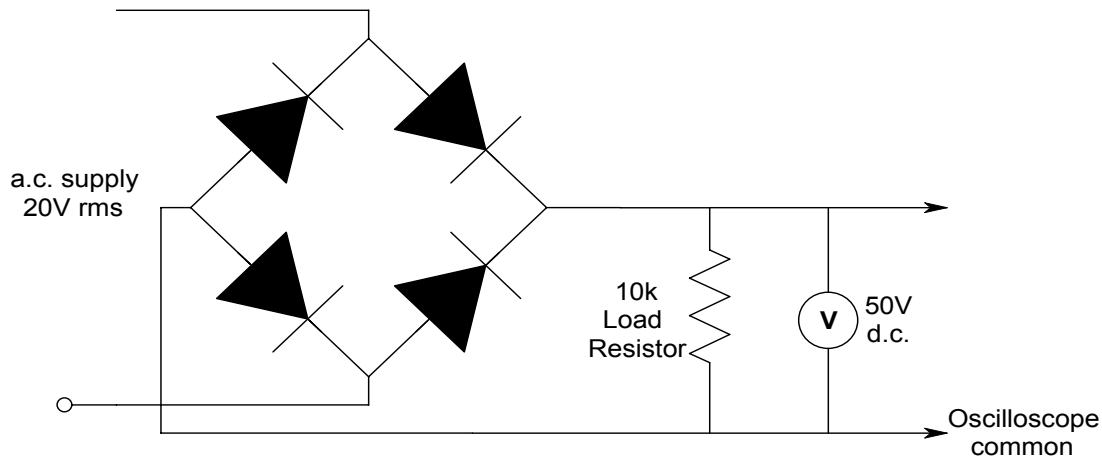


Fig. 2.4. Full-Wave Rectification

- Switch on the sinusoidal supply.
- ❖ Measure and record time mean value of output voltage indicated on the voltmeter  $V_m$ .
  
- ❖ Compare the mean value of output voltage indicated on the voltmeter those obtained in the Half-Wave rectification.

### Questions

7. The mean value of output voltage indicated on the voltmeter is it the same as it was for half-wave rectifier? If there is any difference explain why?

8. How does the mean value compare with that found for half-wave rectification?

(**Hint:** the mean value of a half-sinusoid can be shown by geometry to be:  $\frac{V_{pk}}{\sqrt{2}}$  and

$V_{pk}=10V$ . Then every half-cycle is present, this should be the mean value measured. Confirm this from your readings.

### **The Effect of a Reservoir Capacitor in the Bridge Rectifier**

- ❖ Add a  $1\mu\text{F}$  capacitor in parallel with the load resistor and note the new mean value of the rectified waveform. Compare this values with those obtain in the Simple Half-Wave rectification for the same load and capacitor values.

### **CONCLUSIONS:**