Half-Wave Rectifier





Diode conducts only for positive input voltages. An AC input with zero average yields a non-sinusoidal output with a non-zero DC component. The conversion of AC to DC is called rectification.

The "conduction angle" $\theta_{\rm c}$ is that part of the cycle during which the diode is conducting.

The average DC component is given by

$$V_{dc} = \frac{1}{T} \int_0^T V(t) dt$$



Half-Wave Rectifier



 $V_{in}(t) = V_m \sin \omega t$ $V_{out}(t) = \begin{cases} V_{in}(t) - v_d & V_{in} > v_d \\ 0 & \text{otherwise} \end{cases}$

Conduction Angle

Average DC Value

$$V_{dc} = \frac{1}{T} \int_{0}^{T} V_{out}(t) dt = \frac{1}{T} \int_{t_{on}}^{t_{off}} \left(V_{m} \sin \omega t - v_{d} \right) dt$$

$$V_{dc} = \frac{V_{m}}{\pi} \left[\sqrt{1 - \frac{v_{d}^{2}}{V_{m}^{2}}} - \frac{\theta_{c}}{2} \frac{v_{d}}{V_{m}} \right]$$

$$V_{dc} \approx \frac{V_{m}}{\pi} \left[1 - \frac{\pi}{2} \frac{v_{d}}{V_{m}} + \frac{v_{d}^{2}}{2V_{m}^{2}} \right] \quad \text{for} \quad v_{d} \ll V_{m}$$

Ideal rectifier:

$$v_d = 0$$

 $\theta_c \approx \pi$
 $V_{dc} = \frac{V_m}{\pi} = 0.318V_m$

UCSB

 V_{dc}

Т

 \mathcal{V}_d 1

V_{in} !

 $\theta_{\rm c}$

V_{out}

© Bob York, 2006-2009

Back to TOC

Half-Wave Rectifier



Ideal diode model

 V_{in} V_{out} V_{out} $\theta_{\rm c}$



Constant voltage drop model

Suppose we reverse the diode: now only the negative portion of the input signal passes through



Other than the poarity reversal, all math on conduction angle and DC magnitude is identical

Back to TOC

Peak Detector





Peak-Detector with Load

Any load or leakage path will discharge the capacitor. In this case, the output will depend on how the RC time constant compares with the period of the input signal.



The plots at right consider the various cases for the simple circuit above with a 1kHz, 5V sinusoidal input

$$\tau = RC$$
 T = 1 mS

For $\tau \ll T$, circuit acts like an ideal rectifier For $\tau \gg T$, circuit acts like an ideal peak detector



U C S B

