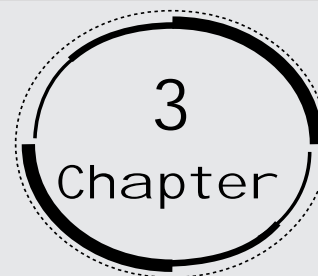


# Current Electricity



**1. The storage battery of a car has an emf of 12 V. If the internal resistance of the battery is  $0.4\Omega$  , what is the maximum current that can be drawn from the battery?**

**Ans:** In the above question it is given that:

Emf of the battery,  $E = 12\text{V}$

Internal resistance of the battery,  $r = 0.4\Omega$

Consider the maximum current drawn from the battery to be  $I$ .

Therefore, using Ohm's law,

$$E = Ir$$

$$\Rightarrow I = \frac{E}{r}$$

$$\Rightarrow I = \frac{12}{0.4}$$

$$\Rightarrow I = 30\text{A}$$

Clearly, the maximum current drawn from the given battery is 30A .

**2. A battery of emf 10V and internal resistance  $3\Omega$  is connected to a resistor. If the current in the circuit is 0.5 A, what is the resistance of the resistor? What is the terminal voltage of the battery when the circuit is closed?**

**Ans:** In the above question it is given that:

Emf of the battery,  $E = 10\text{ V}$

Internal resistance of the battery,  $r = 3\Omega$

Current in the circuit,  $I = 0.5\text{A}$

Consider the resistance of the resistor to be  $R$  .

Therefore, using Ohm's law,

$$I = \frac{E}{R + r}$$

$$R + r = \frac{E}{I}$$

$$\Rightarrow R + r = \frac{10}{0.5}$$

$$\Rightarrow R + r = 20$$

$$\Rightarrow R = 20 - 3 = 17\Omega$$

Let the terminal voltage of the resistor be  $V$ .

Using the Ohm's law,

$$V = IR$$

$$\Rightarrow V = 0.5 \times 17 = 8.5V$$

Thus, the resistance of the resistor is  $17\Omega$  and the terminal voltage is  $8.5V$ .

**3. At room temperature  $27.0^\circ\text{C}$ , the resistance of a heating element is  $100\Omega$ . What is the temperature of the element if the resistance is found to be  $117\Omega$  given that the temperature coefficient of the material of the resistor is  $1.70 \times 10^{-4}^\circ\text{C}^{-1}$ ?**

**Ans:** In the above question it is given that at room temperature ( $T = 27.0^\circ\text{C}$ ), the resistance of the heating element is  $100\Omega$  (say  $R$ ).

Also, the heating element's temperature coefficient is given to be  $\alpha = 1.70 \times 10^{-4}^\circ\text{C}^{-1}$ .

Now, it is said that the resistance of the heating element at an increased temperature (say  $T_1$ ) is  $117\Omega$  (say  $R_1$ ). To compute this unknown increased temperature  $T_1$ , the formula for temperature coefficient of a material can be used.

It is known that temperature co-efficient of a material provides information on the nature of that material with respect to its change in resistance with temperature. Mathematically,

$$\alpha = \frac{R_1 - R}{R(T_1 - T)}$$

$$\Rightarrow T_1 - T = \frac{R_1 - R}{R\alpha}$$

Substituting the given values,

$$\Rightarrow T_1 - 27 = \frac{117 - 100}{100 \times 1.70 \times 10^{-4}}$$

$$\Rightarrow T_1 - 27 = 1000$$

$$\Rightarrow T_1 = 1027^\circ\text{C}$$

Clearly, it is at  $1027^\circ\text{C}$  when the resistance of the element is  $117\Omega$ .

**4. A negligibly small current is passed through a wire of length 15 m and uniform cross-section  $6.0 \times 10^{-7} \text{ m}^2$ , and its resistance is measured to be  $5.0 \Omega$ . What is the resistivity of the material at the temperature of the experiment?**

**Ans:** In the above question it is given that:

Length of the wire,  $l = 15 \text{ m}$

Area of cross-section of the wire,  $a = 6.0 \times 10^{-7} \text{ m}^2$

Resistance of the material of the wire,  $R = 5.0 \Omega$

Let resistivity of the material of the wire be  $\rho$

It is known that, resistance is related with the resistivity as:

$$R = \rho \frac{l}{A}$$

$$\Rightarrow \rho = \frac{RA}{l}$$

$$\Rightarrow \rho = \frac{5 \times 6.0 \times 10^{-7}}{15}$$

$$\Rightarrow \rho = 2 \times 10^{-7} \text{ m}^2$$

Therefore, the resistivity of the material is  $2 \times 10^{-7} \text{ m}^2$ .

**5. A silver wire has a resistance of  $2.1 \Omega$  at  $27.5^\circ \text{C}$ , and a resistance of  $2.7 \Omega$  at  $100^\circ \text{C}$ . Determine the temperature coefficient of resistivity of silver.**

**Ans:** In the above question it is given that:

Temperature,  $T_1 = 27.5^\circ \text{C}$ .

Resistance of the silver wire at  $T_1$  is  $R_1 = 2.1 \Omega$ .

Temperature,  $T_2 = 100^\circ \text{C}$ .

Resistance of the silver wire at  $T_2$  is  $R_2 = 2.7 \Omega$ .

Let the temperature coefficient of silver be  $\alpha$ . It is known that temperature coefficient of a material provides information on the nature of that material with respect to its change in resistance with temperature. Mathematically, it is related with temperature and resistance by the formula:

$$\alpha = \frac{R_2 - R_1}{R_1(T_2 - T_1)}$$

$$\Rightarrow \alpha = \frac{2.7 - 2.1}{2.1(100 - 27.5)} = 0.0039^\circ \text{C}^{-1}$$

Clearly, the temperature coefficient of silver is  $0.0039^\circ \text{C}^{-1}$ .

**6. A heating element using nichrome connected to a 230 V supply draws an initial current of 3.2 A which settles after a few seconds to a steady value of 2.8 A. What is the steady temperature of the heating element if the room**

**temperature is  $27^{\circ}\text{C}$  ? Temperature coefficient of resistance of nichrome averaged over the temperature range involved is  $1.70 \times 10^{-4} \text{ }^{\circ}\text{C}^{-1}$  .**

**Ans:** In the above question it is given that:

Supply voltage is  $V = 230\text{V}$

Initial current drawn is  $I_1 = 3.2\text{A}$  .

Let the initial resistance be  $R_1$  .

Therefore, using Ohm's law,

$$R_1 = \frac{V}{I_1}$$

$$\Rightarrow R_1 = \frac{230}{3.2} = 71.87\Omega$$

Steady state value of the current is  $I_2 = 2.8\text{A}$  .

Let the resistance of the steady state be  $R_2$  .

Therefore, using Ohm's law.

$$R_2 = \frac{V}{I_2}$$

$$\Rightarrow R_2 = \frac{230}{2.8} = 82.14\Omega$$

Temperature co-efficient of nichrome is  $\alpha = 1.70 \times 10^{-4} \text{ }^{\circ}\text{C}^{-1}$  .

Initial temperature of nichrome is  $T_1 = 27^{\circ}\text{C}$  .

Let steady state temperature reached by nichrome be  $T_2$  .

Now, it is known that temperature co-efficient of a material provides information on the nature of that material with respect to its change in resistance with temperature. Mathematically, it is given by

$$\alpha = \frac{R_2 - R_1}{R_1(T_2 - T_1)}$$

$$\Rightarrow (T_2 - T_1) = \frac{R_2 - R_1}{R_1 \alpha}$$

Substituting the given values,


$$\Rightarrow (T_2 - 27) = \frac{82.14 - 71.87}{71.87 \times 1.70 \times 10^{-4}}$$

$$\Rightarrow T_2 - 27 = 840.5$$


$$\Rightarrow T_2 = 867.5^{\circ}\text{C}$$

Clearly, the steady temperature of the heating element is  $867.5^{\circ}\text{C}$  .

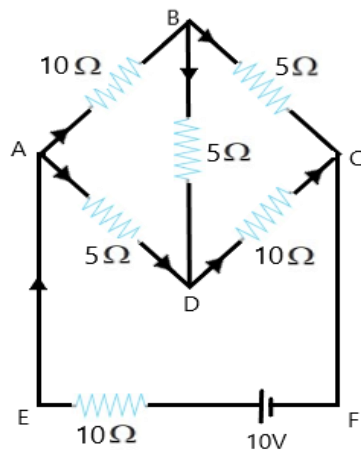7. Determine the current in each branch of the network shown in figure:



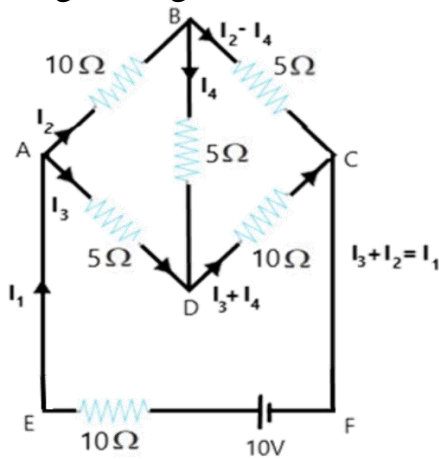**Ans:** Current flowing through various branches of the circuit is represented in the given figure.



Consider

$I_1$  = Current flowing through the outer circuit

$I_2$  = Current flowing through branch AB

$I_3$  = Current flowing through branch AD

$I_2 - I_4$  = Current flowing through branch BC

$I_3 + I_4$  = Current flowing through branch CD

$I_4$  = Current flowing through branch BD

For the closed circuit ABDA, potential is zero i.e.,

$$10I_2 + 5I_4 - 5I_3 = 0$$

$$2I_2 + I_4 - I_3 = 0$$

$$I_3 = 2I_2 + I_4 \quad \dots\dots (1)$$

For the closed circuit BCDB, potential is zero i.e.,

$$5(I_2 - I_4) - 10(I_3 + I_4) - 5I_4 = 0$$

$$5I_2 + 5I_4 - 10I_3 - 10I_4 - 5I_4 = 0$$

$$5I_2 - 10I_3 - 20I_4 = 0$$

$$I_2 = 2I_3 + 4I_4 \quad \dots\dots (2)$$

For the closed circuit ABCFEA, potential is zero i.e.,

$$-10 + 10(I_1) + 10(I_2) + 5(I_2 - I_4) = 0$$

$$10 = 15I_2 + 10I_1 - 5I_4$$

$$3I_3 + 2I_1 - I_4 = 2 \quad \dots\dots (3)$$

From equations (1) and (2), we obtain

$$I_3 = 2(2I_3 + 4I_4) + I_4$$

$$I_3 = 4I_3 + 8I_4 + I_4$$

$$-3I_3 = 9I_4$$

$$-3I_4 = +I_3 \quad \dots\dots (4)$$

Putting equation (4) in equation (1), we obtain

$$I_3 = 2I_2 + I_4$$

$$-4I_4 = 2I_2 \quad \dots\dots (5)$$

It is evident from the given figure that,

$$I_1 = I_3 + I_2 \quad \dots\dots (6)$$

Putting equation (6) in equation (1), we obtain

$$3I_2 + 2(I_3 + I_2) - I_4 = 2$$

$$5I_2 + 2I_3 - I_4 = 2 \quad \dots\dots (7)$$

Putting equations (4) and (5) in equation (7), we obtain

$$5(-2I_4) + 2(-3I_4) - I_4 = 2$$

$$-10I_4 - 6I_4 - I_4 = 2$$

$$17I_4 = -2$$

$$I_4 = -\frac{2}{17} \text{ A}$$

Equation (4) reduces to

$$I_3 = -3(I_4)$$

$$I_3 = -3\left(-\frac{2}{17}\right) = \frac{6}{17} \text{ A}$$

$$I_2 = -2(I_4)$$

$$I_2 = -2\left(-\frac{2}{17}\right) = \frac{4}{17} \text{ A}$$

$$I_2 - I_4 = \frac{4}{17} - \left(-\frac{2}{17}\right) = \frac{6}{17}$$

$$I_3 + I_4 = \frac{6}{17} + \left(\frac{-2}{17}\right) = \frac{4}{17} \text{ A}$$

$$I_1 = I_3 + I_2$$

$$\therefore I_1 = \frac{6}{17} + \frac{4}{17} = \frac{10}{17} \text{ A}$$

$$\text{Therefore, current in branch AB} = \frac{4}{17} \text{ A}$$

$$\text{Current in branch BC} = \frac{6}{17} \text{ A}$$

$$\text{Current in branch CD} = \frac{-4}{17} \text{ A}$$

$$\text{Current in branch AD} = \frac{6}{17} \text{ A}$$

$$\text{Current in branch BD} = \left(\frac{-2}{17}\right) \text{ A}$$

$$\text{Total current} = \frac{4}{17} + \frac{6}{17} + \frac{-4}{17} + \frac{6}{17} + \frac{-2}{17} = \frac{10}{17} \text{ A} .$$

**8. A storage battery of emf 8.0 V and internal resistance  $0.5\Omega$  is being charged by a 120 V DC supply using a series resistor of  $15.5\Omega$ . What is the terminal voltage of the battery during charging? What is the purpose of having a series resistor in the charging circuit?**

**Ans:** In the above question it is given that:

Emf of the storage battery is  $E = 0.8\text{V}$ .

Internal resistance of the battery is  $r = 0.5\Omega$ .

DC supply voltage is  $V = 120\text{V}$

Resistance of the resistor is  $R = 15.5\Omega$ .

Consider effective voltage in the circuit to be  $V'$ , which would be the difference in the supply voltage and the emf of the battery.

$$V' = V - E$$

$$\Rightarrow V' = 120 - 8 = 112\text{V}$$

Now, current flowing in the circuit is  $I$  and the resistance  $R$  is connected in series to the storage battery.

Therefore, using Ohm's law,

$$I = \frac{V'}{R + r}$$

$$\Rightarrow I = \frac{112}{15.5 + 0.5} = 7 \text{ A}$$

Thus, voltage across resistor R would be:

$$IR = 7 \times 15.5 = 108.5 \text{ V}$$

DC supply voltage = Terminal voltage of battery + Voltage drop across R

$$\text{Terminal voltage of battery} = 120 - 108.5 = 11.5 \text{ V}$$

A series resistor in a charging circuit takes the responsibility for controlling the current drawn from the external source. Excluding this series resistor is dangerous as the current flow would be extremely high if so.

### 9. The number density of free electrons in a copper conductor estimated in

**Example 3.1** is  $8.5 \times 10^{28} \text{ m}^{-3}$ . How long does an electron take to drift from one end of a wire 3.0 m long to its other end? The area of cross-section of the wire is  $2.0 \times 10^{-6} \text{ m}^2$  and it is carrying a current of 3.0 A.

**Ans:** In the above question it is given that:

Number density of free electrons in a copper conductor is  $n = 8.5 \times 10^{28} \text{ m}^{-3}$ .

Length of the copper wire is  $l = 3.0 \text{ m}$ .

Area of cross-section of the wire is  $A = 2.0 \times 10^{-6} \text{ m}^2$ .

Current carried by the wire is  $I = 3.0 \text{ A}$ .

Now we know that:

$$I = nAeV_d$$

Where,

$e$  is the electric charge of magnitude  $1.6 \times 10^{-19} \text{ C}$ .

$V_d$  is the drift velocity and

$$\text{Drift velocity} = \frac{\text{Length of the wire (l)}}{\text{Time taken to cover (t)}}$$

$$I = nAe \frac{l}{t}$$

$$\Rightarrow t = \frac{nAel}{I}$$

$$\Rightarrow t = \frac{3 \times 8.5 \times 10^{28} \times 2 \times 10^{-6} \times 1.6 \times 10^{-19}}{3.0}$$

$$\therefore t = 2.7 \times 10^4 \text{ s}$$

Hence the time taken by an electron to drift from one end of the wire to the other is  $2.7 \times 10^4 \text{ s}$ .