SOLVED EXAMPLES

Ex. 1 The peak voltage in a 220 V AC source is (A) 220 V (C) about 310 V

(B) about 160 V (D) 440 V

Sol. $V_0 = \sqrt{2} V_{ms} = \sqrt{2} \times 220 \simeq 330 V$ Ans is (C)

Ans. is **(B)**

Ex. 2 An AC source is rated 220 V, 50 Hz. The average voltage is calculated in a time interval of 0.01 s. It

- (A) must be zero(B) may be zero(C) is never zero(D) is $(220/\sqrt{2})V$ Sol.May be zero
- **Ex.3** Find the effective value of current $i = 2 + 4 \cos 100 \pi t$.

Sol.
$$I_{\rm rms} = \left[\int_0^T \frac{\left(2 + 4\cos 100\pi t\right)^2 dt}{T} \right]^{1/2} = 2\sqrt{3}$$

Ex.4 The peak value of an alternating current is 5 A and its frequency is 60 Hz. Find its rms value. How long will the current take to reach the peak value starting from zero?

Sol.
$$I_{rms} = \frac{I_0}{\sqrt{2}} = \frac{5}{\sqrt{2}} A$$
, $t = \frac{T}{4} = \frac{1}{240} s$

Ex.5 An alternating current having peak value 14 A is used to heat a metal wire. To produce the same heating effect, a constant current i can be used where i is

- Sol. $I_{\rm RMS} = \frac{I_0}{\sqrt{2}} = \frac{14}{\sqrt{2}} \simeq 10$ Ans. is (D)
- Ex.6 Find the average power concumed in the circuit if a voltage $v_s = 200\sqrt{2} \sin \omega t$ is applied to an AC circuit and the current in the circuit is found to be $i = 2 \sin (\omega t + \pi/4)$.

Sol.
$$P = V_{RMS} I_{RMS} \cos \phi = \frac{200\sqrt{2}}{\sqrt{2}} \times \frac{2}{\sqrt{2}} \times \cos \frac{\pi}{4} = 200 \text{ W}$$

Ex. 7 A capacitor acts as an infinite resistance for (A) DC (B) AC (C) DC as well as AC (D) neither AC nor DC

Sol.
$$x_c = \frac{1}{\omega c}$$
 for DC $\omega = 0$. so, $x_c = \infty$
Ans. is (A)



Ex. 8 A 10 μ F capacitor is connected with an ac source E = 200 $\sqrt{2}$ sin (100 t) V through an ac ammeter (it reads rms value). What will be the reading of the ammeter?

Sol.
$$I_0 = \frac{V_0}{x_C} = \frac{200\sqrt{2}}{1/\omega C}$$
; $I_{RMS} = \frac{I_0}{\sqrt{2}} = 200 \text{ mA}$

Ex.9 Find the reactance of a capacitor ($C = 200 \mu F$) when it is connected to (A) 10 Hz AC source, (B) a 50 Hz AC source and (C) a 500 Hz AC source.

Sol. (A)
$$x_c = \frac{1}{\omega C} = \frac{1}{2\pi f C} \simeq 80 \Omega$$
 for f = 10 Hz AC source,

(B)
$$\mathbf{x}_{c} = \frac{1}{\omega C} = \frac{1}{2\pi f C} \simeq 16 \,\Omega$$
 for f = 50 Hz and

(C)
$$\mathbf{x}_{\rm C} = \frac{1}{\omega {\rm C}} = \frac{1}{2\pi {\rm f}{\rm C}} \simeq 1.6 \,\Omega$$
 for f= 500 Hz.

- Ex. 10 An inductor (L = 200 mH) is connected to an AC source of peak current. What is the intantaneous voltage of the source when the current is at its peak value?
- Sol. Because phase difference between volatage and current is $\pi/2$ for pure inductor. So, Ans. is zero
- **Ex. 11** An AC source producing emf $E = E_0 [\cos(100 \pi s^{-1})t + \cos(500 \pi s^{-1})t]$ is connected in series with a capacitor and a resistor. The current in the circuit is found to be $i = i_1 \cos[(100 \pi s^{-1})t + \phi_1] + i_2 \cos[(500 \pi s^{-1})t + \phi_1]$

(A) $i_1 > i_2$ (B) $i_1 = i_2$ (D) $i_1 < i_2$ (D) the information is insufficient to find the relation between i_1 and i_2

Sol. Impedence z is given by $z = \sqrt{\left(\frac{1}{\omega C}\right)^2 + R^2}$

For higher ω , z will be lower so current will be higher Ans is (C)

Ex. 12 An alternating voltage of 220 volt r.m.s. at a frequency of 40 cycles/sec is supplied to a circuit containing a pure inductance of 0.01 H and a pure resistance of 6 ohms in series. Calculate (i) the current, (ii) potential difference across the resistance, (iii) potential difference across the inductance, (iv) the time lag, (v) power factor.

Sol. (i)
$$z = \sqrt{(\omega L)^2 + R^2} = \sqrt{(2\pi \times 40 \times 0.01^2)^2 + 6^2} = \sqrt{(42.4)}$$

 $I_{rms} = \frac{220}{z} = 33.83 \text{ amp.}$
(ii) $V_{rms} = I_{rms} \times R = 202.98 \text{ volts}$ (iii) $\omega L \times I_{rms} = 96.83 \text{ volts}$
(iv) $t = T \frac{\phi}{2\pi} = 0.01579 \text{ sec}$ (v) $\cos \phi = \frac{R}{Z} = 0.92$



Ex.13 Which of the following plots may represent the reactance of a series LC combination ?



Sol. D

- **Ex. 14** A series AC circuit has resistance of 4 Ω and a reactance of 3 Ω . the impedance of the circuit is (A) 5 Ω (B) 7 Ω
 - (C) $12/7 \Omega$ (D) $7/12 \Omega$
- **Sol.** $Z = \sqrt{4^2 + 3^2} = 5 \Omega$ Ans. is (A)
- Ex.15 A periodic voltage V varies with time t as shown in the figure. T is the time period. The r.m.s. value of the voltage is:-



- Sol. The phase difference between V_c and V_{R_2} is $\pi/2$ rad or 90°
- **Ex.17** The potential difference V and current I flowing through the AC circuit is given by $V = 5 \cos(\omega t \pi/6)$ volt and I = 10sin ωt ampere. The average power dissipated in the circuit is

(A)
$$\frac{25\sqrt{3}}{2}$$
 W (B) 12.5 W (C) 25 W (D) 50 W

Sol. $V = 5 \cos (\omega t - \pi/6); i = 10 \sin \omega t = 10 \cos (\omega t - \pi/2)$

 $\phi = \frac{\pi}{2} - \frac{\pi}{6} = \frac{\pi}{3}; P = \frac{VI}{2}\cos\phi = \frac{5 \times 10}{2} \times \frac{1}{2} = 12.5 W$

ALTERNATING CURRENT

2H

000000

V=2t



- (A) current versus time graph is a parabola
- (B) energy stored in magnetic field at t = 2 s is 4J
- (C) potential energy at time t = 1 s in magnetic field is increasing at a rate of 1 J/s

(D) energy stored in magnetic field is zero all the time

Sol.
$$V = 2t \Rightarrow L\frac{di}{dt} = 2t \Rightarrow 2 \times \frac{di}{dt} = 2t \Rightarrow \frac{di}{dt} \Rightarrow i = \frac{t^2}{2} \Rightarrow i - t$$
 graph parabola

$$U = \frac{1}{2} Li^{2} = \frac{1}{2} \times 2 \times 4 = 4J \text{ and } \frac{dU}{dt} = Li \frac{di}{dt} = 2 \times \frac{t^{2}}{2} \times t = t^{3} = 1 J/s$$

Ex.19 The radius of a coil decreases steadily at the rate of 10^{-2} m/s. A constant and uniform magnetic field of induction 10^{-3} Wb/m² acts perpendicular to the plane of the coil. The radius of the coil when the induced e.m.f. in the coil is 1μ V, is :-

(A)
$$\frac{2}{\pi}$$
 cm (B) $\frac{3}{\pi}$ cm (C) $\frac{4}{\pi}$ cm (D) $\frac{5}{\pi}$ cm
Sol. $e = \frac{d\phi}{dt} = \frac{d}{dt} (\pi r^2 B) = 2\pi r B \frac{dr}{dt} \Rightarrow r = \frac{e}{(2\pi B \frac{dr}{dt})} \Rightarrow r = \frac{10^{-6}}{2\pi \times 10^{-3} \times 10^{-2}} = \frac{5}{\pi}$ cm

Ex.20 For an LCR series circuit, phasors of current i and applied voltage $V = V_0 \sin \omega t$ are shown in diagram at t =0. Which of the following is/are correct?

(A) At t =
$$\frac{\pi}{2\omega}$$
, instantaneous power supplied by source is negative

(B) From
$$0 < t < \frac{2\pi}{3\omega}$$
, average power supplied by source is positive.

(C) At
$$t = \frac{5\pi}{6\omega}$$
, instantaneous power supplied by source is negative

(D) If ω is increased slightly, angle between the two phasors decreases.

Sol. The graph shows V & I as function of time.

Current leads the voltage by $\pi/3$

Power is negative if V & I are of opposite sign

If $\omega \uparrow \Rightarrow \frac{1}{\omega C} \downarrow$ thus angle decreases.



π/3





PHYSICS FOR JEE MAIN & ADVANCED

Exercise # 1 [Single Correct Choice Type Questions] The peak value of an alternating e.m.f given by $E = E_0 \cos \omega t$, is 10 volt and frequency is 50 Hz. At time $t = (1/2)^{1/2}$ 1. 600) sec, the instantaneous value of e.m.f is : (A) 10 volt (B) $5\sqrt{3}$ volt (C) 5 volt **(D)** 1 volt r.m.s. value of current i = 3 + 4 sin ($\omega t + \pi/3$) is: 2. (C) $\frac{5}{\sqrt{2}}$ A **(D)** $\frac{7}{\sqrt{2}}$ A **(B)** $\sqrt{17}$ A (A) 5 A 3. The voltage of an AC source varies with time according to the equation, $V = 100 \sin 100 \pi t \cos 100 \pi t$. Where t is in second and V is in volt. Then : (A) the peak voltage of the source is 100 volt (B) the peak voltage of the source is $(100/\sqrt{2})$ volt (C) the peak voltage of the source is 50 volt (D) the frequency of the source is 50 Hz 4. An AC voltage is given by : $E = E_0 \sin \frac{2\pi t}{T}$ Then the mean value of voltage calculated over time interval of T/2 seconds : (A) is always zero (B) is never zero (C) is $(2E_o/\pi)$ always (D) may be zero An alternating voltage is given by : $e = e_1 \sin \omega t + e_2 \cos \omega t$. Then the root mean square value of voltage is 5. given by : **(D)** $\sqrt{\frac{e_1^2 + e_2^2}{2}}$ (C) $\sqrt{\frac{e_1 e_2}{2}}$ (B) $\sqrt{e_1 e_2}$ (A) $\sqrt{e_1^2 + e_2^2}$ Energy dissipates in LCR circuit in : 6. (A) L only (B) C only (C) R only (D) all of these The average power delivered to a series AC circuit is given by (symbols have their usual meaning) : 7. $(\mathbf{A}) \mathbf{E}_{\rm rms} \mathbf{I}_{\rm rms}$ **(B)** $E_{rms} I_{rms} \cos \phi$ (C) $E_{rms} I_{rms} \sin \phi$ (D) zero An AC voltage of V = $220\sqrt{2} \sin\left(100\pi t + \frac{\pi}{2}\right)$ is applied across a DC voltmeter, its reading will be: 8. (A) $220\sqrt{2}$ V (B) $\sqrt{2}$ V (C) 220 V (D) zero 9. The potential difference V across and the current I flowing through an instrument in an AC circuit are given by: $V = 5 \cos \omega t \text{ volt}$ $I = 2 \sin \omega t Amp.$ The power dissipated in the instrument is : (A) zero (B) 5 watt (C) 10 watt (D) 2.5 watt

10.	What is the rms value of is thrice that produced b	of an alternating current why a D.C. current of 2 amp	hich when passed through ere in the same resistor in	a resistor produces heat, which the same time interval?
	(A) 6 ampere	(B) 2 ampere	(C) $2\sqrt{3}$ ampere	(D) 0.65 ampere
11.	A direct current of 2 A a resistances. The ratio of	and an alternating current h heat produced in the two r	aving a maximum value o resistances in the same time	f 2 A flow through two identical e interval will be:
	(A) 1 : 1	(B) 1 : 2	(C) 2 : 1	(D) 4 : 1
12.	A sinusoidal AC current dissipated is :	flows through a resistor o	f resistance R. If the peak	current is I_{p} , then average power
	(A) $I_p^2 R \cos \theta$	$(\mathbf{B}) \ \frac{1}{2} I_p^2 \ \mathbf{R}$	(C) $\frac{4}{\pi} I_p^2 R$	(D) $\frac{1}{\pi^2} I_p^2 \mathbf{R}$
13.	The impedance of a series circuit is :	es circuit consists of 3 ohr	n resistance and 4 ohm rea	actance. The power factor of the
	(A) 0.4	(B) 0.6	(C) 0.8	(D) 1.0
14.	A resistor and a capacitor is 2 ampere. If the powe	or are connected to an AC so r consumed in the circuit is	upply of 200 volt, 50 Hz in 100 watt, then the resistar	series. The current in the circuit ace in the circuit is:
	(A) 100 Ω	(B) 25 Ω	(C) $\sqrt{125 \times 75} \Omega$	(D) 400 Ω
15.	An electric bulb and a c the source, the brightne	capacitor are connected in ess of the bulb :	series with an AC source.	On increasing the frequency of
	(A) increase		(B) decreases	
	(C) remains unchanged		(D) sometimes increases	s and sometimes decreases
16.	A coil of inductance $V = 10 \sin (100 t)$. The p	5.0 mH and negligible eak current in the circuit w	e resistance is connect vill be :	ed to an alternating voltage
	(A) 2 amp	(B) 1 amp	(C) 10 amp	(D) 20 amp
17.	By what percentage the changes from $(1/2)$ to (1)	e impedance in an AC ser 1/4) (when R is <mark>const</mark> ant) ?	ries circuit should be incr	reased so that the power factor
	(A) 200%	(B) 100%	(C) 50% (D) 400	%
18.	A 0.21-H inductor and a circuit and the phase ar (Use $\pi = 22/7$)	88- Ω resistor are connectengle between the current a	ed in series to a 220-V, 50- nd the source voltage are	Hz AC source. The current in the respectively.
	(A) 2 A, $\tan^{-1} 3/4$	(B) 14.4 A, $\tan^{-1} 7/8$	(C) 14.4 A, $\tan^{-1} 8/7$	(D) 3.28 A, $\tan^{-1} 2/11$
19.	If the frequency of the s	source e.m.f. in an AC circ	uit is n, the power varies v	with a frequency :
	(A) n	(B) 2 n	(C) n/2	(D) zero
20.	A 100 volt AC source C = 5 μ F and R = 10 Ω ,	of angular frequency 50 all connected in series. Th	00 rad/s is connected to a ne potential difference acro	a LCR circuit with $L = 0.8$ H, oss the resistance is
	(A) $\frac{100}{\sqrt{2}}$ volt	(B) 100 volt	(C) 50 volt	(D) 50√3



21. An LCR series circuit with 100 Ω resistance is connected to an AC source of 200 V and angular frequency 300 radians per second. When only the capacitance is removed, the current lags the voltage by 60°. When only the inductance is removed, the current leads the voltage by 60°. Then the current and power dissipated in LCR circuit are respectively

(A) 1A, 200 watt. (B) 1A, 400 watt. (C) 2A, 200 watt. (D) 2A, 400 watt.

22. In an L-R series circuit (L = $\frac{175}{11}$ mH and R = 12 Ω), a variable emf source (V = V₀ sin ω t) of V_{rms} = 130 $\sqrt{2}$ V and frequency 50 Hz is applied. The current amplitude in the circuit and phase of current with respect to voltage are respectively (Use π = 22/7)

- (A) 14.14A, 30° (B) 10 $\sqrt{2}$ A, tan⁻¹ $\frac{5}{12}$ (C) 10 A, tan⁻¹ $\frac{5}{12}$ (D) 20 A, tan⁻¹ $\frac{5}{12}$
- 23. A pure resistive circuit element X when connected to an AC supply of peak voltage 200 V gives a peak current of 5 A which is in phase with the voltage. A second circuit element Y, when connected to the same AC supply also gives the same value of peak current but the current lags behind by 90°. If the series combination of X and Y is connected to the same supply, what will be the rms value of current ?
 - (A) $\frac{10}{\sqrt{2}}$ amp (B) $\frac{5}{\sqrt{2}}$ amp (C) $\frac{5}{2}$ amp (D) 5 amp
- In an AC circuit the potential differences across an inductor and resistor joined in series are respectively 16 V and 20 V. The total potential difference across the circuit is
 (A) 20 V
 (B) 25.6 V
 (C) 31.9 V
 (D) 53.5 V

25. In an AC circuit, a resistance of R ohm is connected in series with an inductance L. If phase angle between voltage and current be 45°, the value of inductive reactance will be.
(A) R/4
(B) R/2
(C) R
(D) cannot be found with the given data

- 26. An AC voltage source $V = 200 \sqrt{2}$ sin 100 t is connected across a circuit containing an AC ammeter (it reads rms value) and capacitor of capacity 1 μ F. The reading of ammeter is : (A) 10 mA (B) 20 mA (C) 40 mA (D) 80 mA
- 27. If in a series LCR AC circuit, the rms voltage across L, C and R are V₁, V₂ and V₃ respectively, then the voltage of the source is always :
 (A) equal to V + V + V
 (B) equal to V V + V

A) equal to $V_1 + V_2 + V_3$	(B) equal to $V_1 - V_2 + V_3$
C) more than $V_1 + V_2 + V_3$	(D) none of these is true

28. When 100 V DC is applied across a solenoid, a steady current of 1 A flows in it. When 100 V AC is applied across the same solenoid, the current drops to 0.5 A. If the frequency of the AC source is $150\sqrt{3}/\pi$ Hz, the impedance and inductance of the solenoid are :

(A) 200 Ω and 1/3 H	(B) 100 Ω and 1/16 H
(C) 200 Ω and 1.0 H	(D) 1100 Ω and 3/117 H

29. The value of power factor $\cos\phi$ in series LCR circuit at resonance is :

(A) zero (B) 1 (C) 1/2 (D) 1/2 ohm



Add. 41-42A, Ashok Park Main, New Rohtak Road, New Delhi-110035 +91-9350679141

30.	In the series LCR circuit	In the series LCR circuit as shown in figure, the voltmeter and ammeter readings are :									
	(A) $V = 100$ volt, $I = 2$ am	(B) $V = 100 \text{ volt}$	I = 5 amp								
	(C) $V = 1000$ volt, $I = 2$ ar	mp (D) $V = 300$ volt	I = 1 amp	100V, 50Hz							
31.	A resistor R, an inductor resonant frequency is v_r	r L and a capacitor C are , then the current lags bel	connected in series to an nind voltage, when :	oscillator of frequency v. If the							
	$(\mathbf{A}) \upsilon = 0$	(B) $\upsilon < \upsilon_r$	(C) $\upsilon = \upsilon_r$	(D) $\upsilon > \upsilon_r$							
32.	A series LCR circuit 4×10^3 rad s ⁻¹ . At resona values of L and C are resp	c containing a resistant nce, the voltage across res pectively :	ice of 120 ohm has a istance and inductance are	angular resonance frequency e 60V and 40 V respectively. The							
	(A) 20 mH, 25/8 μF	(B) 2mH, 1/35 μF	(C) 20 mH, 1/40 μF	(D) $2mH$, $25/8 nF$							
33.	In an LCR circuit, the ca in inductance, so that the	pacitance is made one-fo e circuit remains in reson	urth, when in resonance. ance ?	Then what should be the change							
	(A) 4 times	(B) 1/4 times	(C) 8 times	(D) 2 times							
34.	A power transformer (st secondary is $10^4 \Omega$. The	ep up) with an 1 : 8 turn t current in the secondary	ratio has 60 Hz, 120 V ac is	cross the primary; the load in the							
	(A) 96 A	(B) 0.96 A	(C) 9.6 A	(D) 96 mA							
35.	A resistor R, an inductor connected to an oscillato When the frequency o frequency, the voltmeter case of :	L, a capacitor C and volta r in the circuit as shown in f the oscillator is incre reading (at resonance fr	meters V_1 , V_2 and V_3 are the adjoining diagram. ased, upto resonance equency) is zero in the								
	(A) voltmeter V ₁	(B) voltmeter V ₂	(C) voltmeter V_3	(D) all the three voltmeters							
36.	In a step-up transformer found to be 22000 V. Th	the voltage in the primary e current in the secondary	v is 220 V and the current v (neglect losses) is	is 5A. The secondary voltage is							
	(A) 5 A	(B) 50 A	(C) 500 A	(D) 0.05 A							
37.	A transformer is used to 1 0.7 amp. The efficiency of	light a 140 watt, 24 volt la of the transformer is :	mp from 240 V AC mains	. The current in the main cable is							
	(A) 48%	(B) 63.8%	(C) 83.3%	(D) 90%							
38.	A capacitor is a perfect i (A) constant direct curre (C) direct as well as alter	nsulator for : ent rnating current	(B) alternating current(D) variable direct current								
39.	The core of a transforme	r is laminated to reduce									
	(A) eddy current loss	(B) hysteresis loss	(C) copper loss	(D) magnetic loss							
40.	A choke coil is preferred (A) it consumes almost z (C) it increases power	l to a rheostat in AC circu ero power	it as : (B) it increases current (D) it increases voltage								



Add. 41-42A, Ashok Park Main, New Rohtak Road, New Delhi-110035 +91-9350679141

PHYSICS FOR JEE MAIN & ADVANCED

41.	A choke coil sould have	:							
	(A) high inductance and	l high resistance	(B) low inductance and	low resistance					
	(C) high inductance and	l low resistance	(D) low inductance and	high resistance					
42.	With increase in frequen	ncy of an AC supply, the c	apacitive reactance :						
	(A) varies inversely with	h frequency	(B) varies directly with	frequency					
	(C) varies directly as sq	uare of frequency	(D) remains constant						
43.	3. With increase in frequency of an AC supply, the inductive reactance :								
	(A) decreases		(B) increases directly p	roportional to frequency					
	(C) increases as square	of frequency	(D) decreases inversely	with frequency					
44.	In an a.c. circuit consist	ing of resistance R and in	ductance L, the voltage ac	cross R is 60 volt and that across					
	L is 80 volt. The total v	oltage across the combina	tion is						
	(A) 140 V	(B) 20 V	(C) 100 V	(D) 70 V					
45.	An AC ammeter is used	to measure current in a cir	rcuit. When a given direct	constant current passes through					
	the circuit, the AC amm ammeter reads 4 ampere	eter reads 3 ampere. Whe Then the reading of this an	n an alternating current pa meter if DC and AC flow t	asses through the circuit, the AC					

(A) 3 A (B) 4 A (C) 7 A (D) 5 A



is :

Exercise # 2 Part # I [Multiple Correct Choice Type Questions]

- 1. In an AC series circuit when the instantaneous source voltage is maximum, the instantaneous current is zero. Connected to the source may be a
 - (A) pure capacitor
 - (B) pure inductor
 - (C) combination of pure an inductor and pure capacitor
 - (D) pure resistor

3.

2. Average power consumed in an A.C. series circuit is given by (symbols have their usual meaning) :

(A) $E_{rms} I_{rms} \cos \phi$ (B) $(I_{rms})^2 R$ (C) $\frac{E_{max}^2 R}{2(|z|)^2}$ (D) $\frac{I_{max}^2 |z| \cos \phi}{2}$ Power factor may be equal to 1 for : (A) pure inductor (B) pure capacitor (C) pure resistor (D) An LCR circuit

4. In the circuit shown in figure, if both the bulbs B_1 and B_2 are identical :



- (A) their brightness will be the same
- **(B)** B_2 will be brighter than B_1
- (C) as frequency of supply voltage is increased the brightness of bulb B_1 will increase and that of B_2 will decrease.
- (**D**) only B_2 will glow because the capacitor has infinite impedance
- 5. In the AC circuit shown below, the supply voltage has constant rms value V but variable frequency f. At resonance, the circuit :
 - (A) has a current I given by $I = \frac{V}{R}$
 - (B) has a resonance frequency 500 Hz
 - (C) has a voltage across the capacitor which is 180° out of phase with that across the inductor
 - (D) has a current given by I =

$$\frac{V}{\sqrt{R^2 + \left(\frac{1}{\pi} + \frac{1}{\pi}\right)^2}}$$

6. In a series LCR circuit with an AC source ($E_{rms} = 50$ V and $v = 50/\pi$ Hz), R = 300 Ω , C = 0.02 mF, L = 1.0 H, Which of the following is correct

- (A) the rms current in the circuit is 0.1 A
- (B) the rms potential difference across the capacitor is 50 V
- (C) the rms potential difference across the capacitor is 14.1 V
- (D) the rms current in the circuit is 0.14 A





PHYSICS FOR JEE MAIN & ADVANCED

7. Which of the following quantities have zero average value over a cycle. If an inductor coil having some resistance is connected to a sinusoidal AC source. (A) induced emf in the inductor (B) current (C) joule heat (D) magnetic energy stored in the inductor An AC source supplies a current of 10 A (rms) to a circuit, rms voltage of source is 100 V. The average power 8. delivered by the source : (A) must be 1000 W (B) may be less than 1000 W (C) may be greater than 1000 W (D) may be 1000 W A circuit is set up by connecting L = 100 mH, C = 5 μ F and R = 100 Ω in series. An alternating emf of (150 $\sqrt{2}$) 9. volt, $\frac{500}{\pi}$ Hz is applied across this series combination. Which of the following is correct (A) the impedance of the circuit is 141.4Ω (B) the average power dissipated across resistance 225 W (C) the average power dissipated across inductor is zero. (D) the average power dissipated across capacitor is zero. 10. A pure inductance of 1 henry is connected across a 110 V, 70Hz source. Then correct option are (Use $\pi = 22/7$): (A) reactance of the circuit is 440 Ω (B) current of the circuit is 0.25 A (C) reactance of the circuit is 880 Ω (D) current of the circuit is 0.5 A 11. In a series RC circuit with an AC source (peak voltage $E_0 = 50$ V and $f = 50 / \pi$ Hz), R = 300 Ω , C = 25 μ F. Then : (A) the peak current is 0.1 A (B) the peak current is 0.7 A (C) the average power dissipated is 1.5 W (D) the average power dissipated is 3 W 12. A coil of inductance 5.0 mH and negligible resistance is connected to an oscillator giving an output voltage $E = (10V) \sin \omega t$. Which of the following is correct (A) for $\omega = 100 \text{ s}^{-1}$ peak current is 20 A **(B)** for $\omega = 500 \text{ s}^{-1}$ peak current is 4 A (D) for $\omega = 1000 \text{ s}^{-1}$ peak current is 4 A (C) for $\omega = 1000 \text{ s}^{-1}$ peak current is 2 A 11 kW of electric power can be transmitted to a distant station at (i) 220 V or (ii) 22000 V. Which of the 13. following is correct (A) first mode of transmission consumes less power (B) second mode of transmission consumes less power (C) first mode of transmission draws less current (D) second mode of transmission draws less current 14. A town situated 20 km away from a power house at 440 V, requires 600 KW of electric power at 220 V. The resistance of transmission line carrying power is 0.4 Ω per km. The town gets power from the line through a 3000 V-220 V step-down transformer at a substation in the town. Which of the following is/are correct (A) The loss in the form of heat is 640 kW (B) The loss in the form of heat is 1240 kW (C) Plant should supply 1240 kW (D) Plant should supply 640 kW



Part # II **>** [Assertion & Reason Type Questions]

In each of the following questions, a Assertion of Statement -1 and Statement - 2 of Reason.

(A) Statement-1 is True, Statement-2 is True; Statement-2 is a correct explanation for Statement-1.

- (B) Statement-1 is True, Statement-2 is True; Statement-2 is NOT a correct explanation for Statement-1
- (C) Statement-1 is True, Statement-2 is False
- (D) Statement-1 is False, Statement-2 is True
- 1. Statement-1: An inductor is connected to an ac source. When the magnitude of current decreases in the circuit, energy is absorbed by the ac source.

Statement-2: When current through an inductor decreases, the energy stored in inductor decreases.

2. Statement-1: In a series R,L,C circuit if V_R , V_L , and V_C denote rms voltage across R, L and C repectively and V_S is the rms voltage across the source, then $V_S = V_R + V_L + V_C$.



- Statement-2: In AC circuits, kirchoff voltage law is correct at every instant of time.
- 3. Statement-1: The electrostatic energy stored in capacitor plus magnetic energy stored in inductor will always be zero in a series LCR circuit driven by ac voltage source under condition of resonance.

Statement-2 : The complete voltage of ac source appears across the resistor in a series LCR circuit driven by ac voltage source under condition of resonance.

- Statement-1: Average power consumed in an ac circuit is equal to average power consumed by resistors in the circuit.
 - Statement-2: Average power consumed by capacitor and inductor in an ac circuit is zero.



4.

Exercise # 3 Part # I [Matrix Match Type Questions]

1. A steady current 4 A flows in an inductor coil when connected to a 12 V dc source as shown in figure 1. If the same coil is connected to an ac source of 12 V, 50 rad/s, a current of 2.4 A flows in the circuit as shown in figure 2. Now after these observations, a capacitor of capacitance $\frac{1}{50}$ F is connected in series with the coil as shown in figure 3 with the same AC source :



Part # II >> [Comprehension Type Questions]

Comprehension #1

An ac generator G with an adjustable frequency of oscillation is used in the circuit, as shown.



1. Current drawn from the ac source will be maximum if its angular frequency is -

(A) 10^5 rad/s (B) 10^4 rad/s (C) 5000 rad/s (D) 500 rad/s

2. To increase resonant frequency of the circuit, some of the changes in the circuit are carried out. Which change(s) would certainly result in the increase in resonant frequency ?

(A) R is increased.

- **(B)** L_1 is increased and C_1 is decreased.
- (C) L_2 is decreased and C_2 is increased.
- **(D)** C_3 is removed from the circuit.

2.

- 3. If the ac source G is of 100 V rating at resonant frequency of the circuit, then average power supplied by the source is (A) 50 W
 (B) 100 W
 (C) 500 W
 (D) 1000 W
- 4. Average energy stored by the inductor L₂ (Source is at resonance frequency) is equal to (A) zero (B) 1.2 mJ (C) 2.4 mJ (D) 4 mJ
- 5. Thermal energy produced by the resistance R in time duration 1 µs, using the source at resonant condition, is

(A) 0 J
(B) 1 μJ
(C) 100 μJ
(D) not possible to calculate from the given information

Comprehension #2

A voltage source $V = V_0 \sin(100 \text{ t})$ is connected to a black box in which there can be either one element out of L, C, R or any two of them connected in series.



At steady state. the variation of current in the circuit and the source voltage are plotted together with time, using an oscilloscope, as shown



1.The element(s) present in black box is/are :
(A) only C(B) L and C(C) L and R(D) R and C

2. Values of the parameters of the elements, present in the black box are -

(A) $R = 50\Omega$, $C = 200 \mu f$	(B) $R = 50\Omega$, $L = 2m\mu$
(C) $R = 400 \Omega$, $C = 50 \mu f$	(D) None of these

- 3. If AC source is removed, the circuit is shorted for some time so that capacitor is fully discharged and then a battery of constant EMF is connected across the black box, at t = 0. The current in the circuit will -
 - (A) increase exponentially with time constant = 0.02 sec.
 - (B) decrease exponentially with time constant = 0.01 sec.
 - (C) oscillate with angular frequency 20 rad/sec
 - (D) first increase and then decrease



Comprehension #3

In the LCR circuit shown in figure unknown resistance and alternating voltage source are connected. When switch

'S' is closed then there is a phase difference of $\frac{\pi}{4}$ between current and applied voltage and voltage across resister

is $\frac{100}{\sqrt{2}}$ V. When switch is open current and applied voltage are in same phase. Neglecting resistance of connecting wire answer the following questions :





Exercise # 4 [Subjective Type Questions]

- 1. In a LR circuit discharging current is given by $I = I_0 e^{-t/\tau}$ where τ is the time constant of the circuit find the rms current for the period t = 0 to $t = \tau$.
- 2. The household supply of electricity is at 220 V rms value and 50 Hz .Calculate the peak voltage and the minimum possible time in which the voltage can change from the rms value to zero.
- 3. If a direct current of value 'a' ampere is superimposed on an alternating current I = b sin ωt flowing through a wire, what is the effective (rms) value of the resulting current in the circuit?



- 4. A bulb is designed to operate at 12 volts constant direct current. If this bulb is connected to an alternating current source and gives same brightness. What would be the peak voltage of the source ?
- 5. Find the average for the saw-tooth voltage of peak value V_0 from t=0 to t=2T as shown in figure.



- 6. The dielectric strength of air is 3.0×10^6 V/m. A parallel plate air capacitor has area 20 cm² and plate separation $\sqrt{2}$ mm. Find the maximum rms voltage of an AC source which can be safely connected to this capacitor.
- 7. In an ac circuit the instantaneous values of current and applied voltage are respectively i = 2(Amp)sin (250 π s⁻¹)t and $\varepsilon = (10V) \sin [(250 \pi s^{-1})t + \frac{\pi}{3}]$. Find the instantaneous power drawn from the source at $t = \frac{2}{3}$ ms and its average value.
- 8. A resistor of resistance 100 Ω is connected to an AC source $\varepsilon = (12V) \sin (250 \pi \text{ s}^{-1})t$. Find the power consumed by the bulb.
- 9. An electric bulb is designed to consume 55 W when operated at 110 volts. It is connected to a 220 V, 50 Hz line through a choke coil in series. What should be the inductance of the coil for which the bulb gets correct voltage?



- 10. A 20 volts 5 watt lamp (lamp to be treated as a resistor) is used on AC mains of 200 volts and $\frac{50}{\pi}\sqrt{11}$ c.p.s. Calculate the (i) capacitance of the capacitor, or inductance of the inductor, to be put in series to run the lamp. (ii) How much pure resistance should be included in place of the above device so that the lamp can run on its rated voltage. (iii) which is more economical (the capacitor, the inductor or the resistor).
- 11. A resistor, a capacitor and an inductor ($R = 300 \Omega$, $C = 20 \mu$ F, L = 1.0 henry) are connected in series with an AC

source of, $E_{rms} = 50$ V and $v = \frac{50}{\pi}$ Hz. Find

(A) the rms current in the circuit and

- (B) the rms potential differences across the capacitor, the resistor and the inductor.
- 12. Consider the situation of the previous problem calculate the average electric field energy stored in the capacitor and the average magnetic field energy stored in the inductor coil.
- 13. A coil draws a current of 1.0 ampere and a power of 100 watt from an A.C. source of 110 volt and $\frac{5\sqrt{22}}{\pi}$ hertz. Find the inductance and resistance of the coil.
- 14. A circuit has a resistance of 50 ohms and an inductance of $\frac{3}{\pi}$ henry. It is connected in series with a condenser of
 - $\frac{40}{\pi}$ µF and AC supply voltage of 200 V and 50 cycles/sec. Calculate
 - (i) the impedance of the circuit,
 - (ii) the p.d. across inductor coil and condenser.
 - (iii) Power factor

and

15. A series circuit consists of a resistance, inductance and capacitance. The applied voltage and the current at any instant are given by

 $E = \frac{141.4 \text{ cos}}{1 = 5 \text{ cos}} (5000 \text{ t} - 10^\circ)$ $I = 5 \text{ cos} (5000 \text{ t} - 370^\circ)$

The inductance is 0.01 henry. Calculate the value of capacitance and resistance.

- 16. An inductor $2/\pi$ Henry, a capacitor $100/\pi \mu$ F and a resistor 75 Ω are connected in series across a source of emf $V = 10 \sin 100 \pi$ t. Here t is in second.
 - (A) find the impedance of the circuit.
 - (B) find the energy dissipated in the circuit in 20 minutes.
- An inductance of 2.0 H, a capacitance of 18 μF and a resistance of 10 kΩ are connected to an AC source of 20 V with adjustable frequency
 - (A) What frequency should be chosen to maximise the current(RMS) in the circuit?
 - (B) What is the value of this maximum current (RMS) ?
- 18. An electro magnetic wave of wavelength 300 metre can be transmitted by a transmission centre. A condenser of capacity 2.5 μ F is available. Calculate the inductance of the required coil for a resonant circuit.Use $\pi^2=10$.
- 19. An inductor-coil, a capacitor are connected in series with an AC source of rms voltage 24 V. When the frequency of the source is varied a maximum rms current of 6.0 A is observed. If this inductor coil is connected to a DC source of 12 V and having internal resistance 4.0 Ω , what will be the current in steady state?



20. In a transformer ratio of secondary turns (N₂) and primary turns (N₁) i.e. $\frac{N_2}{N_1} = 4$. If the voltage applied in primary

is 200 V, 50 Hz, find

- (A) voltage induced in secondary
- (B) If current in primary is 1A, find the current in secondary if the transformer is (i) ideal and (ii) 80% efficient and there is no flux leakage.
- 21. A transformer has 50 turns in the primary and 100 turns in the secondary. If the primary is connected to a 220 V DC supply, what will be the voltage across the secondary ?
- 22. A series LCR circuit with $L = 0.125/\pi$ H, $C = 500/\pi$ nF, $R = 23 \Omega$ is connected to a 230 V variable frequency supply.
 - (A) What is the source frequency for which current amplitude is maximum? Obtain this maximum value.
 - (B) What is the source frequency for which average power absorbed by the circuit is maximum? Obtain the value of this maximum power.
 - (C) For what reactance of the circuit, the power transferred to the circuit is half the power at resonance? What is the current amplitude at this reactance?
 - (D) If ω is the angular frequency at which the power consumed in the circuit is half the power at resonance, write an expression for ω
 - (E) What is the Q-factor (Quality factor) of the given circuit?
- 23. A circuit containing a 0.1 H inductor and a 500 μ F capacitor in series is connected to a 230 volt, $100/\pi$ Hz supply. The resistance of the circuit is negligible.
 - (A) Obtain the current amplitude and rms values.
 - (B) Obtain the rms values of potential drops across each element.
 - (C) What is the average power transferred to the inductor?
 - (D) What is the average power transferred to the capacitor?
 - (E) What is the total average power absorbed by the circuit? ['Average' implies average over one cycle.]
- 24. A 2000 Hz, 20 volt source is connected to a resistance of 20 ohm, an inductance of $0.125/\pi$ H and a capacitance of $500/\pi$ nF all in series. Calculate the time in which the resistance (thermal capacity = 100 joule/°C) will get heated by 10° C. (Assume no loss of heat)
- 25. An LCR circuit has L = 10 mH, $R = 150 \Omega$ and $C = 1 \mu \text{F}$ connected in series to a source of $150 \sqrt{2} \cos \omega t$ volt. At a frequency that is 50% of the resonant frequency, calculate
 - (A) the net reactance of the circuit.
 - (B) the current amplitude and the average power dissipated per cycle
- 26. Find the rms value for the saw-tooth voltage of peak value V_0 from t=0 to t=2T as shown in figure.





PHYSICS FOR JEE MAIN & ADVANCED

E	xercise # 5	Part # I Prev	ious Year Ques	tions] [AIEEE/JEE-M	[AIN]
1.	In an oscillating LC of is stored equally betw	circuit the maximum charge on t ween the electric and magnetic	he capacitor is Q. 7 field is :	The charge on the capacitor	when the energy [AIEEE 2003]
	(1) Q/2	(2) $Q/\sqrt{3}$	(3) Q/ $\sqrt{2}$	(4) Q	
2.	The core of any trans	sformer is laminated so as to :			[AIEEE 2003]
	(1) reduce the energ(3) make is robust an	y loss due to eddy currents nd strong	(2) make it light(4) increase the	weight secondary voltage	
3.	In an LCR series a.c. LC combination will	circuit, the voltage across each be :	of the components	s. L, C and R is 50 V. The v	oltage across the [AIEEE 2004]
	(1) 50 V	(2) $50\sqrt{3}$ s	(3) 100 V	(4) 0 V (zero)	
4.	Alternating current c (1) A.C. current pass (2) A.C. change direc (3) average value of (4) D.C. ammeter wil	an not be measured by D.C. an through d.C. ammeter ction current for complete cycle is ze	nmeter because : ro		[AIEEE 2004]
5.	In an LCR circuit, c	apacitance is changed from C	to 2C. For the res	sonant frequency to remain	unchanged, the
	inductance should be	e changed from L to :			[AIEEE 2004]
	(1) 4L	(2) 2L	(3) L/2	(4) L/4	
6.	A circuit has a resista	ance of 12 ohm and an impedan	ce of 15 ohm. The	power factor of the circuit	will be : [AIEEE 2005]
-	(1) 0.8	(2) 0.4	(3) 1.25	(4) 0.125	.1 .1
7.	ent of the circuit?	between the alternating current	and emf is $\pi/2$. W	hich of the following canno	[AIEEE 2005]
0	(1) C alone	(2) R, L	(3) L, C	(4) L alone	
8.	In a series LCR circ respectively. On takin the inductor from the	Further $R = 200 \Omega$ and the voltaging out the capacitance from the end of the current leads the voltage of the current leads the curre	e and the frequence circuit the current l ltage by 30°. The p	ags behind the voltage by 3 ower dissipated in the LCI	20 V and 50 Hz 0°. On taking out R circuit is
	(1) 305 W	(2) 210 W	(3) Zero W	(4) 242 W	
9.	An LCR circuit is ec connected to the L a	quivalent to a damped pendulu nd R as shown below :	m. In an LCR circ	uit the capacitor is charge	d to Q_0 and then E-MAIN : 2015]
			00000		
	If a student plots gra	phs of the square of maximum	charge (Q^2_{max}) on t	he capacitor with time (T)	for two different
	values L_1 and L_2 (L_1	> L ₂) of L then which of the following	lowing represents t	his graph correctly? (Plots	are shematic and
	not drawn to scale)			I	
	Q ² _{Max}	$Q^2_{Max} = Q_0$ (For both L ₁ and L ₂)	Q ² _{Max}	L ₁ Q ² _{Max}	-2
	(1) L ₂	t (2) $t \rightarrow t$	(3) L ₂	\rightarrow t (4) L_1	>t



→t

→t



(A) the bulb glows dimmer(C) total impedence of the circuit is unchanged

- (D) total impedence of the circuit increases
- 4. You are given many resistances, capacitors and inductors. These are connected to a variable DC voltage source (the first two circuits) or an AC voltage source of 50 Hz frequency (the next three circuits) in different ways as shown in Column II. When a current I (steady state for DC or rms for AC) flows through the circuit, the corresponding voltage V₁ and V₂. (indicated in circuits) are related as shown in Column I. Match the two column.

[**JEE 2010**]











Add. 41-42A, Ashok Park Main, New Rohtak Road, New Delhi-110035 +91-9350679141

- In an AC circuit the potential differences across an inductance and resistance joined in series are respectively 16 V and 20 V. The total potential difference across the circuit is
 (A) 20 V
 (B) 25.6 V
 (C) 31.9 V
 (D) 53.5 V
- 8. Current in an ac circuit is given by $i = 3 \sin \omega t + 4 \cos \omega t$ then : (A) rms value of current is 5 A.
 - (B) mean value of this current in one half period will be $6/\pi$.
 - (C) if voltage applied is $V = V_m \sin \omega t$ then the circuit must be containing resistance and capacitance.
 - (D) if voltage applied is $V = V_m \sin \omega t$, the circuit may contain resistance and inductance.
- 9. A current source sends a current $i = i_0 \cos(\omega t)$. When connected across an unknown load gives a voltage output of, $v = v_0 \sin(\omega t + \pi/4)$ across that load. Then voltage across the current source may be brought in phase with the current through it by:

(B) $2\sqrt{2}$ A (D) $\sqrt{0.4}$ A

- (A) connecting an inductor in series with the load
- (B) connecting a capacitor in series with the load
- (C) connecting an inductor in parallel with the load
- (D) connecting a capacitor in parallel with the load.
- 10. In the circuit diagram shown, $X_C = 100 \Omega$, $X_L = 200 \Omega \&$ R = 100 Ω . The effective current through the source is:
 - (A) 2 A
 - (C) 0.5 A
- 11. If the readings of v_1 and v_3 are 100 volt each then reading of v_2 is :
 - (A) 0 volt
 - (B) 100 volt
 - (C) 200 volt
 - (D) cannot be determined by given information.
- 12. For a LCR series circuit with an A.C. source of angular frequency ω .
 - (A) circuit will be capacitive if $\omega > \frac{1}{\sqrt{LC}}$
 - **(B)** circuit will be inductive if $\omega = \frac{\Gamma}{\sqrt{LC}}$
 - (C) power factor of circuit will by unity if capacitive reactance equals inductive reactance
 - (**D**) current will be leading voltage if $\omega > \frac{1}{\sqrt{LC}}$
- 13. The value of current in two series L C R circuits at resonance is same when connected across a sinusoidal voltage source. Then:
 - (A) both circuits must be having same value of capacitance and inductor
 - (B) in both circuits ratio of L and C will be same
 - (C) for both the circuits X_L/X_C must be same at that frequency
 - (D) both circuits must have same impedance at all frequencies.
- 14. In series LCR circuit voltage drop across resistance is 8 volt, across inductor is 6 volt and across capacitor is 12 volt. Then:
 - (A) voltage of the source will be leading current in the circuit
 - (B) voltage drop across each element will be less than the applied voltage
 - (C) power factor of circuit will be 4/3
 - (D) none of these





200 V, 50 Hz

7

۰t

the

T/2

(D) zero

T/4

- 15. In a black box of unknown elements (L, C or R or any other combination) an AC voltage $E = E_0 \sin(\omega t + \phi)$ is applied and current in the circuit was found to be $i = i_0 \sin(\omega t + \phi + \pi/4)$. Then the unknown elements in the box may be :
 - (A) only capacitor
 - **(B)** inductor and resistor both
 - (C) either capacitor, resistor and inductor or only capacitor and resistor
 - (D) only resistor
- 16. The voltage time (V t) graph for triangular wave having peak value. V_0 is as shown in figure.

The rms value of V in time interval from t = 0 to $\frac{T}{4}$ is :

(B) $\frac{V_0}{2}$



17. In the above questions the average value of voltage (v) in one time period will be :

(A)
$$\frac{V_0}{\sqrt{3}}$$

18.A series AC circuit has resistance of 4 Ω and a reactance of 3 Ω . The impedance(Z) of the circuit is(A) 5 Ω (B) 7 Ω (C) 12/7 Ω (D) 7/12 Ω

(C) $\frac{V_0}{\sqrt{2}}$



20. What is the amount of power delivered by the ac source in the circuit shown (in watts).

		X _c =12Ω R X _c =8Ω 	=5Ω R ₂ =6Ω 		
	(A) 500 watt	(B) 1014 watt	(C) 1514 watt	(D) 2013 watt	
21.	The secondary coil or ratio of turns in the p	of an ideal step down tran primary to the secondary i	sformer is delivering 50 s 5 : 1, then the current f	0 watt power at 12.5 A cur lowing in the primary coil	rent. If th will be :
	(A) 62.5 A	(B) 2.5 A	(C) 6 A	(D) 0.4 A	



Add. 41-42A, Ashok Park Main, New Rohtak Road, New Delhi-110035 +91-9350679141

SECTION - II : MULTIPLE CORRECT ANSWER TYPE

V/

KKKKK

- **22.** Graph shows variation of source emf V and current *i* in a series RLC circuit, with time.
 - (A) The current leads the emf in the circuit.
 - (B) The circuit is more inductive than capacitive.
 - (C) To increase the rate at which energy is transferred to the resistive load, L should be decreased.
 - (D) To increase the rate at which energy is transferred to the resistive load, C should be decreased.
- 23. In the given AC circuit, which of the following is incorrect :



- (A) Voltage across resistance is lagging by 90° than the voltage across capacitor.
- (B) voltage across capacitor is lagging by 180° than voltage across inductor.
- (C) voltage across inductor is leading by 90° than voltage across resistance.
- (D) Resistance of the circuit is equal to reactance of circuit.



capacitance $C = \frac{8}{\pi} \mu F$ are connected in series with an ac source of 200 volt and frequency 'f'. If the readings of the hot wire voltmeters V_1 and V_2 are same then :

(A) f = 125 Hz
(C) current through R is 2A



25. An alternating emf of frequency $\left(v = \frac{1}{2\pi\sqrt{LC}}\right)$ is applied to a series LCR circuit. For the frequency of the applied emf,

- (A) the current is at 'resonance' and its impedance is made up only of a reactive part
- (B) the current in the circuit is in phase with the applied emf and the voltage across R equals this applied emf.
- (C) the sum of the p.d.'s across the inductance and capacitance equals the applied emf which is 180° ahead of phase of the current in the circuit.
- (D) the quality factor of the circuit is $\omega L/R$ or $1/\omega CR$ and this is a measure of the voltage magnification (produced by the circuit at resonance) as well as the sharpness of resonance of the circuit

SECTION - III : ASSERTION AND REASON TYPE

26.

- Statement-1 : The D.C. and A.C. both can be measured by a hot wire instrument.
- **Statement-2**: The hot wire instrument is based on the principle of magnetic effect of current.
- (A) Statement-1 is True, Statement-2 is True; Statement-2 is a correct explanation for Statement-1
- (B) Statement-1 is True, Statement-2 is True; Statement-2 is NOT a correct explanation for Statement-1
- (C) Statement-1 is True, Statement-2 is False
- (D) Statement-1 is False, Statement-2 is True.



27. Statement-1: In a series R,L,C circuit if V_R , V_L , and V_C denote rms voltage across R, L and C respectively and V_S is the rms voltage across the source, then $V_S = V_R + V_L + V_C$.



Statement-2 : In AC circuits, kirchoff voltage law is correct at every instant of time.

- (A) Statement-1 is True, Statement-2 is True; Statement-2 is a correct explanation for Statement-1
- (B) Statement-1 is True, Statement-2 is True; Statement-2 is NOT a correct explanation for Statement-1
- (C) Statement-1 is True, Statement-2 is False
- **(D)** Statement-1 is False, Statement-2 is True.
- 28. Statement-1 : The electrostatic energy stored in capacitor plus magnetic energy stored in inductor will always be zero in a series LCR circuit driven by ac voltage source under condition of resonance.

Statement-2 : The complete voltage of ac source appears across the resistor in a series LCR circuit driven by ac voltage source under condition of resonance.

(A) Statement-1 is True, Statement-2 is True; Statement-2 is a correct explanation for Statement-1

- (B) Statement-1 is True, Statement-2 is True; Statement-2 is NOT a correct explanation for Statement-1
- (C) Statement-1 is True, Statement-2 is False
- **(D)** Statement-1 is False, Statement-2 is True.
- 29. Statement-1 : An inductor is connected to an ac source. When the magnitude of current decreases in the circuit, energy is absorbed by the ac source.

Statement-2 : When current through an inductor decreases, the energy stored in inductor decreases.

(A) Statement-1 is True, Statement-2 is True; Statement-2 is a correct explanation for Statement-1

- (B) Statement-1 is True, Statement-2 is True; Statement-2 is NOT a correct explanation for Statement-1
- (C) Statement-1 is True, Statement-2 is False
- (D) Statement-1 is False, Statement-2 is True.

SECTION - IV : COMPREHENSION TYPE

Comprehension #1

A steady current 4 A flows in an inductor coil when connected to a 12 V dc source as shown in figure 1. If the same coil is connected to an ac source of 12 V, 50 rad/s, a current of 2.4 A flows in the circuit as shown in figure 2. Now after these observations, a capacitor of capacitance $\frac{1}{50}$ F is connected in series with the coil and with the same AC source as shown in figure 3 :



B

Comprehension #2

In a series L-R circuit, connected with a sinusoidal ac source, the maximum potential difference across L and R are respectively 3 volts and 4 volts.

- **33.** At an instant the potential difference across resistor is 2 volts. The potential difference in volt, across the inductor at the same instant will be :
 - (A) $3\cos 30^{\circ}$ (B) $3\cos 60^{\circ}$ (C) $6\cos 45^{\circ}$ (D) 6
- 34. At the same instant, the magnitude of the potential difference in volt, across the ac source will be (A) $3 \cos 67^{\circ}$ (B) $5 \sin 67^{\circ}$ (C) $6 \cos 97^{\circ}$ (D) 0
- 35. If the current at this instant is decreasing the magnitude of potential difference at that instant across the ac source is
 (A) Increasing
 (B) Decreasing
 (C) constant
 (D) cannot be said

Comprehension #3

An ac generator G with an adjustable frequency of oscillation is used in the circuit, as shown.



- 36. Current drawn from the ac source will be maximum if its angular frequency is (A) 10⁵ rad/s
 (B) 10⁴ rad/s
 (C) 5000 rad/s
 (D) 500 rad/s
- 37. To increase resonant frequency of the circuit, some of the changes in the circuit are carried out. Which change(S) would certainly result in the increase in resonant frequency ?

 (A) R is increased.
 (B) L₁ is increased and C₁ is decreased.
 (C) L₂ is decreased and C₂ is increased.
 (D) C₃ is removed from the circuit.
- 38. If the ac source G is of 100 V rating at resonant frequency of the circuit, then average power supplied by the source is (A) 50 W
 (B) 100 W
 (C) 500 W
 (D) 1000 W
- 39. Average energy stored by the inductor L_2 (Source is at resonance frequency) is equal to (A) zero (B) 1.2 mJ (C) 2.4 mJ (D) 4 mJ
- 40. Thermal energy produced by the resistance R in time duration 1 μs, using the source at resonant condition, is
 (A) 0 J
 (B) 1 μJ
 (C) 100 μJ
 (D) not possible to calculate from the given information

SECTION - V : MATRIX - MATCH TYPE

41. In Column I, variation of current i with time t is given in figures. In column II root mean square current i_{ms}, and average current is given. Match the column I with corresponding quantities given in Column II





Add. 41-42A, Ashok Park Main, New Rohtak Road, New Delhi-110035 +91-9350679141



42. Four different circuit components are given in each situation of column-I and all the components are connected across an AC source of same angular frequency $\omega = 200$ rad/sec. The information of phase difference between the current and source voltage in each situation of column-I is given in column-II. Match the circuit components in column-I with corresponding results in column-II.

Column - I



Column - II (P) the magnitude of required phase difference is $\frac{\pi}{2}$.

<u>г</u>

(Q) the magnitude of required phase difference is $\frac{\pi}{4}$.

(R) the current leads in phase to source voltage.

(S) the magnitude of required phase difference is zero.(T) the current lags in phase to source voltage.

SECTION - VI : INTEGER TYPE

43. Find the average value of current from t = 0 to $t = \frac{2\pi}{\omega}$ if the current varies as $i = I_m \sin \omega t$.

- 44. Find the rms value of current from t = 0 to $t = \frac{2\pi}{\omega}$ if the current varies as $i = I_m \sin \omega t$.
- 45. In a series LCR circuit with an ac source E₀ = 50 V, R = 300Ω, frequency v = ⁵⁰/_π Hz. The average electric field energy stored in the capacitor and average magnetic energy stored in the coil are 25 mJ and 5 mJ respectively of RMS current in the circuit is .10 A. Then find:
 (A) Capacitance (C) of capacitor in μ f
 (B) Inductance (L) of inductor.in Henri
- 46. An inductor $(x_L = 2\Omega)$, a capacitor $(x_C = 8\Omega)$ and a resistance (8Ω) are connected in series with an AC source. The voltage output of A.C source is given by $v = 10 \cos 100\pi t$.
 - (A) Find the impedance of the circuit(in Ω).
 - (B) the instantaneous p.d. between A and B when it is half of the voltage output from

source at that instant is $\frac{x}{5}$ volt then x is.





ANSWER KEY

EXERCISE - 1

4. D 5. D 6. C 7. B 8. D 9. A 10. C 11. C 12. B 13. B **1.** B **2.** B **3.** C 14. B 15. A 16. D 17. B 18. A 19. B 20. B 21. D 22. D 23. C 24. B 25. C 26. B 27. D 28. A 29. B **30.** A 31. D 32. A 33. A 34. D 35. B 36. D 37. C 38. A 39. A 40. A 41. C 42. A 43. B 44. C 45. D

EXERCISE - 2 : PART # I

1. A,B,C	2. A,B,C,D	3. C,D	4. B,C	5. A,B,C	6. A,B	7. A,B	8. B,D	9. A,B,C,D
10. A,B	11. A,C	12. A,B,C	13. B,D	14. A,C				

PART # II

1. A 2. D 3. D 4. A

EXERCISE - 3 : PART # I

1. $A \rightarrow R$; $B \rightarrow Q$; $C \rightarrow P$; $D \rightarrow Q$ 2. $A \rightarrow Q,R$; $B \rightarrow Q,R$; $C \rightarrow P,Q,R,S$; $D \rightarrow Q,R,S$

PART # II

 Comp. #1 : 1.
 C
 2.
 D
 3.
 B
 4.
 B
 5.
 D
 Comp. #2 : 1.
 D
 2.
 A
 3.
 B

 Comp. #3 : 1.
 C
 2.
 B
 3.
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 C
 <

EXERCISE - 4

1.
$$\frac{I_o}{e}\sqrt{(e^2-1)/2}$$
 2. 220 $\sqrt{2}$ V, 2.5 ms **3.** $I_{eff} = \left[a^2 + \frac{1}{2}b^2\right]^{1/2}$ **4.** 12 $\sqrt{2}$ volts **5.** 0 **6.** 3.0 kV **7.** 10 W, 5 W

8.0.72 W

W 9.
$$\frac{2.2\sqrt{3}}{\pi} = 1.2 \text{ H} = \frac{7\sqrt{3}}{10} \text{ H}$$

10. (i) $\frac{125}{33} \mu$ F or 2.4 H (ii) 720 Ω (iii) It will be more economical to use inductance or capacitance in series with the lamp to run it as it. It consumes no power while there would be dissipation of power when resistance is inserted in series with the lamp.

- 11. (A) 0.1 A (B) 50 V, 30 V, 10 V (Note that the sum of the RMS potential differences across the three elements is greater than the rms voltage of the source.)
- **12.** 25 mJ, 5mJ **13.** $\sqrt{\frac{21}{22}}$ H, -100 Ω **14.** Z = 50 $\sqrt{2}$ ohm, V_c = 500 $\sqrt{2}$ volt and V_L = 600 $\sqrt{2}$ volt, $\frac{1}{\sqrt{2}}$ **15.** 4 µF, R = $\frac{141.4}{5} \Omega$ **16.** 125 Ω , 288 J **17.** (A) $\frac{250}{3\pi}$ Hz (B) 2 mA **18.** 1×10⁻⁸ henry **19.** 1.5 A **20.** (A) 800 V (B) (i) 0.25 A (ii) 0.2 A **21.** zero **22.** (A) 2000 Hz, 10 $\sqrt{2}$ A (B) 2000 Hz, 2300 watt (C) 23 Ω , 10 A.



(D)	0.125 π	$-\frac{1\times1}{\omega\frac{50}{2}}$	$\frac{0^9}{\frac{00}{\pi}} =$	±23 (E)	500/2	23 23. (A	A) 23	$\sqrt{2}$ A, 2	23 A	(B) 460 volt, 2	30 volt (C) ze	ero (D) zero	o (E) zero	
24.	50 sec.	25. (a)) 150 9	Ω (b)1	amp, ′	75 watt.	26	$\frac{V_0}{\sqrt{3}}$							
	EXERCISE - 5 : PART # I														
1. 0	3	2.	1	3.	4	4.	3	5.	3	6.	1	7.	2	8.	4
9.	9. 3 PART # II														
1.	А		2.	20 A,	$\frac{\pi}{4}$	3.	В	4.	A-	\rightarrow R,S,T ; B \rightarrow	Q,R,S,T	;C-	→ P,Q ; D -	→Q,R,S,T	
5.	B,C		6.	4	7.	A,C o	or C	Since I _{rr}	_{ns} ≈	0.3 A so A ma	y or may	not l	oe correct.	8. C,D	
							I	моск	TE	ST					
1.	А	2. B		3. D		4. A		5. D		6 A	7. B		8. C	9. A	
10.	В	11. C		12. C		13. C		14. D		15. C	16. A		17. D	18. A	
19.	В	20. C		21. B		22. B,C		23. A,I)	24. A,C,D	26. C		27. D	28. D	
29.	A	30. D		31. C		32. A		33. A		34. B	35. D		36. C	37. D	
38. 41.	$ \begin{array}{c} B \\ A \rightarrow S \\ I \\ I_m \end{array} $	$39. B \rightarrow P,$	R, S ;	40. D C \rightarrow Q,	S, T ;	$D \rightarrow Q, T$	Т	42. A –	→Q,	$\mathbf{R};\mathbf{B}\to\mathbf{P},\mathbf{T};$	$C \rightarrow P, I$	R ; D	\rightarrow Q, T	43. 0.	
44.	$\sqrt{1}\sqrt{2}$														

