
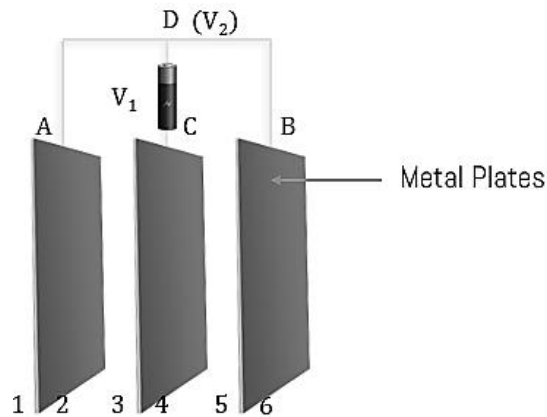


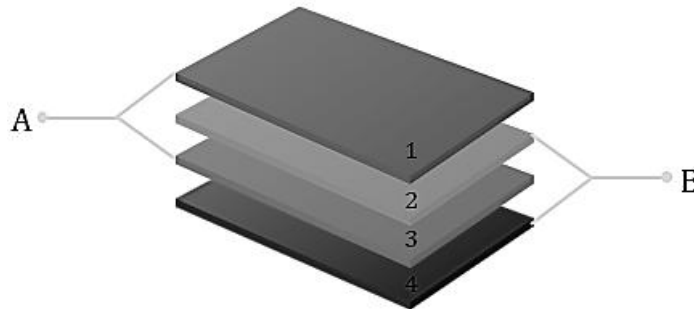- Q.1** Each of the three plates shown in the figure has area of  $400 \text{ cm}^2$  on one side and the gap between the adjacent plates is  $8.85 \text{ mm}$ . The equivalent capacitance of the system is  
 (A)  $70.8 \text{ pF}$  (B)  $80 \text{ pF}$  (C)  $160 \text{ pF}$  (D)  $40 \text{ pF}$




- Q.2** Four metal plates numbered 1, 2, 3 and 4 are arranged as shown below. The area of each plate is  $A$  and separation between adjacent plates is  $d$ . The capacitance of the arrangement is  
 (A)  $\frac{\epsilon_0 A}{d}$  (B)  $\frac{2\epsilon_0 A}{d}$  (C)  $\frac{3\epsilon_0 A}{d}$  (D)  $\frac{4\epsilon_0 A}{d}$




- Q.3** Four capacitors  $C_1$ ,  $C_2$ ,  $C_3$  and  $C_4$  of capacitance  $3 \mu\text{F}$ ,  $4 \mu\text{F}$ ,  $6 \mu\text{F}$  and  $2 \mu\text{F}$  are charged up to a potential difference of  $2 \text{ V}$ ,  $3 \text{ V}$ ,  $4 \text{ V}$  and  $4 \text{ V}$  respectively, if terminal a is connected with f, terminal d is connected with g, terminal e is connected to h and b is connected c, then find the charge flows in the circuit?

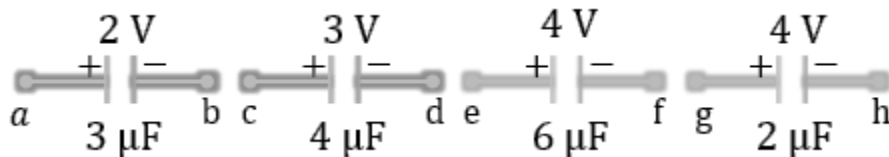- (A)  $26 \mu\text{C}$  (B)  $18 \mu\text{C}$  (C)  $\frac{156}{16} \mu\text{C}$  (D)  $\frac{156}{15} \mu\text{C}$



- Q.4** Consider the situation shown in figure, the switch  $S$  open for a long time and then closed. Then work done by the battery will be:

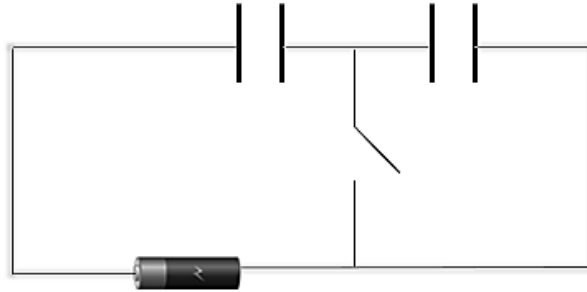- (A)  $\frac{CE^2}{2}$  (B)  $\frac{CE^2}{4}$  (C)  $2CE^2$  (D)  $\frac{CE^2}{8}$




**Q.5** The following arrangement consists of five identical metal plates parallel to each other. Area of each plate is  $A$  and separation between the successive plates is  $d$ . The capacitance between P and Q is

(A)  $\frac{5\epsilon_0 A}{d}$

(B)  $\frac{7\epsilon_0 A}{3d}$

(C)  $\frac{4\epsilon_0 A}{3d}$

(D)  $\frac{5\epsilon_0 A}{3d}$

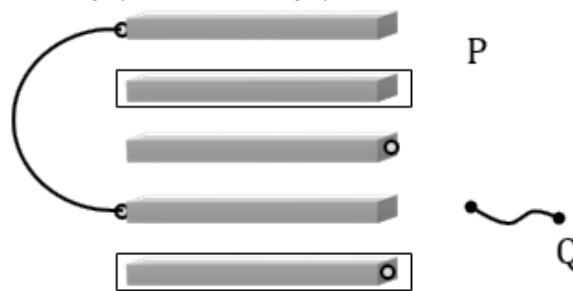


**Q.6** Five conducting parallel plates having area  $A$  and separation between them  $d$  are placed as shown in figure. Plate number 2 and 4 are connected and between points A and B a cell of emf  $E$  is connected. The charge flow through the cell is

(A)  $\frac{3\epsilon_0 AE}{4d}$

(B)  $\frac{2\epsilon_0 AE}{3d}$

(C)  $\frac{4\epsilon_0 AE}{d}$

(D)  $\frac{\epsilon_0 AE}{d}$

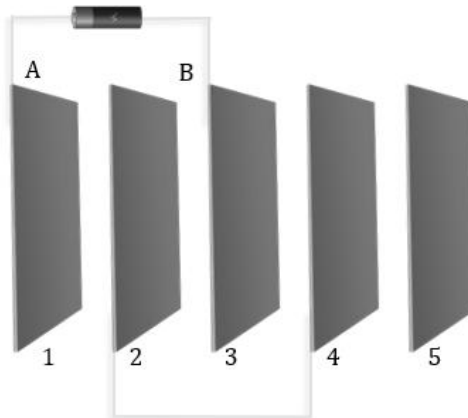


**Q.7** If the two terminals of a battery of 21 V is connected across A and B, the charge flown through the battery will be Given:  $C_1 = 2 \text{ pF}$ ;  $C_2 = 13 \text{ pF}$ ;  $C_3 = 6 \text{ pF}$ ;  $C_4 = 1 \text{ pF}$ ; and  $C_5 = 12 \text{ pF}$

(A)  $5.4 \times 10^{-12} \text{ C}$

(B)  $5.4 \times 10^{-13} \text{ C}$

(C)  $5.4 \times 10^{-10} \text{ C}$

(D)  $5.4 \times 10^{-11} \text{ C}$

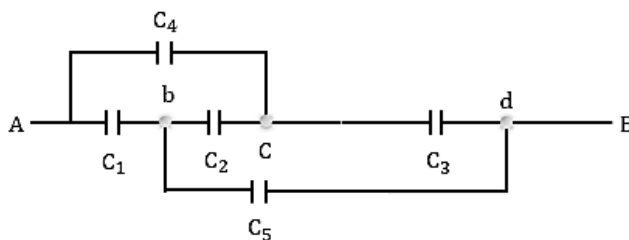


**Q.8** The net capacity between the points A and B in the following circuit will be

(A)  $C$

(B)  $\frac{C}{2}$

(C)  $2C$

(D)  $4C$

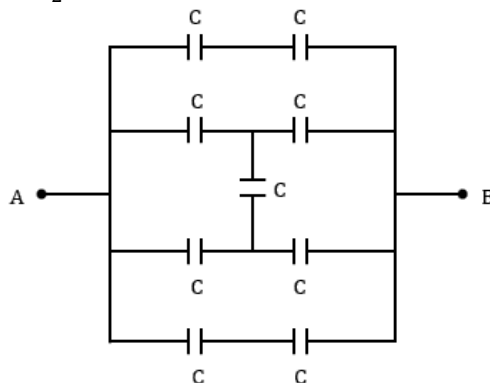


**Q.9** Four metal plates numbered 1,2,3 and 4 are arranged as shown below. The area of each plate is A and separation between adjacent plates is d. The capacitance of the arrangement is

(A)  $\frac{\epsilon_0 A}{d}$

(B)  $\frac{2\epsilon_0 A}{d}$

(C)  $\frac{3\epsilon_0 A}{d}$

(D)  $\frac{4\epsilon_0 A}{d}$

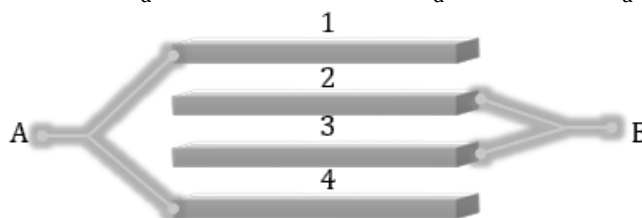

**Q.10** Five similar condenser plates, each of area A are placed at equal distance d apart and are connected to source voltage V as shown in the following diagram. The charge on plates 1 and 4 will be:

(A)  $\frac{\epsilon_0 A}{d}, \frac{-2\epsilon_0 A}{d}$

(B)  $\frac{\epsilon_0 AV}{d}, \frac{-2\epsilon_0 AV}{d}$

(C)  $\frac{-\epsilon_0 AV}{d}, \frac{-3\epsilon_0 AV}{d}$

(D)  $\frac{\epsilon_0 AV}{d}, \frac{-4\epsilon_0 AV}{d}$


## WORKSHEET

## Ideal Gas Equation

- Q.1 12 g He and 4 g  $H_2$  filled in a container of volume 20 L maintained at temperature 300 K. The pressure of the mixture is nearly  
 (A) 3.225 atm (B) 225 atm (C) 6.225 atm (D) 1.225 atm

## Young's Modulus of Elasticity

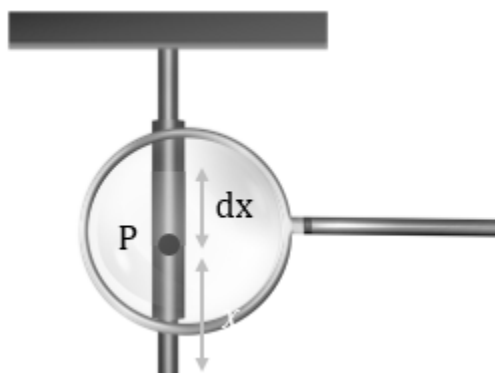- Q.2 The extension in a uniform rod of length  $l$ , mass  $m$ , cross sectional area  $A$  and young's modulus  $Y$  when it is suspended vertically at one end is  
 (A)  $\frac{mgl}{AY}$  (B)  $\frac{mgl}{2AY}$  (C)  $\frac{2mgl}{AY}$  (D)  $\frac{mgl}{4AY}$




## Root Mean Square Speed

- Q.3 At what temperature root mean square velocity of hydrogen becomes double of its value at S.T.P, keeping pressure constant?  
 (A) 273°C (B) 514°C (C) 819°C (D) 1012°C


## Equilibrium

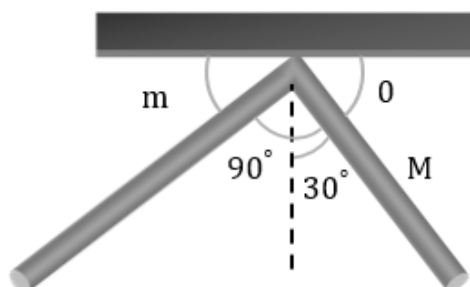- Q.4 Two uniform rods of equal length but of different masses are rigidly combined to form a L-shaped body, which is then pivoted about O as shown in figure. If combination is in equilibrium then ratio  $M/m$  will be  
 (A) 2 (B) 3 (C)  $\sqrt{2}$  (D)  $\sqrt{3}$




## Excess Pressure in Bubbles

- Q.5 A water droplet splits into 27 identical small droplets. The pressure difference between the inner and outer surface of the big droplet will be  
 (A) Same as that of smaller droplet  
 (B) 1/3rd of the pressure difference for a smaller droplet.  
 (C) 1/4th of the pressure difference for a smaller droplet.  
 (D) None of these

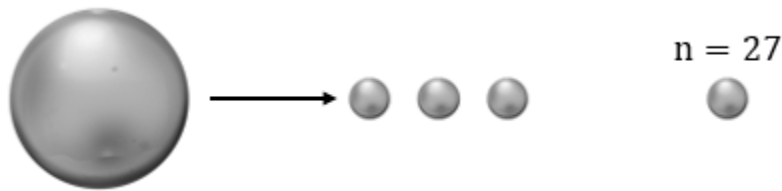**Relative Motion**

**Q.6** Two fixed frictionless inclined planes making the angles  $30^\circ$  and  $60^\circ$  with the horizontal are shown in the figure. Two blocks A and B are placed on the two planes. What is the relative vertical acceleration of A with respect of B?

- (A)  $4.9 \text{ ms}^{-2}$  in vertical direction  
 (B)  $9.8 \text{ ms}^{-2}$  in vertical direction  
 (C) Zero  
 (D)  $9.8 \text{ ms}^{-2}$  in vertical direction

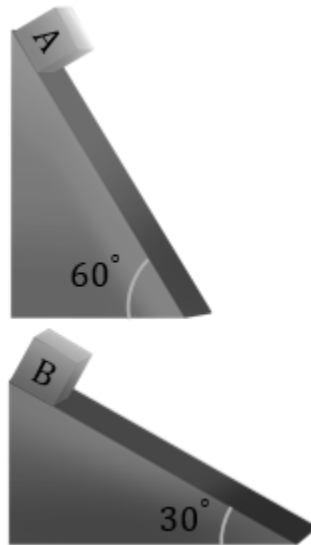**Superposition of Electric Fields**

**Q.7** Three charges  $2q$ ,  $-q$  and  $-q$  are located at the vertices of an equilateral triangle. At the center of the triangle,

- (A) The field is zero but potential is non-zero  
 (B) The field is non-zero but potential is zero  
 (C) Both field and potential are zero  
 (D) both field and potential are non-zero

**Relative Motion**


**Q.8** A man can row a boat at  $4 \text{ km/hr}$  in still water. If he is travelling in a river where the current is  $2 \text{ km/hr}$ , how long will it take him to row  $6 \text{ km}$  upstream and then back to his starting point?

- (A)  $0.5 \text{ hr}$  (B)  $1 \text{ hr}$  (C)  $2 \text{ hr}$  (D)  $4 \text{ hr}$

**Equilibrium**

**Q.9** A body of mass  $1 \text{ kg}$  lies on a smooth inclined plane. A horizontal force  $F = 10 \text{ N}$  is applied on the block of mass  $1 \text{ kg}$  as shown in figure. If the block remains at rest, then the magnitude of normal reaction on the block is (Take  $g = 10 \text{ m/s}^2$ )

- (A)  $10\sqrt{2} \text{ N}$  (B)  $\frac{10}{\sqrt{2}} \text{ N}$  (C)  $10 \text{ N}$  (D) None of these

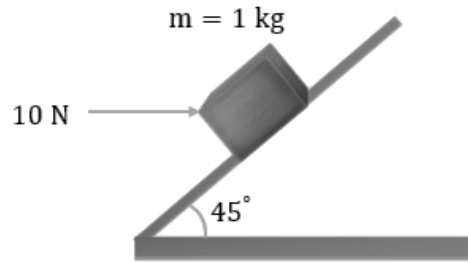**Electric Field Due to an Arc at the Centre**


**Q.10** Half ring of radius  $a$  is uniformly charged with linear charge density  $\lambda$ . Find out electric field intensity at point  $O$ .

(A)  $\frac{\lambda}{2\pi\epsilon_0 a}(-\hat{i})$

(B)  $\frac{\lambda}{4\pi\epsilon_0 a}(+\hat{i})$

(C)  $\frac{\lambda}{2\pi\epsilon_0 a}(+\hat{i})$

(D)  $\frac{\lambda}{4\pi\epsilon_0 a}(-\hat{i})$

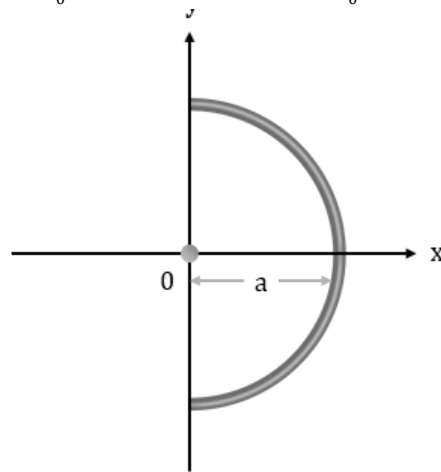**Parallel and Series Combination of Capacitors**

**Q.11** Find the equivalent capacitance between A and B of the circuit shown in the figure.


Given:  $C_1 = 5 \mu\text{F}$ ,  $C_2 = 20 \mu\text{F}$ ,  $C_3 = 10 \mu\text{F}$ ,  $C_4 = 40 \mu\text{F}$ ,  $C_5 = 30 \mu\text{F}$

(A)  $12 \mu\text{F}$

(B)  $24 \mu\text{F}$

(C)  $6 \mu\text{F}$

(D)  $21 \mu\text{F}$

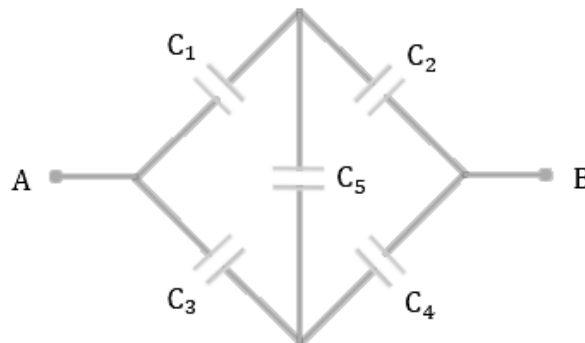**Energy of a Capacitor**


**Q.12** Each capacitor in the figure has a capacitance of  $10 \mu\text{F}$ . The emf of the battery is  $100 \text{ V}$ . Find the ratio of the energy stored in b to a.

(A)  $0.25$

(B)  $4$

(C)  $25$

(D)  $0.4$

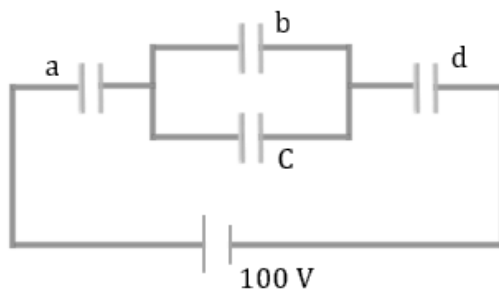

### Parallel and Series Combination of Capacitors


**Q.13** What is the equivalent capacitance of the system of capacitors between A and B

(A)  $\frac{7}{6}C$

(B)  $1.6C$


(C)  $C$


(D) None

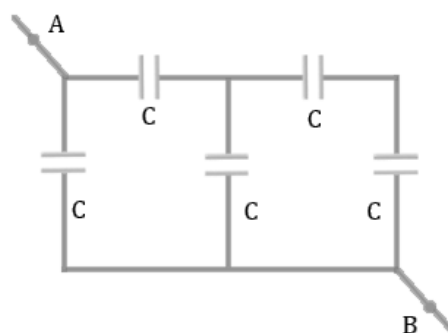

### Potential Difference

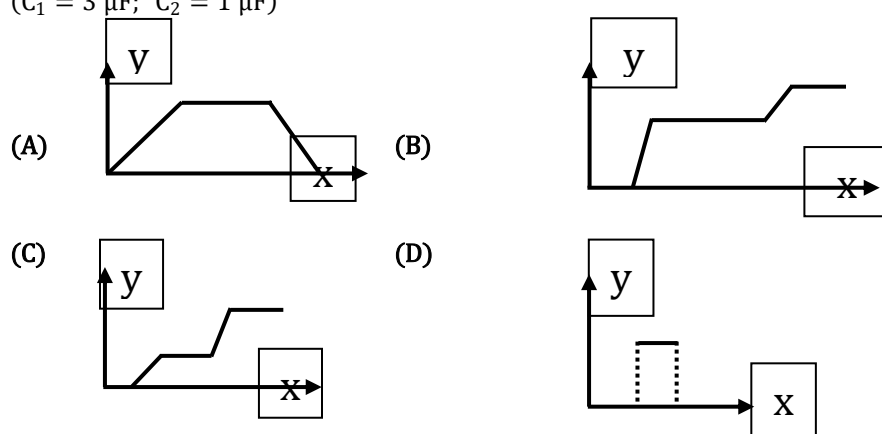
**Q.14** Figure shows two capacitors connected with a battery in a circuit. On moving from left to right on the branch containing the capacitors, the correct graph representing potential ( $V$ ) vs distance ( $x$ ) will be:  
( $C_1 = 3 \mu\text{F}$ ;  $C_2 = 1 \mu\text{F}$ )



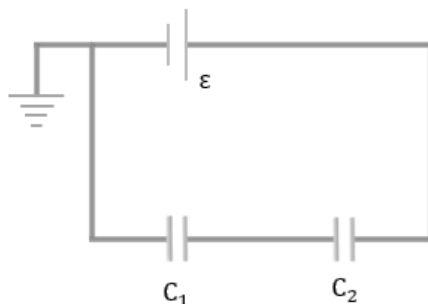


### Parallel and Series Combination of Capacitors

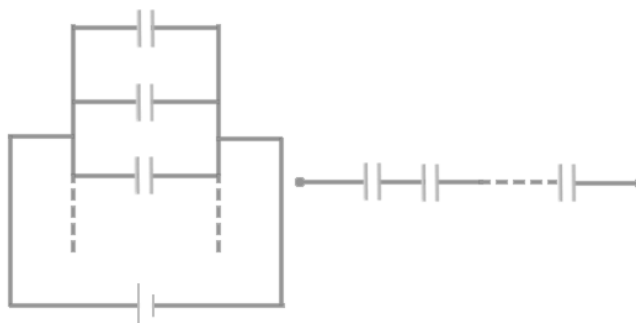- Q.15** There are  $n$  identical capacitors which are connected in parallel to a potential difference  $V$ . these capacitors are then reconnected in series. The potential difference between the extreme ends is  
 (A) 0 (B)  $nV$  (C)  $(n - 1)V$  (D)  $(n - 2)V$



### Parallel and Series Combination of Capacitors

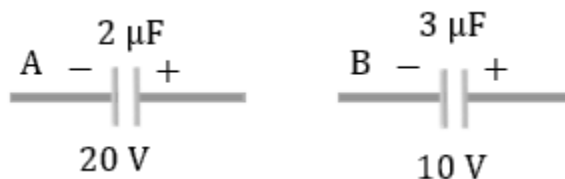
- Q.16** Two parallel plate capacitors A and B having capacitances  $2 \mu\text{F}$  and  $3 \mu\text{F}$  are charged separately up to  $20 \text{ V}$  and  $10 \text{ V}$  respectively. Now, the positive plate of A is connected to the positive plate of B and negative plate of A is connected with negative plate of B. Find how much charge flows in the circuit ?  
 (A)  $28 \mu\text{C}$  (B)  $42 \mu\text{C}$  (C)  $12 \mu\text{C}$  (D)  $12 \mu\text{C}$




### Parallel and Series Combination of Capacitors

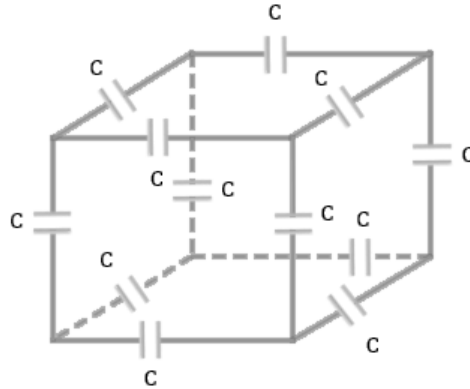- Q.17** Twelve capacitors each having a capacitance  $C$ , are connected to form a cube. Find the equivalent capacitance of the cube along its body diagonal? [Take  $C = 15 \mu\text{F}$ ]  
 (A)  $18 \mu\text{F}$  (B)  $12 \mu\text{F}$  (C)  $\frac{6}{5} \mu\text{F}$  (D)  $\frac{5}{6} \mu\text{F}$




**Energy of a Capacitor**

**Q.18** Three capacitors  $C_1$ ,  $C_2$  and  $C_3$  of capacitance  $4\ \mu\text{F}$ ,  $3\ \mu\text{F}$  and  $6\ \mu\text{F}$  are charged up to a potential difference of  $5\text{ V}$ ,  $6\text{ V}$  and  $4\text{ V}$  respectively. If terminal  $a$  is connected with  $f$ , terminal  $e$  is connected with  $d$  and  $b$  is connected with  $c$ , then find the amount of heat produced in the circuit?

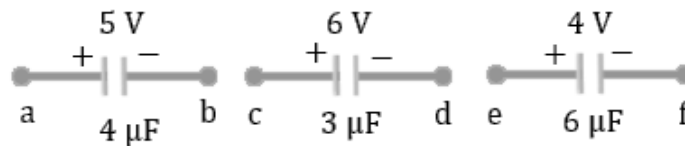
(A)  $20\ \mu\text{J}$ (B)  $2\ \mu\text{J}$ (C)  $152\ \mu\text{J}$ (D)  $150\ \mu\text{J}$ **Energy of a Capacitor**

**Q.19** If  $\text{att} = 0$ , switch  $S$  is closed, at steady state find heat generated ( $H$ ) in the given circuit having a battery of  $16\text{ volts}$ .

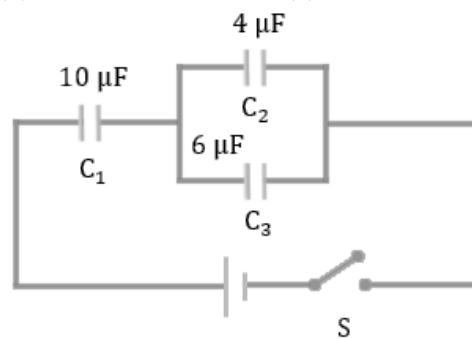(A)  $1280\ \mu\text{J}$ (B)  $640\ \mu\text{J}$ (C)  $320\ \mu\text{J}$ (D)  $192\ \mu\text{J}$ **Energy of a Capacitor**

**Q.20** Initially, the switch  $S$  is open in the circuit for a long time. After the switch is closed, the heat generated in the circuit will be:

(A)  $600\ \mu\text{J}$ (B)  $750\ \mu\text{J}$ (C)  $350\ \mu\text{J}$ (D)  $450\ \mu\text{J}$

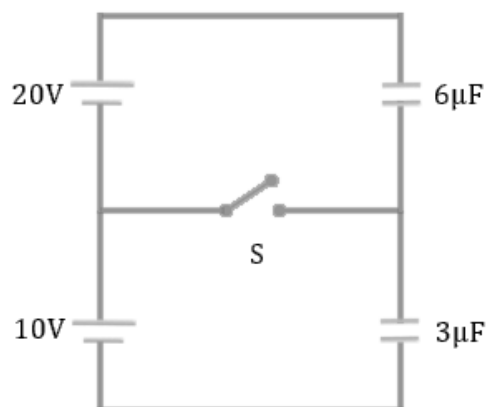**ANSWER KEY**

Q.	1	2	3	4	5	6	7	8	9	10
Sol.	(B)	(C)	(D)	(A)	(D)	(B)	(D)	(C)	(B)	(B)
WORK SHEET										
Q.	1	2	3	4	5	6	7	8	9	10
Sol.	(C)	(B)	(C)	(D)	(B)	(A)	(B)	(D)	(A)	(A)
Q.	11	12	13	14	15	16	17	18	19	20
Sol.	(A)	(A)	(B)	(C)	(B)	(C)	(A)	(D)	(B)	(D)