
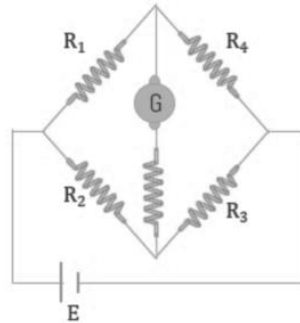


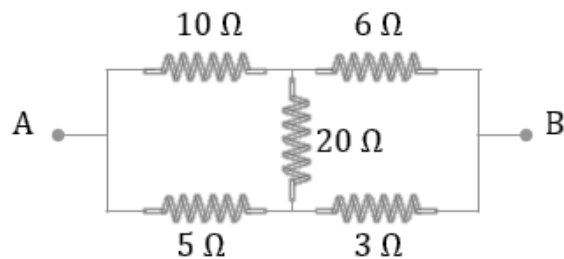- Q.1** In a balanced Wheatstone bridge, current in the galvanometer is zero. It remains zero when
- (1) The emf is increased
 - (2) All resistance are increased by $10\ \Omega$
 - (3) All resistance are made five times
 - (4) The battery and the galvanometer are interchanged
- (A) Only (1) is correct
 (B) (1), (2) and (3) are correct
 (C) (1), (3) and (4) are correct
 (D) (1) and (3) are correct




- Q.2** Find equivalent resistance of the circuit between the terminal A and B

(A) $\frac{4}{3}\ \Omega$ (B) $\frac{8}{3}\ \Omega$ (C) $\frac{16}{3}\ \Omega$ (D) $\frac{32}{3}\ \Omega$




- Q.3** Find equivalent resistance of the circuit

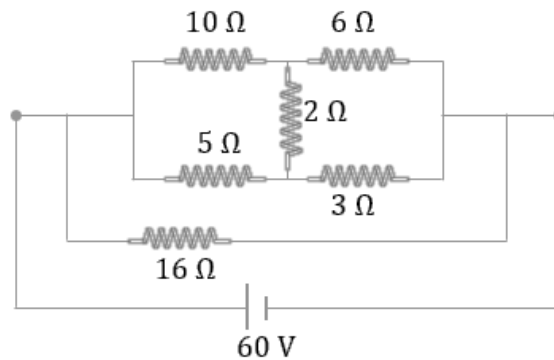(A) $1\ \Omega$ (B) $4\ \Omega$ (C) $2\ \Omega$ (D) $8\ \Omega$




- Q.4** For the network shown in the figure, the value of the current i is

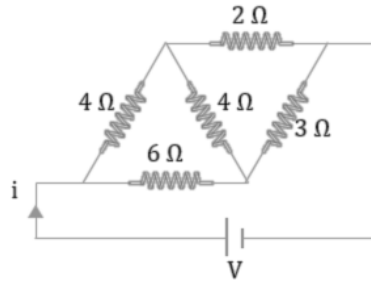(A) $\frac{9V}{35}$ (B) $\frac{5V}{18}$ (C) $\frac{5V}{9}$ (D) $\frac{5V}{9}$




Q.5 What resistor should be connected in parallel with the $20\ \Omega$ resistor in branch ADC in the circuit shown in figure, so that potential difference between B and D may be zero?

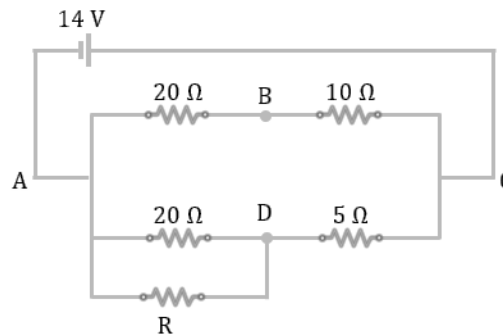- (A) $20\ \Omega$ (B) $10\ \Omega$ (C) $5\ \Omega$ (D) $15\ \Omega$




Q.6 In a circuit, three resistance P, Q and R are connected in the three arms and the fourth arm is formed by two resistance S_1 and S_2 connected in parallel. The condition for which the circuit will become a balanced Wheatstone bridge is

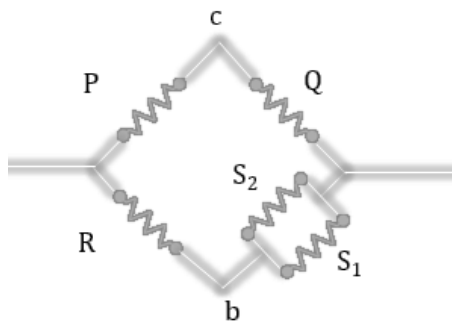- (A) $\frac{P}{Q} = \frac{R(S_1+S_2)}{2S_1S_2}$ (B) $\frac{P}{Q} = \frac{R}{S_1+S_2}$ (C) $\frac{P}{Q} = \frac{2R}{S_1+S_2}$ (D) $\frac{P}{Q} = \frac{R(S_1+S_2)}{S_1S_2}$



Q.7 The equivalent resistance between A and B will be :

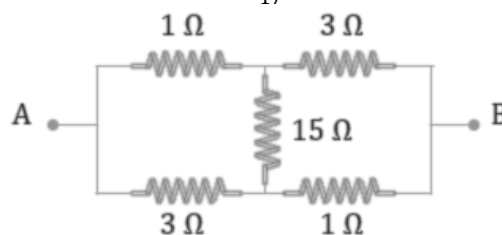- (A) $\frac{25}{7}\ \Omega$ (B) $\frac{33}{7}\ \Omega$ (C) $\frac{25}{17}\ \Omega$ (D) $4\ \Omega$




- Q.8** The wire has linear resistance p ($\text{in } \Omega/\text{m}$). The resistance between points A and B if the side of the big square is d .

(A) $\frac{pd}{\sqrt{2}}$

(B) $\sqrt{2}pd$

(C) $2pd$

(D) $3pd$

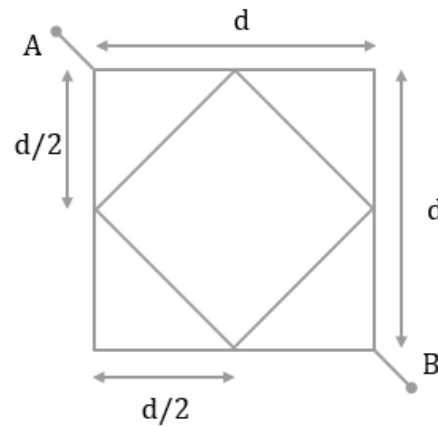


- Q.9** Find the equivalent resistance between A and B.

(A) $2R$

(B) $3R$

(C) R

(D) $\frac{R}{2}$

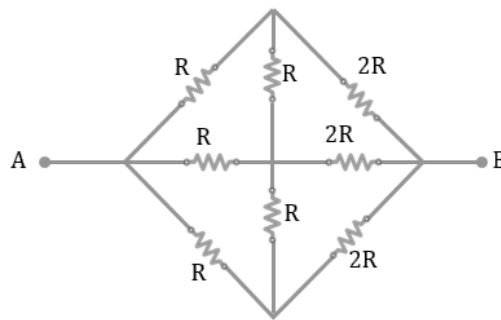


- Q.10** The effective resistance between points P and Q of the electrical circuit shown in the figure is:

(A) $\frac{2Rr}{R+r}$

(B) $2r + 4R$

(C) $\frac{8R(R+r)}{3R+r}$

(D) $\frac{5}{2}R + 2r$

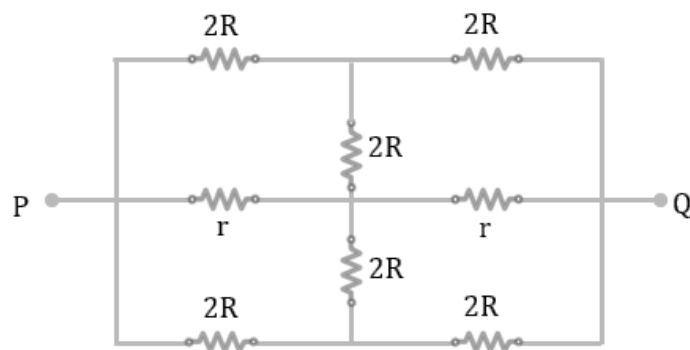

ANSWER KEY

Q.	1	2	3	4	5	6	7	8	9	10
Sol.	(C)	(C)	(B)	(B)	(A)	(D)	(B)	(A)	(C)	(A)