**Q.1** In the circuit shown below, the current in the **1**  $\Omega$  resistor is



**Q.2** To get maximum current through a resistance of  $2.5 \Omega$ , one can use **m** rows of cells, each row having **n** cells. The internal resistance of each cell is  $0.5 \Omega$ . What are the values of **n** and **m** if the total number of cells is **45**?

**Q.3** A circuit whose resistance **R** is connected to **n** similar cells. If the current in the circuit is the same whether the cells are connected in series or parallel, then the internal resistance **r** of each cell is given by



**Q.4** Three equal resistors connected in series across a source of emf together dissipate **10 W** of power. What would be the power dissipated if the same resistors are connected in parallel across the same source of emf?



Q.5Resistors P, Q and R in the circuit have equal resistances. If the battery is supplying a total power of<br/>12 W, what is the power dissipated as heat in resistor R ?<br/>(A) 2 W(B) 6 W(C) 3 W(D) 8 W



**Q.6** A battery of internal resistance  $4 \Omega$  is connected to the network of resistance as shown in figure. In order that the maximum power can be delivered to the network, the value of **R** (in  $\Omega$ ) should be



Q.7 If the length of the filament of a heater is reduced by10%, the power of the heater will (A)Increase by about 9% (B)increase by about 11%
(C)Increase by about 19% (D)decrease by about 10%



**Q.8** Power generated across uniform wire connected across a supply is **H**. If the wire is cut into **n** equal parts and all the parts are connected in parallel across the same supply, the total power generated in the wire is



**Q.9** Two identical batteries, each of emf2 V and internal resistance  $\mathbf{r} = 1 \ \Omega$  are connected as shown. The maximum power that can be developed across R using these batteries is



**Q.10** For the given power output, there exists two values of external resistance, the product of these resistances will be equal to



### WORKSHEET

## Time of Flight with Incline as Frame of Reference

Q.1 Two inclined planes **OA** and **OB** having inclination (with horizontal) **30**° and**60**°, respectively, intersect each other at **O** as shown in figure. A particle is projected from point **P** with velocity  $\mathbf{u} = \mathbf{10}(\sqrt{3}) \, \mathbf{ms^{-1}}$  along a direction perpendicular to the plane**OA**. If the particle strikes the plane **OB** perpendicular at**Q**, calculate the displacement **PQ** 



### Projectile Time, Height and Range

**Q.2** A particle is projected from point **G** such that it touches the points **B**, **C**, **D** and **E** of a regular hexagon of side**a**. Its horizontal range **GH** is



#### Latent Heat

**Q.3** An ice cube of mass  $M_0$  is given a velocity  $v_0$  on a rough horizontal surface with coefficient of friction $\mu$ . The block is at its melting point and latent heat of fusion of ice is **L**. The block receives heat only due to the friction forces and all work is converted into heat. Find the mass  $(M_t)$  of the remaining ice block after timet.

#### Newtons Second Law

**Q.4** In the figure shown a cart moves on a smooth horizontal surface due to an external constant force of magnitude**F**. The initial mass of the cart is  $M_0$  and velocity is zero. Sand falls on to the cart with negligible velocity at constant rate  $\mu$  kg/s and sticks to the cart. The velocity of the cart at time t is:

$$(\mathbf{A})_{\overline{M_0 + \mu t}}^{\overline{Ft}} \qquad \qquad (\mathbf{B})_{\overline{M_0}}^{\overline{Ft}} e^{\mu t} \qquad \qquad (\mathbf{C})_{\overline{M_0}}^{\overline{Ft}} \qquad \qquad (\mathbf{D})_{\overline{M_0 + \mu t}}^{\overline{Ft}} e^{\mu t}$$



## **Bernoulli's Principle**

**Q.5** An open large tank with a nozzle attached contains three immiscible, inviscid fluids as shown. Assuming that the changes in  $h_1$ ,  $h_2$  and  $h_3$  are negligible, the instantaneous discharge velocity is



# Potential Energy of a System of Multiple Point Charges

**Q.6** Four charges  $q_1 = 1 \mu C$ ,  $q_2 = 2 \mu C$ ,  $q_3 = -3 \mu C$  and  $q_4 = 4 \mu C$  are kept on the vertices of a square of side 1 m. Find the electric potential energy of this system of charges



#### **Conservation of Energy in Case of Electrostatics**

**Q.7** Figure shows a charge +**Q** clamped at a point in free space. From a large distance another charge particle of charge -**q** and mass of **m** is thrown towards +**Q** with an impact parameter **d** as shown with speed**v**. How many positions for minimum separation would be obtained for the particle?



# Linear Charge Distribution

**Q.7** If the linear charge density of a rod of length **3 m** varies  $as\lambda = (2 + x) C/m$ , where x is the distance from one end of the rod, then find the total charge on the rod



### **EMF and EMF Devices**

Q.8 A battery has emf 4 V and internal resistancer. When this battery is connected to an external resistance of 2 Ω, a current of 1 A flows in the circuit. How much current will flow if the terminals of the battery are connected directly?
 (A) 1 A
 (B) 2 A
 (C) 4 A
 (D) Infinite

#### Series Combination of Cells

**Q.9 n** identical cells, each of e.m.f **ε** and internal resistance **r** are joined in series to form a closed circuit. The potential difference across any one cell is

(A)Zero (B) $\varepsilon$  (C) $\frac{\varepsilon}{n}$  (D) $\frac{n-1}{n}\varepsilon$ 

## Kirchhoff's Voltage Law

**Q.10** In order to determine the emf of a storage battery, it was connected in series with a standard cell in a certain circuit and a current  $I_1$  was obtained. When the battery is connected to the same circuit opposite to the standard cell a current  $I_2$  flows in the external circuit from the positive plate of the storage battery. What is the emf  $E_1$  of the storage battery, if the emf of the standard cell is  $E_2$ ?

(A)
$$E_1 = \frac{I_1 + I_2}{I_1 - I_2} E_2$$
 (B) $E_1 = \frac{I_1 + I_2}{I_2 - I_1} E_2$  (C) $E_1 = \frac{I_1 - I_2}{I_1 + I_2} E_2$  (D) $E_1 = \frac{I_2 - I_1}{I_1 + I_2} E_2$ 

#### Kirchhoff's Voltage Law

**Q.11** Two batteries of emf **4 V** and **8 V** with internal resistances **1**  $\Omega$  and **2**  $\Omega$  are connected in a circuit with a resistance of **9**  $\Omega$  as shown in figure. The current and potential difference between the points **P** and **Q** are

$$(\mathbf{A})\frac{1}{3}\mathbf{A} \text{ And } 3 \text{ V} \qquad (\mathbf{B})\frac{1}{6}\mathbf{A} \text{ and } 4 \text{ V} \qquad (\mathbf{C})\frac{1}{9} \text{ A and } 9 \text{ V} \qquad (\mathbf{D})\frac{1}{2}\mathbf{A} \text{ and } 12 \text{ V}$$

$$P \xrightarrow{1 \Omega}_{r_1} 4 \text{ V} 8 \text{ V} \xrightarrow{r_2}_{r_2} Q$$

$$9 \Omega$$

## Mixed Combination of Cells

**Q.12 N** identical cells are connected to form a battery. When the terminals of the battery are joined directly (short-circuited), current **I** flows in the circuit. To obtain the maximum value of **I** 

(A)All the cells should be joined in series

(B)All the cells should be joined in parallel

(C)Two rows of *N*/*S* cells each should be joined in parallel

**(D)** $\sqrt{N}$  Rows of  $\sqrt{N}$  cells each should be joined in parallel

## **Mixed Combination of Cells**

Q.13 N identical cells are connected to form a battery. When the terminals of the battery are joined directly (short-circuited), current I flows in the circuit. To obtain the maximum value of I

(A)All the cells should be joined in series

(B)All the cells should be joined in parallel

(C)Two rows of N/S cells each should be joined in parallel

**(D)** $\sqrt{N}$  Rows of  $\sqrt{N}$  cells each should be joined in parallel

# **Power in Electric Circuits**

**Q.14** Power generated across uniform wire connected across a supply is**H**. If the wire is cut into **n** equal parts and all the parts are connected in parallel across the same supply, the total power generated in the wire is

| $(\mathbf{A})_{n^2}^{\mathrm{H}}$ | <b>(B)</b> n <sup>2</sup> H | <b>(C)</b> nH | $(\mathbf{D})_{n}^{\mathrm{H}}$ |
|-----------------------------------|-----------------------------|---------------|---------------------------------|
| II-                               |                             |               | 11                              |

# **Power in Electric Circuits**

| Q.15 | If the length of the filament of a heater is reduced by <b>10%</b> , the power of the heater wil |                                  |  |  |  |  |  |
|------|--|----------------------------------|--|--|--|--|--|
|      | <b>(A)</b> Increase by about 9%  | <b>(B)</b> Increase by about 11% |  |  |  |  |  |
|      | <b>(C)</b> Increase by about 19%   | <b>(D)</b> Decrease by about 10% |  |  |  |  |  |

## **Centripetal Acceleration**

**Q.16** An electric kettle has two heating filaments. One brings it to boil in **10 min** and the other in **15 min** when they are connected across the same potential difference. If the two heating filaments are connected in parallel, then water in kettle will boil in

| <b>(A)</b> 6 min | <b>(B)</b> 8 min | <b>(C)</b> 25 min | <b>(D)</b> 5 min |
|------------------|------------------|-------------------|------------------|
|------------------|------------------|-------------------|------------------|

## Power Delivered and Heat Dissipated in a Circuit

**Q.17** A 100 W bulb is designed to operate at a potential difference of 230 V. Find the current drawn by the bulb if it is operated at a potential difference for which it is designed.



## **Electric Bulbs**

**Q.18** The above configuration shows three identical bulbs, grade them in order of their brightness  $(\mathbf{A})B_3 > B_2 = B_1(\mathbf{B})B_1 = B_2 > B_3(\mathbf{C})B_3 > B_1 > B_2(\mathbf{D})B_2 > B_1 > B_3$ 



## **Electric Bulbs**

**Q.19** Bulb **1** and Bulb **2** are rated (**30 W** – **200 V**) and (**60 W** – **200 V**) respectively. They are connected with a **400 V** power supply. Find which bulb will get fused if they are connected in parallel

(A)Bulb 1 will get fused

(C)Both will get fused

(B)Bulb 2 will get fused(D)No bulb will get fused



# Electric Bulbs

Q.20A factory is served by a 220 V supply line. In a circuit protected by a fuse marked 10 A, the maximum<br/>number of 100 W lamps in parallel that can be turned on is<br/>(A)11(B)22(C)33(D)66

# **ANSWER KEY**

| Q.   | 1   | 2   | 3   | 4   | 5   | 6   | 7   | 8   | 9   | 10  |
|------|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|
| Sol. | (C) | (A) | (C) | (C) | (A) | (B) | (B) | (B) | (C) | (A) |

| WORK SHEET |     |     |     |     |     |     |     |     |     |     |
|------------|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|
| Q.         | 1   | 2   | 3   | 4   | 5   | 6   | 7   | 8   | 9   | 10  |
| Sol.       | (A) | (C) | (B) | (B) | (A) | (B) | (A) | (C) | (B) | (A) |
| Q.         | 11  | 12  | 13  | 14  | 15  | 16  | 17  | 18  | 19  | 20  |
| Sol.       | (A) | (A) | (B) | (B) | (B) | (A) | (D) | (A) | (C) | (B) |