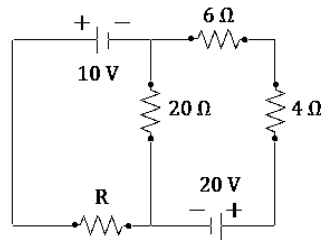


- Q.1** In the circuit shown in figure, for what value of  $R$  will the power consumed by this resistance will be maximum

(A)  $40\ \Omega$  (B)  $\frac{20}{3}\ \Omega$  (C)  $\frac{10}{7}\ \Omega$  (D)  $30\ \Omega$




- Q.2** A cell of internal resistance  $r$  is connected to a load of resistance  $R$ . Energy is dissipated in the load, but some thermal energy is also wasted in the cell. The efficiency of such arrangement is found from the expression  $\frac{\text{Energy dissipated in the load}}{\text{Energy dissipated in the complete circuit}}$ . which of the following gives the efficiency in this case?

(A)  $\frac{r}{R}$  (B)  $\frac{R}{r}$  (C)  $\frac{r}{R+r}$  (D)  $\frac{R}{R+r}$


- Q.3** For a given power output, there exists two values of external resistance, the product of these resistances will be equal to

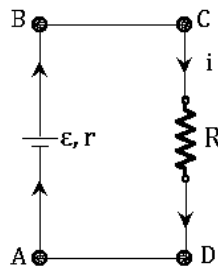(A)  $r^2$  (B)  $\frac{r^2}{4}$  (C)  $2r^2$  (D)  $\frac{r^2}{3}$




- Q.4** Two identical batteries, each of emf  $2\text{ V}$  and internal resistance  $r = 1\ \Omega$  are connected as shown. The maximum power that can be developed across  $R$  using these batteries is

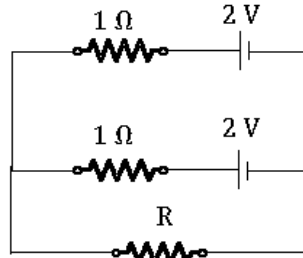(A)  $3.2\text{ W}$  (B)  $8.2\text{ W}$  (C)  $2\text{ W}$  (D)  $4\text{ W}$




- Q.5** A battery of internal resistance  $4\ \Omega$  is connected to the network of resistance as shown in figure. In order that the maximum power can be delivered to the network, the value of  $R$  (in  $\Omega$ ) should be

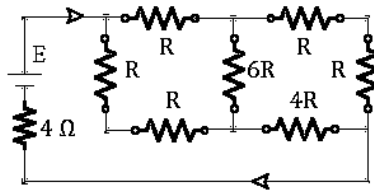
(A)  $\frac{4}{9}$  (B)  $2$  (C)  $\frac{8}{3}$  (D)  $18$



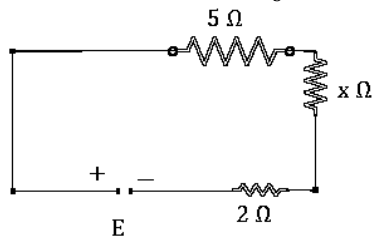
- Q.6 In the given circuit the power generated in  $5\ \Omega$  resistance will be maximum for  $x$  equal to  
 (A)  $1\ \Omega$  (B)  $7\ \Omega$  (C)  $\frac{2}{3}\ \Omega$  (D)  $0\ \Omega$



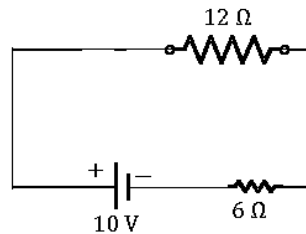
- Q.7 Find the efficiency of the below given battery having internal resistance  $6\ \Omega$ .  
 (A) 75 % (B) 37.5 % (C) 50 % (D) 67 %



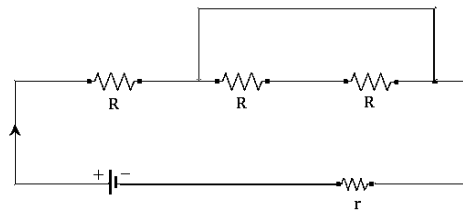- Q.8 Find the value of  $r$  in terms of  $R$ , so that power in external circuit is maximum.  
 (A)  $r = 3R$  (B)  $r = 3R$  (C)  $r = \frac{R}{3}$  (D)  $r = \frac{R}{2}$



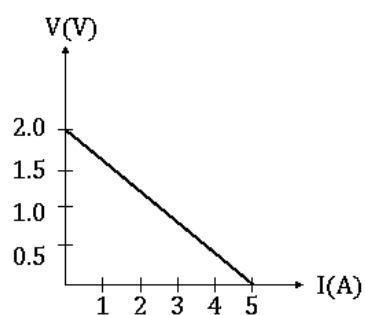- Q.9 A battery of emf  $E$  and internal resistance  $r$  is connected across a resistance  $R$ . Resistance  $R$  can be adjusted to any value greater than or equal to zero. A graph is plotted between the current passing through the resistance ( $I$ ) and potential difference across the terminals of the battery ( $V$ ). Maximum power developed across the resistance  $R$  is  
 (A) 5 W (B) 15 W (C) 25 W (D) 10 W




**Q.10** In the given circuit diagram, battery has internal resistance of  $6\ \Omega$ . For what value of  $r$ , external circuit will consume maximum power?

(A)  $5\ \Omega$

(B)  $6\ \Omega$

(C)  $9\ \Omega$

(D)  $3\ \Omega$

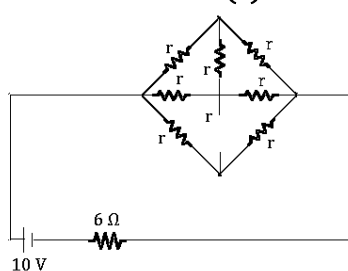

## WORKSHEET

## Principle of Superposition


**Q.1** Two equally charged identical metallic spheres **A** and **B** repel each other with a force  $2 \times 10^{-5} \text{ N}$ , when placed in air (neglect the dimension of sphere as they are very small). Another identical uncharged sphere **C** is touched to **B** and then placed at the midpoint of line joining **A** and **B**. What is the net electrostatic force on **C**?

(A)  $1 \times 10^{-5} \text{ N}$ , toward BA

(B)  $2 \times 10^{-5} \text{ N}$ , towards AB

(C)  $4 \times 10^{-5} \text{ N}$ , towards BA

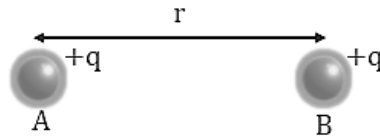(D)  $0.5 \times 10^{-5} \text{ N}$ , towards AB



## Electric Field Due to a Line of Charge Not on Its Axis


**Q.2** Which of the following graph shows the curve between electric field (**E**) versus distance (**r**) from infinite line charge having constant positive charge density

(A) 



(C) 

(D) 

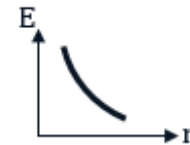

## Electric Potential Due to Shell


**Q.3** Two concentric spheres of radii **R** and **2R** are charged. The inner sphere has a charge of  $1 \mu\text{C}$  and the outer sphere has a charge of  $2 \mu\text{C}$  of the same sign. The potential is  $9000 \text{ V}$  at a distance  $3R$  from the common center. The value of **R** is

(A) 1 m

(B) 2 m

(C) 3 m

(D) 4 m

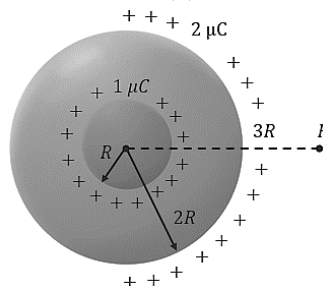

## Mirror Formula


**Q.4** Find the position of the final image of the object **O** after three successive reflections taking the first reflection on **m<sub>1</sub>**

(A) 12.5 cm in front of the mirror **m<sub>1</sub>**

(B) 10 cm In front of the mirror **m<sub>1</sub>**

(C) 12.5 cm In front of the mirror **m<sub>2</sub>**

(D) 10 cm In front of the mirror **m<sub>2</sub>**

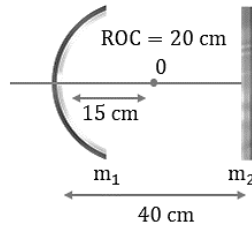**COM in Oblique Collision**


- Q.5** The point B lies on a smooth plane inclined at  $30^\circ$  to the horizontal. A particle of mass  $\frac{1}{7}$  kg is dropped from a point A which lies **10 m** vertically above B. The particle rebounds from the plane in the direction **BC** with speed **v m/s** at an angle of  $45^\circ$  to the plane. Find the impulse exerted by the plane on the particle (inNs)

(A)  $1 + \sqrt{3}$

(B)  $1 - \sqrt{3}$

(C)  $2 + \sqrt{3}$

(D)  $2 - 2\sqrt{3}$

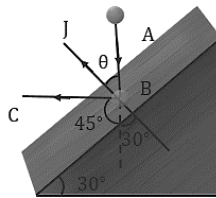**Speed of Efflux**


- Q.6** A water tank stands on the roof of a building as shown in the figure. The value of height of water above the hole (**h**) for which the horizontal distance covered by the water (**x**) is maximum

(A) 0.5 m

(B) 0.8 m

(C) 1 m

(D) 0.2 m

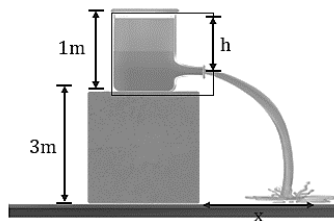**Heat Engines**

- Q.7** For which combination of temperatures the efficiency of Carnot's engine is highest?

(A) 80 K, 60 K

(B) 100 K, 80 K

(C) 60 K, 40 K

(D) 40 K, 20 K

**Moment of Inertia of Solid Bodies**


- Q.8** Two particles having masses **3 kg** and **6 kg** are situated in a plane perpendicular to line **AB** at a perpendicular distance of **2 m** and **4 m** respectively as shown in figure. Find the moment of inertia about an axis **A'B'** parallel to **AB**

(A)  $216 \text{ kg} - \text{m}^2$

(B)  $108 \text{ kg} - \text{m}^2$

(C)  $300 \text{ kg} - \text{m}^2$


(D)  $200 \text{ kg} - \text{m}^2$

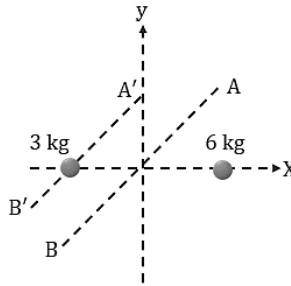**Relative Motion: Rain Example**


**Q.9** Rain is falling vertically with a velocity of  $15 \text{ ms}^{-1}$ . A person rides a bicycle with a speed of  $15 \text{ ms}^{-1}$  in the west to east direction. What is the direction (angle with vertical) in which he should hold his umbrella to save himself from the rain?

(A)  $45^\circ$ (B)  $90^\circ$ (C)  $30^\circ$ (D)  $15^\circ$ **Longitudinal Strain**

**Q.10** A steel wire of length  $1 \text{ m}$  and cross sectional area  $A$  is stretched by  $1 \text{ cm}$  under a given load. When the same load is applied to another steel wire of double length and half the cross-sectional area of the first one, the amount of stretching (extension) is

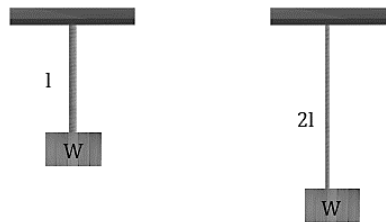(A)  $0.5 \text{ m}$ (B)  $2 \text{ m}$ (C)  $4 \text{ m}$ (D)  $1.5 \text{ m}$ **Electric Bulbs**

**Q.11** Three light bulbs ( $60 \text{ W}$ ,  $120 \text{ V}$ ) are connected across a  $120 \text{ V}$  power source. If the resistance of each bulb does not change with current, then find out total power delivered to the three bulbs

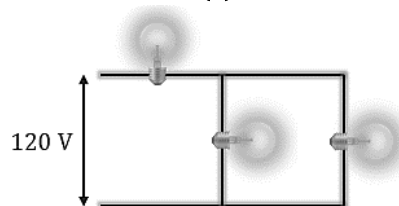
(A)  $80 \text{ W}$ (B)  $60 \text{ W}$ (C)  $40 \text{ W}$ (D)  $20 \text{ W}$ 

**Electric Bulbs**


- Q.12** When electric bulbs of same power, but different marked voltage are connected in series across the power line, their brightness will be
- (A) Proportional to their marked voltage
  - (B) Inversely proportional to their marked voltage
  - (C) Proportional to the square of their marked voltage
  - (D) Inversely proportional to the square of their marked voltage

**Power in Electric Circuits**


- Q.13**  $n$  identical light bulbs, each designed to draw  $P$  power from a certain voltage supply, are joined in series across that supply. The total power which they will draw is
- (A)  $nP$
  - (B)  $P$
  - (C)  $P/n$
  - (D)  $P/n^2$

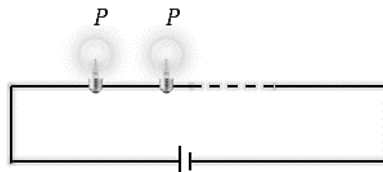**Power in Electric Circuits**

- Q.14** Two electric bulbs **A** and **B** are rated **60 W** and **100 W** respectively. If they are connected in parallel to the same source, then (assume the bulb **A** and **B** have the same voltage rating.)
- (A) Both the bulbs draw the same current
  - (B) Bulb A draws more current than bulb B
  - (C) Bulb B draws more current than bulb A
  - (D) Current drawn in the bulbs are in the ratio of their resistances

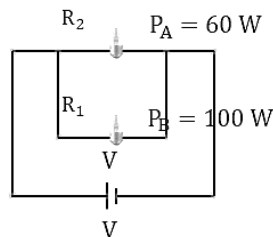
**Electric Bulbs**

- Q.15** Three similar light bulbs are connected to a constant voltage D.C. supply as shown in the figure. Each bulb operates at normal brightness and the ammeter (of negligible resistance) registers a steady current.
- The filament of one of the bulbs breaks. What happens to the ammeter reading and to the brightness of the remaining bulbs?
- (A) Both ammeter reading and bulb brightness increases
  - (B) Ammeter reading increases and bulb brightness remains unchanged
  - (C) Both ammeter reading and bulb brightness remains unchanged
  - (D) Ammeter reading decreases and bulb brightness remains unchanged

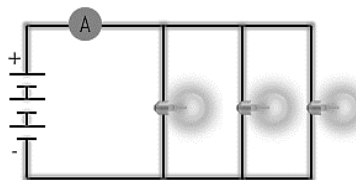**Power in Electric Circuits**


**Q.16** Three identical bulbs are connected in series and these together dissipate a power  $P$ . If now these bulbs are connected in parallel, then the power dissipated will be

- (A)  $\frac{P}{3}$  (B)  $3P$  (C)  $9P$  (D)  $\frac{P}{9}$

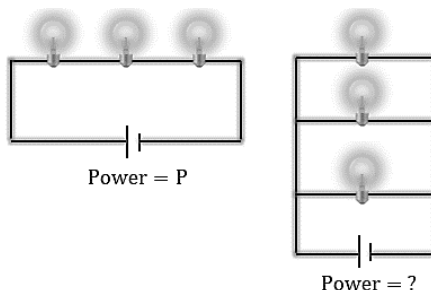**Power in Electric Circuits**


**Q.17** A cell of constant emf is first connected to a resistance  $R_1$  and then connected to a resistance  $R_2$ . If power delivered in both cases is same, then the internal resistance of the cell is

- (A)  $\sqrt{R_1 R_2}$  (B)  $\sqrt{\frac{R_1}{R_2}}$  (C)  $\frac{R_1 - R_2}{2}$  (D)  $\frac{R_1 + R_2}{2}$

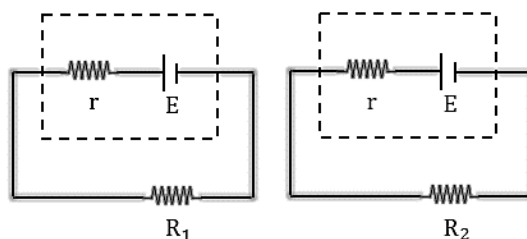**Power Delivered and Heat Dissipated in a Circuit**

**Q.18** A battery of internal resistance  $4\ \Omega$  is connected to the network of resistances as shown. What must be the value of  $R$  so that maximum power is delivered to the network?

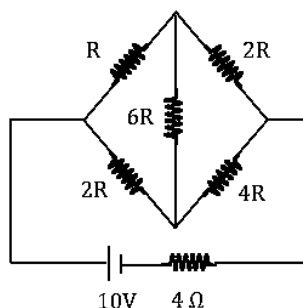- (A)  $4\ \Omega$  (B)  $2\ \Omega$  (C)  $1\ \Omega$  (D)  $0.5\ \Omega$





**Power in Electric Circuits**


- Q.19** Three identical cells, each having an e.m.f. of  $1.5\text{ V}$  and a constant internal resistance of  $2.0\ \Omega$ , are connected in series with a  $4.0\ \Omega$  resistor  $R$ , first as in circuit (i) and secondly as in circuit (ii). What is the ratio of  $\frac{\text{Power across } R \text{ in circuit (i)}}{\text{Power across } R \text{ in circuit (ii)}}$  ?

(A) 9.0


(B) 7.2

(C) 1.8

(D) 3.0

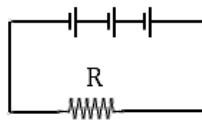


Circuit (i)

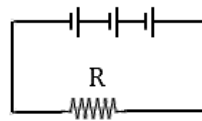

Circuit (ii)

**Power Delivered and Heat Dissipated in a Circuit**

- Q.20** A battery having emf  $10\text{ V}$  and internal resistance  $2\ \Omega$  is connected to an external circuit as shown in the diagram. Find the value of  $R$  for which maximum power will be transferred to the external circuit. Also find the efficiency of the battery.

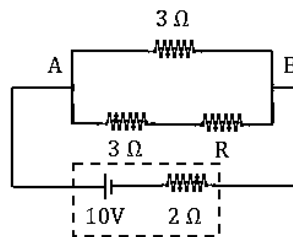(A)  $2\ \Omega$ , 50(B)  $4\ \Omega$ , 50(C)  $2\ \Omega$ , 67(D)  $4\ \Omega$ , 67

**ANSWER KEY**

<b>Q.</b>	<b>1</b>	<b>2</b>	<b>3</b>	<b>4</b>	<b>5</b>	<b>6</b>	<b>7</b>	<b>8</b>	<b>9</b>	<b>10</b>
<b>Sol.</b>	(B)	(D)	(A)	(C)	(B)	(D)	(D)	(C)	(A)	(C)
<b>WORK SHEET</b>										
<b>Q.</b>	<b>1</b>	<b>2</b>	<b>3</b>	<b>4</b>	<b>5</b>	<b>6</b>	<b>7</b>	<b>8</b>	<b>9</b>	<b>10</b>
<b>Sol.</b>	(B)	(D)	(A)	(A)	(A)	(C)	(D)	(A)	(A)	(C)
<b>Q.</b>	<b>11</b>	<b>12</b>	<b>13</b>	<b>14</b>	<b>15</b>	<b>16</b>	<b>17</b>	<b>18</b>	<b>19</b>	<b>20</b>
<b>Sol.</b>	(C)	(C)	(C)	(C)	(D)	(C)	(A)	(B)	(A)	(A)