
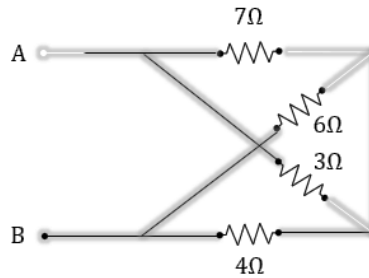


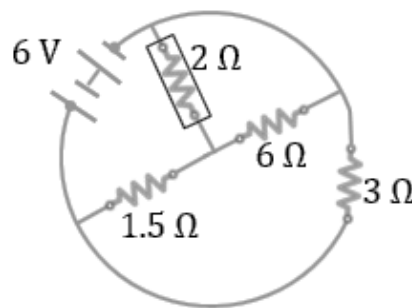
- Q.1** The equivalent resistance between A and B (of the circuit as shown in figure) is
 (A) $4.5\ \Omega$ (B) $12\ \Omega$ (C) $5.4\ \Omega$ (D) $20\ \Omega$




- Q.2** The total current supplied to the circuit by the battery is
 (A) 1 A (B) 2 A (C) 4 A (D) 6 A



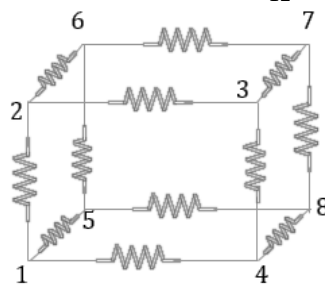- Q.3** Twelve resistors each of resistance r are connected together so that each lies along the edge of the cube as shown in the figure. The equivalent resistance between points 1 and 4 is
 (A) $\frac{5r}{12}$ (B) $\frac{7r}{12}$ (C) $\frac{11r}{12}$ (D) $\frac{13r}{12}$




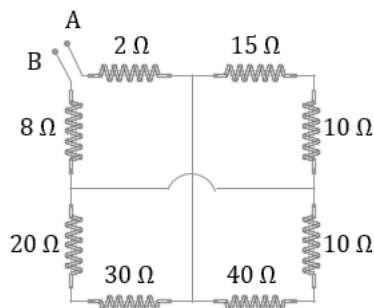- Q.4** The equivalent resistance between point's A and B is
 (A) $\frac{65}{2}\ \Omega$ (B) $\frac{45}{2}\ \Omega$ (C) $45\ \Omega$ (D) $135\ \Omega$




Q.5 Find the equivalent resistance between X and Y.

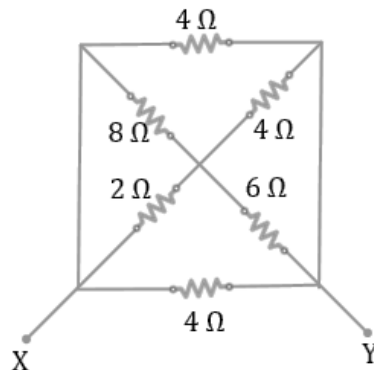- (A) $1\ \Omega$ (B) $4\ \Omega$ (C) $\frac{4}{3}\ \Omega$ (D) $\frac{2}{3}\ \Omega$




Q.6 Find the equivalent resistance between A and B.

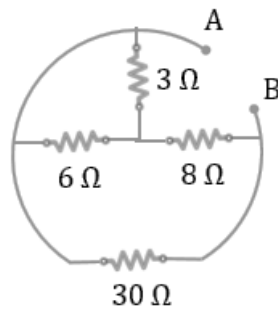- (A) $\frac{15}{2}\ \Omega$ (B) $15\ \Omega$ (C) $\frac{7}{2}\ \Omega$ (D) $7\ \Omega$




Q.7 Find the equivalent resistance between A and B.

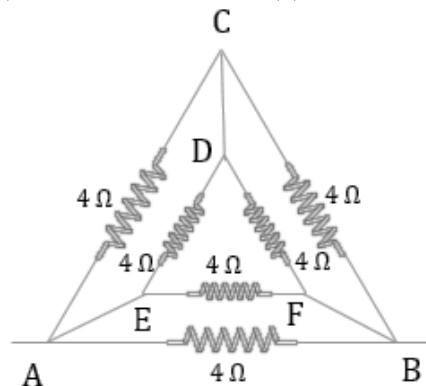- (A) $2\ \Omega$ (B) $3\ \Omega$ (C) $4\ \Omega$ (D) $8\ \Omega$




Q.8 For the circuit shown in the figure, choose the correct options

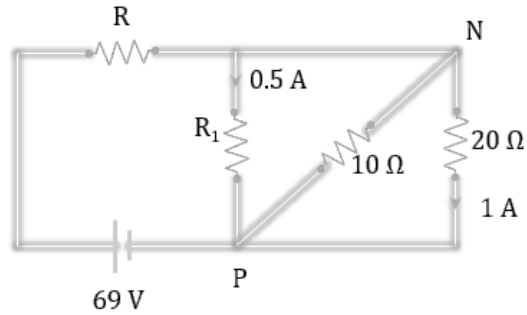- (A) The current through $10\ \Omega$ resistor connected across NP is $0.5\ \text{A}$
 (B) The value of $R_1 = 50\ \Omega$
 (C) The value of $R = 14\ \Omega$
 (D) The potential difference across resistor R is equal to $20\ \text{V}$




Q.9 In the circuit shown in figure, after closing the switch S , what is the change in current flowing through the resistance A ?

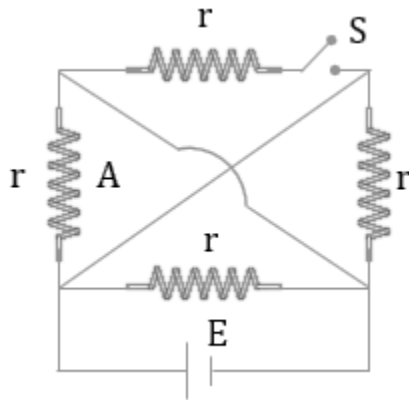- (A) No change in the value of current passing through resistance A
 (B) The current passing through resistance A decreases
 (C) The current passing through resistance A increases
 (D) Data is insufficient to say anything



Q.10 Find the current i in the circuit shown below.

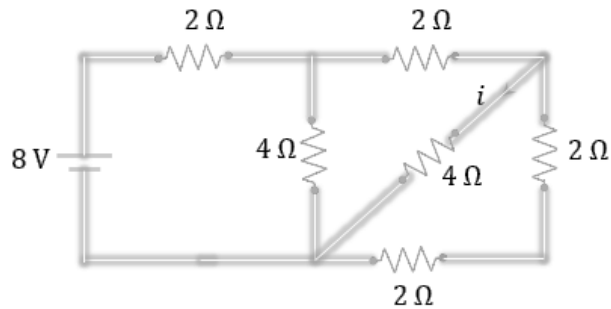- (A) 1 A (B) 3 A (C) $\frac{3}{2}$ A (D) $\frac{1}{2}$ A



WORKSHEET

Angular Velocity


Q.1 Two particles A and B are moving in opposite directions on a circle. Initially particles A and B are diagonally opposite to each other. Particle A move with angular velocity π rad/s, angular acceleration $\pi/2$ rad/s² and particle B moves with constant angular velocity 2π rad/s. Find the time after which both the particles A and B will collide.

(A) 3.2 sec

(B) 2 sec

(C) 3.6 sec

(D) 4.5 sec

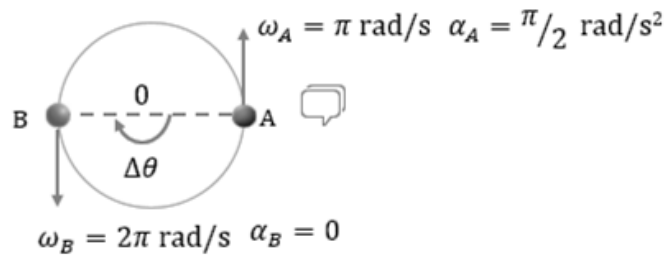

Net Contact Force


Q.2 The minimum mass of C that must be placed on A to prevent it from moving is equal to

(A) 15 kg

(B) 10 kg

(C) 5 kg

(D) 3 kg

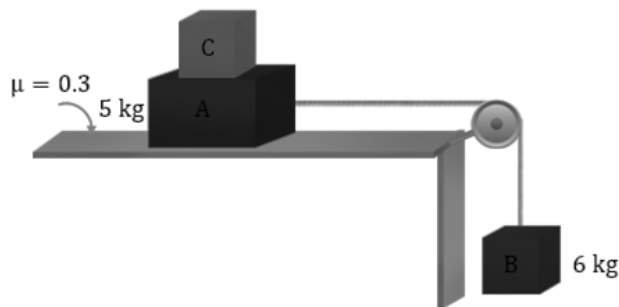

Motion under Variable Acceleration


Q.3 A particle moves in a straight line with an acceleration 'a' m/s² given as function of time, $a = (-1)/t^2$. At time $t = 1$ s the particle has a velocity of 3 m/s, then find the velocity at $t = 4$ s.

(A) 2.25 m/s

(B) 5 m/s

(C) 4.5 m/s

(D) 7 m/s

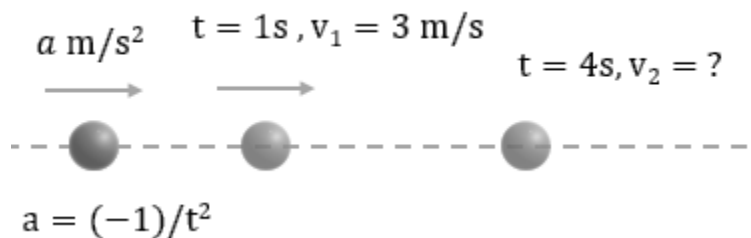

Partially Inelastic Collision

Q.4 A 1.0 kg ball drops vertically onto a floor from a height of 25 cm. It rebounds to a height of 4 cm. The coefficient of restitution for the collision is-

(A) 0.16


(B) 0.32

(C) 0.40

(D) 0.56


Thermal Stress

- Q.5** Two uniform rods AB and BC have Young's modulus $1.2 \times 10^{11} \text{ N/m}^2$ and $1.5 \times 10^{11} \text{ N/m}^2$ respectively. If coefficient of linear expansion of AB is $1.5 \times 10^{-5}/^\circ\text{C}$ and both have equal area of cross section, then coefficient of linear expansion of BC, for which there is not shift of the junction at all temperatures, is
- (A) $1.5 \times 10^{-5}/^\circ\text{C}$ (B) $1.2 \times 10^{-5}/^\circ\text{C}$ (C) $0.6 \times 10^{-5}/^\circ\text{C}$ (D) $0.75 \times 10^{-5}/^\circ\text{C}$

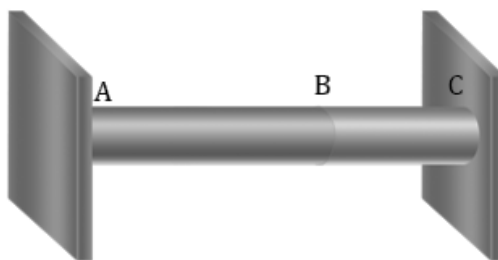
**Surface Tension**

- Q.6** Consider a U-shaped frame with a sliding wire of length ℓ and mass 'm' on its arm. It is dipped in a soap solution, taken out and placed in a vertical position such that a thin film is formed on it as shown in figure. Find maximum value of m so that wire does not descend: (Surface tension of soap solution is S)

(A) $\frac{2S\ell}{g}$ (B) $\frac{S\ell}{g}$ (C) $\frac{S\ell}{2g}$ (D) $\frac{S\ell}{4g}$

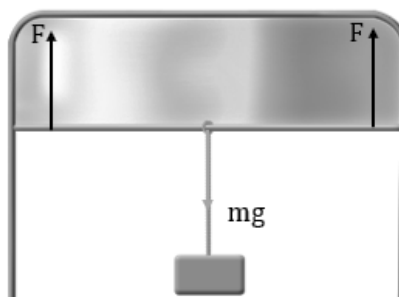**Deviation in Prism**

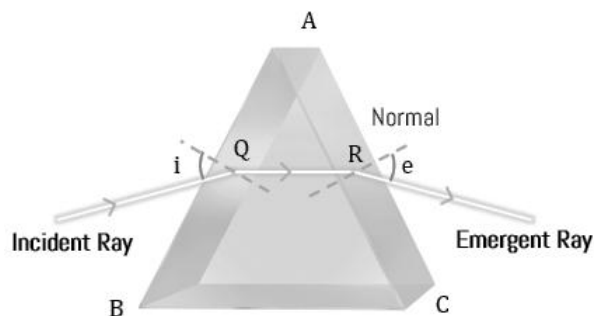- Q.7** A ray of light passes through an equilateral prism ($\mu = 1.5$) such that the angle of incidence is equal to the angle of emergence & the either is equal to $3/4$ th of the angle of prism. Calculate angle of deviation.
- (A) 30° (B) 45° (C) 20° (D) 60°



Minimum Deviation


Q.8 If a light ray is incident at $i = 90^\circ$, find the minimum value of the prism angle in degrees for which emergence is not possible.

(A) 15°

(B) 30°

(C) 45°

(D) 60°

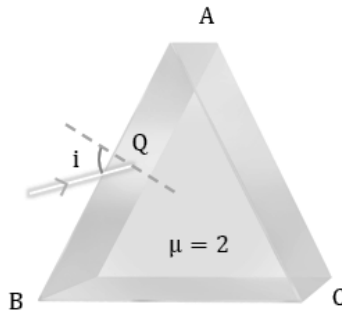


Q.9 The following diagram represents a semicircular wire of linear charge density $\lambda = \lambda_0 \sin \theta$, where λ_0 is a positive constant. The electric potential at O is (take $k = 1/(4\pi\epsilon_0)$)

(A) $k\lambda_0 \sin \theta$

(B) $\frac{k\lambda_0 \cos \theta}{2}$

(C) Zero

(D) $k\lambda_0 \cos \theta$

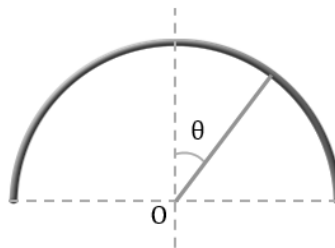**Application of Gauss's Law**


Q.10 Electric field in a certain region is acting radially outward and the variation of electric field with distance from the origin is represented below. The slope of the graph is A' . The charge contained in a sphere of radius a centre at the origin will be given by

(A) $8\pi\epsilon_0 A' a^3$

(B) $4\pi\epsilon_0 A' a^3$

(C) $4\pi\epsilon_0 A' a^2$

(D) $\pi\epsilon_0 A' a^2$

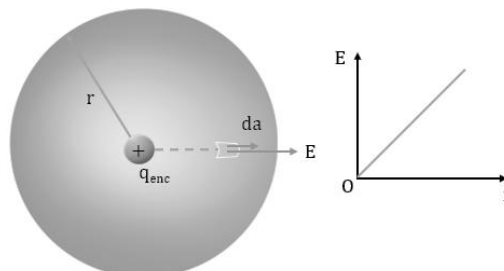**Series and Parallel Combination of Resistors**


Q.11 Equivalent resistance between the points A and B is (in Ω)

(A) $\frac{1}{5}$

(B) $\frac{5}{4}$


(C) $\frac{7}{3}$

(D) $\frac{7}{2}$

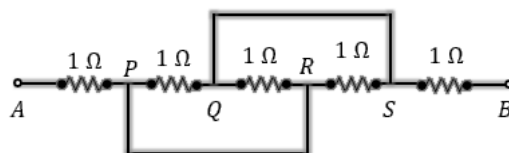


Series and Parallel Combination of Resistors

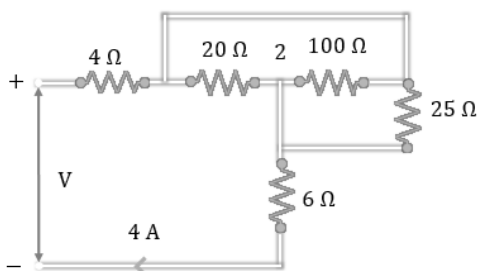- Q.12** In the circuit shown in figure, the potential difference V must be
 (A) 50 V (B) 80 V (C) 100 V (D) 1290 V




Series and Parallel Combination of Resistors

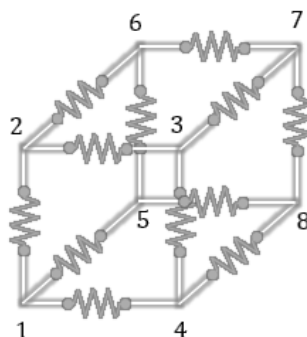- Q.13** Twelve resistors each of resistance r are connected together so that each lies along the edge of the cube as shown in the figure. The equivalent resistance between points 1 and 3 is
 (A) $\frac{1}{4}r$ (B) $\frac{1}{2}r$ (C) $\frac{3}{4}r$ (D) $\frac{5}{4}r$




Series and Parallel Combination of Resistors

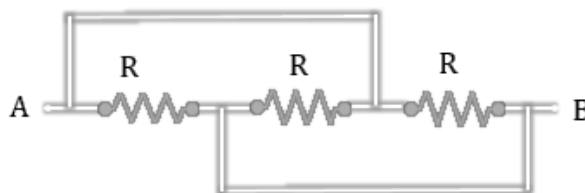- Q.14** Find the equivalent resistance between A and B.
 (A) R (B) $\frac{R}{3}$ (C) $3R$ (D) $\frac{R}{6}$




Series and Parallel Combination of Resistors

- Q.15** What is the equivalent resistance between A and B in the following circuit?
 (A) 1 Ω (B) 2 Ω (C) 3 Ω (D) 4 Ω

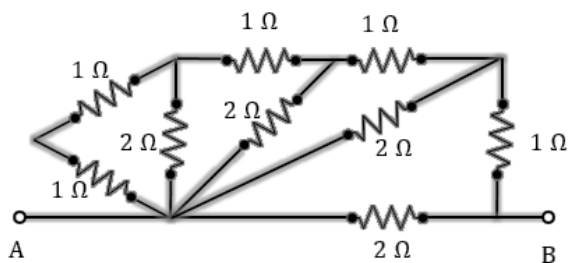**Series and Parallel Combination of Resistors**


Q.16 The equivalent resistance between A and B is :

- (A) $\frac{7}{5} \Omega$ (B) $\frac{13}{5} \Omega$ (C) $\frac{16}{5} \Omega$ (D) 2Ω

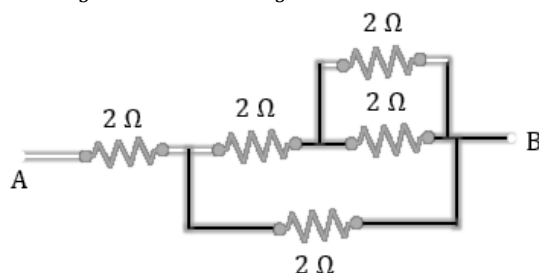**Series and Parallel Combination of Resistors**


Q.17 The equivalent resistance between A and B is :

- (A) $\frac{R}{2}$ (B) R (C) $2R$ (D) $3R$

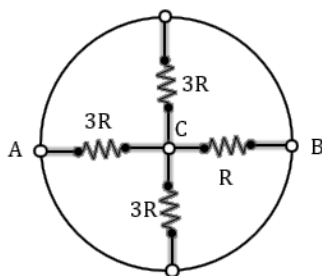**Kirchhoff's Voltage Law**

Q.18 In the circuit shown, the current in 3Ω resistance is

- (A) 1 A (B) $\frac{1}{7} \text{ A}$ (C) $\frac{5}{7} \text{ A}$ (D) $\frac{15}{7} \text{ A}$

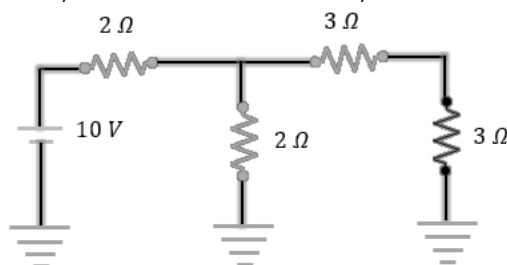
**Kirchhoff's Voltage Law**

Q.19 When 2 resistors are in parallel combination, then determine i_1 and i_2 , if the combination carries a current i ?

- (A) $i_1 = \frac{iR_2}{R_1+R_2}$ And $i_2 = \frac{iR_1}{R_1+R_2}$ (B) $i_1 = \frac{iR_2}{R_1+R_2}$ and $i_2 = \frac{iR_1}{R_1+R_2}$

(C) $i_1 = \frac{iR_2}{R_1}$ And $i_2 = \frac{iR_1}{R_2}$

(D) None

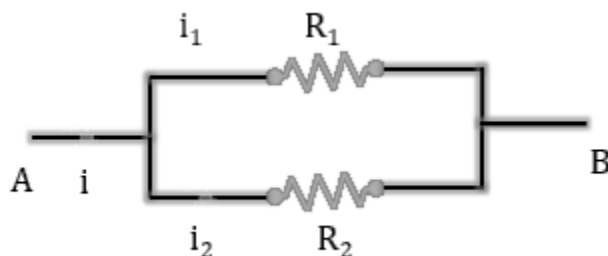

Kirchhoff's Voltage Law


Q.20 Find the current i in the circuit shown below:

(A) $\frac{3}{2}$ A

(B) $\frac{5}{2}$ A

(C) $\frac{7}{2}$ A

(D) $\frac{1}{2}$ A

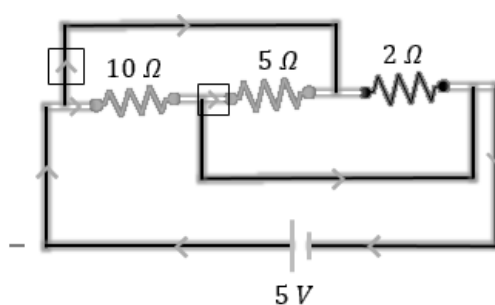

ANSWER KEY

Q.	1	2	3	4	5	6	7	8	9	10
Sol.	(A)	(C)	(B)	(B)	(C)	(A)	(B)	(C)	(A)	(D)
WORK SHEET										
Q.	1	2	3	4	5	6	7	8	9	10
Sol.	(B)	(A)	(A)	(C)	(B)	(A)	(A)	(D)	(C)	(B)
Q.	11	12	13	14	15	16	17	18	19	20
Sol.	(C)	(B)	(C)	(B)	(A)	(C)	(C)	(C)	(A)	(C)