
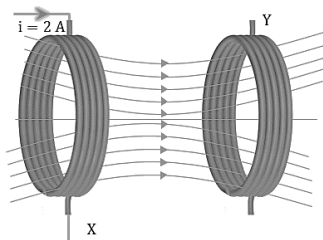


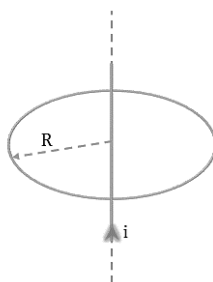- Q.1** Two coils **X** and **Y** are placed in a circuit such that when the current changes by **2 A** in coil **X** the magnetic flux changes by **0.4 Wb** in **Y**. The value of mutual inductance of the coils is-




- (A) 0.2 H (B) 5 H (C) 0.8 H (D) 4 H

- Q.2** A long straight wire carrying current **i** is placed along the axis of a circular ring of radius **R**. The mutual inductance of this system is




- (A) $\frac{\mu_0 R}{2}$ (B) $\frac{\mu_0 \pi R}{2}$ (C) $\frac{\mu_0}{2}$ (D) Zero

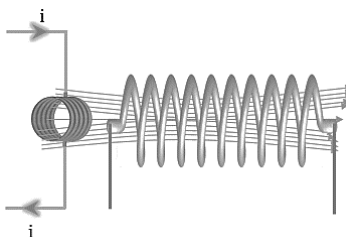- Q.3** Coil of **100** turns and having radius **1 cm** is kept co-axially within a long solenoid of **8** turns per **cm** with radius **5 cm**. Find the mutual inductance between the coil and solenoid-




- (A) 2.25×10^{-5} H (B) 4.75×10^{-5} H (C) 1.35×10^{-5} H (D) 3.15×10^{-5} H

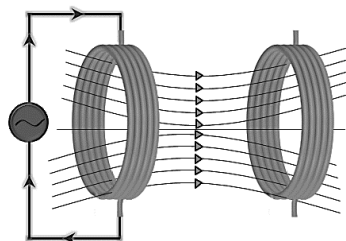- Q.4** Two coaxial coils are very close to each other and their mutual inductance is **3 H**. If a current $i_1 = 2\sin 30t$ A is passing through the first coil, then find the peak value of induced **emf** in the second coil.




- (A) 0 V (B) 90 V (C) $\frac{180}{\sqrt{2}}$ V (D) 180 V

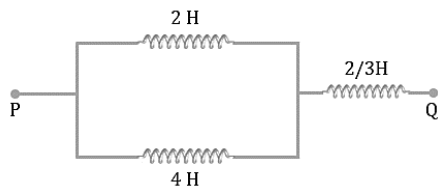- Q.5** The equivalent inductance between points **P** and **Q** is




- (A) 2 H (B) 4 H (C) 6 H (D) 8 H

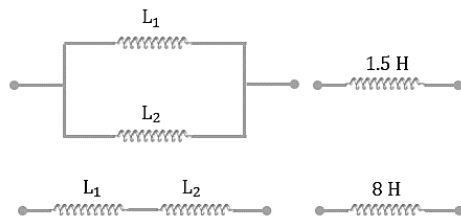Q.6 Two inductances connected in parallel are equivalent to a single inductance of **1.5 H** and when connected in series are equivalent to a single inductance of **8 H**. The difference in their inductance is-




- (A) 3 H (B) 7.5 H (C) 2 H (D) 4 H

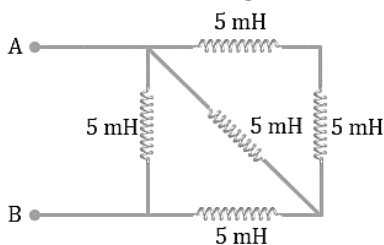Q.7 Find the equivalent inductance in the combination given below between points **A** and **B**.



- (A) 3.8 mH (B) 3.1 mH (C) 2.4 mH (D) 5.6 mH

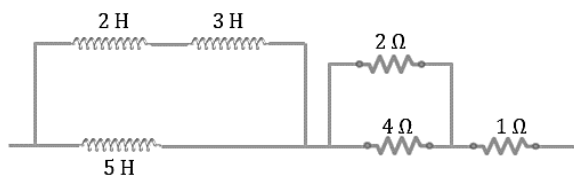Q.8 The time constant of the given circuit is-



- (A) 0.032 s (B) 0.032 s (C) 0.18 s (D) 1.07 s

Q.9 If the voltage of a source in an AC circuit is represented by the equation, $\mathcal{E} = 220\sqrt{2}\sin(314t)$. The frequency of the voltage is -

- (A) 100 Hz (B) 50 Hz (C) 200 Hz (D) 150 Hz

Q.10 If the voltage of a source in an AC circuit is represented by the equation, $\mathcal{E} = 220\sqrt{2}\sin(314t)$. Calculate the peak value of the current if the net resistance of the circuit is **220 Ω**.

- (A) 1.8 A (B) 1.6 A (C) 1.4 A (D) 1.2 A

ANSWER KEY

Q.	1	2	3	4	5	6	7	8	9	10
Sol.	(A)	(D)	(D)	(D)	(A)	(D)	(B)	(D)	(B)	(C)