
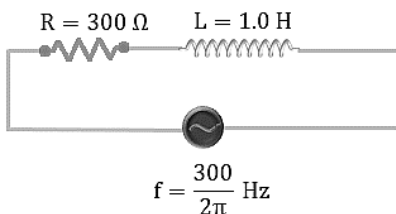


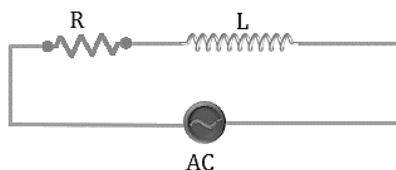- Q.1** A coil of resistance **300 Ω** and inductance **1.0 H** is connected across an alternating voltage of frequency **$\frac{300}{2\pi}$ Hz**. Calculate the phase difference between the voltage and current in the circuit.







- (A) $\frac{\pi}{3}$ (B) $\frac{\pi}{6}$ (C) $\frac{\pi}{4}$ (D) π

- Q.2** A circuit contains a resistance **R** and an inductance **L** in series. An alternating voltage **$V = V_0 \sin \omega t$** is applied across it. The currents in **R** and **L** respectively will be (**I_0** is the peak current)




- (A) $I_R = I_0 \cos \omega t, I_L = I_0 \cos \omega t$ (B) $I_R = I_0 \sin \omega t, I_L = I_0 \cos \omega t$
 (C) $I_R = I_0 \sin \omega t, I_L = -I_0 \cos \omega t$ (D) $I_R = I_L = I_0 \sin \omega t$

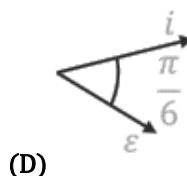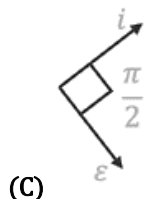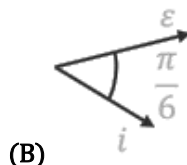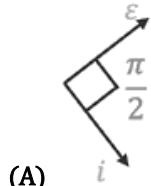- Q.3** An AC voltage **$\epsilon = 220 \sin(\omega t - \pi/6)$** is connected across a certain device. The current flowing through this device is **$i = 115 \sin(\omega t + \pi/3)$** . the correct phasor diagram, of applied voltage and current flowing in the circuit is.




- Q.4** An inductive circuit contains resistance of **12 Ω** and an inductance of **2.0 H**. If an AC voltage of **120 V** and frequency **60 Hz** is applied to this circuit, the current would be nearly
 (A) 0.8 A (B) 0.48 A (C) 0.16 A (D) 0.32 A

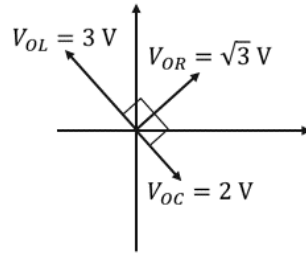- Q.5** The given figure represents the phasor diagram of a series **LCR** circuit connected to an **AC** source. At instant **t** when the source voltage is given by **$V = V_0 \cos \omega t$** , the current in the circuit in terms of peak current **I_0** will be




- (A) $I = I_0 \cos(\omega t + \frac{\pi}{6})$ (B) $I = I_0 \cos(\omega t - \frac{\pi}{6})$ (C) $I = I_0 \cos(\omega t + \frac{\pi}{3})$ (D) $I = I_0 \cos(\omega t - \frac{\pi}{3})$

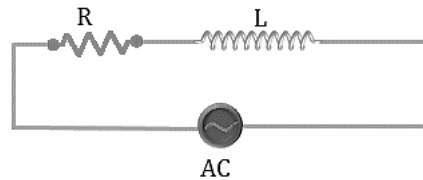
- Q.6** When **100 VDC** is applied across a solenoid, a current of **1 A** flows in it. When **100 VAC** is applied across the same coil, the current drops to **0.5 A**. If the frequency of the **AC** source is **50 Hz**, the impedance and inductance of the solenoid are



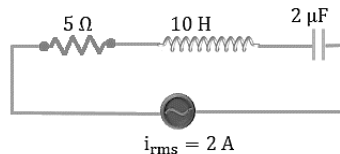- (A) 100 Ω , 0.93 H (B) 200 Ω , 1.0 H (C) 10 Ω , 0.86 H (D) 200 Ω , 0.55 H
- Q.7** A **12 Ω** resistance and an inductance of $\frac{0.05}{\pi}$ H with negligible resistance are connected in series. Across the ends of this circuit a **130 V** alternating voltage of frequency **50 Hz** is connected. Calculate the alternating current in the circuit and the potential difference across the resistance.
- (A) 10 A, 50 V (B) 10 A, 120 V (C) 5 A, 50 V (D) 10 A, 120 V
- Q.8** In an **AC** circuit, the impedance is $\sqrt{3}$ times the **R**. Then, the phase angle is
- (A) $\cos^{-1}(\frac{1}{\sqrt{2}})$ (B) $\cos^{-1}(\frac{1}{3})$ (C) $\cos^{-1}(\frac{1}{2})$ (D) $\cos^{-1}(\frac{1}{\sqrt{3}})$
- Q.9** A capacitor **C = 2 μ F** and an inductor with **L = 10 H** and coil resistance **5 Ω** are in series in a circuit. When an alternating current of **rms** value **2 A** flows in the circuit, the average power (in **W**) in the circuit is



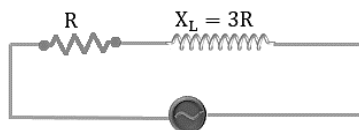- (A) 100 (B) 50 (C) 20 (D) 10
- Q.10** In series **LR** circuit, **X_L = 3R**. Now a capacitor with **X_C = R** is added in series. Ratio of new to old power factor is



- (A) 1 (B) 2 (C) $\frac{1}{\sqrt{2}}$ (D) $\sqrt{2}$

ANSWER KEY

Q.	1	2	3	4	5	6	7	8	9	10
Sol.	(C)	(D)	(C)	(C)	(B)	(D)	(D)	(D)	(C)	(D)