
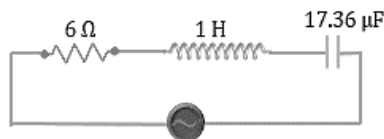


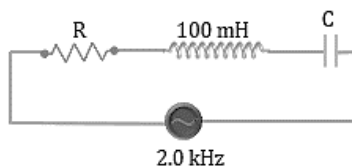- Q.1** A resistor of $R = 6\ \Omega$ an inductor of $L = 1\ \text{H}$ and a capacitor of $C = 17.36\ \mu\text{F}$ are connected in series with an AC source. Find the quality factor.




- (A) 3.72 (B) 40 (C) 2.37 (D) 80

- Q.2** An inductor of inductance $100\ \text{mH}$ is connected in series with a resistance, a variable capacitance and an AC source of frequency $2.0\ \text{kHz}$. What should be the value of the capacitance so that maximum current may be drawn into the circuit?



- (A) 10 nF (B) 28 nF (C) 47 nF (D) 63 nF

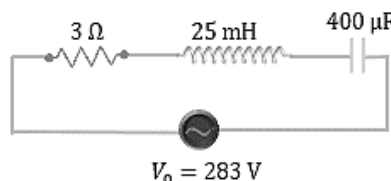- Q.3** A voltage of peak value $283\ \text{V}$ and varying frequency is applied to a series LCR combination in which $R = 3\ \Omega$, $L = 25\ \text{mH}$ and $C = 400\ \mu\text{F}$. Then, the frequency (in Hz) of the source at which maximum power is dissipated in the above circuit, is




- (A) 52.5 (B) 56.7 (C) 53.1 (D) 50.3

- Q.4** A telephone wire of length $200\ \text{km}$ has a capacitance of $0.014\ \mu\text{F per km}$. If it carries an AC of frequency $5\ \text{kHz}$, what should be the value of an inductor required to be connected in series so that the impedance of the circuit is minimum.


- (A) 0.36 mH (B) 36 mH (C) 3.6 mH (D) 0

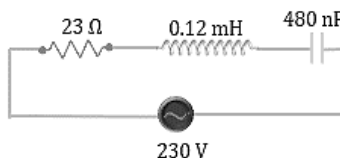- Q.5** A series RLC circuit has inductance of $0.12\ \text{H}$, capacitance of $480\ \text{nF}$ and resistance of $23\ \Omega$ is connected to a $230\ \text{V AC}$ supply whose frequency can be varied. What is the source frequency for which average power absorbed by the circuit is maximum? Also, find the value of maximum power.




- (A) 500.3 Hz, 1400 W (B) 580.2 Hz, 2000 W (C) 663.5 Hz, 2300 W (D) 753.5 Hz, 2800 W

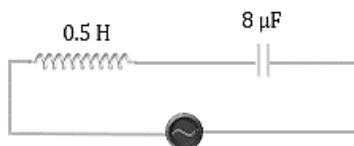- Q.6** An AC circuit consists of an inductor of inductance $0.5\ \text{H}$ and a capacitor of capacitance $8\ \mu\text{F}$ in series. The current in the circuit is maximum when the angular frequency of AC source is,




- (A) 500 Hz (B) 2×10^5 Hz (C) 4000 Hz (D) 5000 Hz

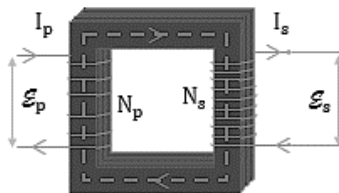- Q.7** In a step-up transformer the turns ratio is **10**. The input current of the transformer is **12.5 A** and the frequency is **50 Hz**. If the efficiency of the transformer is **80%**, then the frequency of the output current will be




- (A) 500 Hz (B) 5 Hz (C) 40 Hz (D) 50 Hz

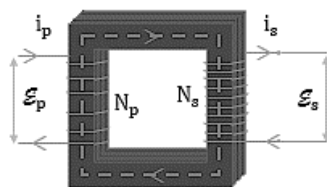- Q.8** The primary and the secondary coil of a transformer have **50** and **1500 turns**, respectively. If the magnetic flux ϕ linked with the primary coil is given by $\phi = \phi_0 + 4t$, where ϕ is in **Wb**, **t** is the time in **s** and ϕ_0 is a constant, the output voltage across the secondary coil is




- (A) 120 V (B) 220 V (C) 30 V (D) 90 V

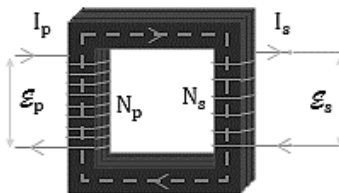- Q.9** A transformer has 200 turns in primary coil and 600 turns in secondary coil. If a 220 V DC is applied across the primary coil, what will be the voltage across the secondary coil.



- (A) 0.4 A, 100 W (B) 0.8 A, 200 W (C) 0.2 A, 50 W (D) 0.1 A, 50 W

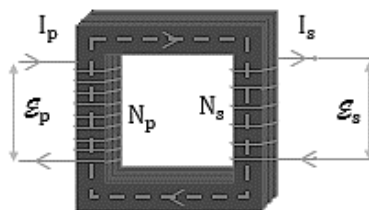- Q.10** In a step-down transformer having primary to secondary turns ratio of **20:1**, the input voltage applied is **250 V** and output current is **8 A**. Assuming **100%** efficiency, calculate current in the primary coil and the output power.



(A) 0.4 A, 100 W

(B) 0.8 A, 200 W

(C) 0.2 A, 50 W

(D) 0.1 A, 50 W

ANSWER KEY

Q.	1	2	3	4	5	6	7	8	9	10
Sol.	(B)	(D)	(D)	(A)	(C)	(A)	(D)	(A)	(C)	(A)