ELECTROSTATIC POTENTIAL AND CAPACITANCE ENERGY STORED IN A CAPACITOR

ENERGY STORED IN A CHARGED CAPACITOR:



Work has to be done in charging a conductor against the force of repulsion by the already existing charges on it. The work is stored as a potential energy in the electric field of the conductor. Suppose a conductor of capacity C is charged to a potential V0 and let q0 be the charge on the conductor at this instant. The potential of the conductor when (during charging) the charge on it was q (< q0)

$$V = \frac{q}{c}$$

Now, work done in bringing a small charge dq at this potential is,

$$dW = Vdq = \left(\frac{q}{c}\right)dq$$

 \therefore total work done in charging it from 0 to q₀ is,

$$W = \int_{0}^{q_0} dW = \int_{0}^{q_0} \frac{q}{C} dq = \frac{1}{2} \frac{q_0^2}{C}$$

This work is stored as the potential energy

$$U = \frac{1}{2} \frac{q_0^2}{C}$$

Further by using $q_0 = CV_0$ we can write this expression also

$$U = \frac{1}{2}CV_0^2 = \frac{1}{2}q_0V_0$$

In general, if a conductor of capacity C is charged to a potential V by giving it a charge q,

CLASS 12

PHYSICS

Then

$$U = \frac{1}{2}CV^2 = \frac{1}{2}\frac{q^2}{C} = \frac{1}{2}qV$$

ENERGY DENSITY OF A CHARGED CAPACITOR:

This energy is localized on the charges or the plates but is distributed in the field. Since in case of a parallel plate capacitor, the electric field is only between the plates, i.e., in a volume ($A \times d$), the energy density.

$$U_{E} = \frac{U}{volume} = \frac{\frac{1}{2}CV^{2}}{A \times d} = \frac{1}{2} \left[\frac{\varepsilon_{0}A}{d}\right] \frac{V^{2}}{Ad}$$
$$U_{E} = \frac{1}{2}\varepsilon_{0} \left(\frac{V}{d}\right) = \frac{1}{2}\varepsilon_{0}E^{2} \left[\frac{V}{d} = E\right]$$

0r

CALCULATION OF CAPACITANCE:

The method for the calculation of capacitance involves integration of the electric field between two conductors or the plates which are just equipotential surfaces to obtain the potential difference V_{ab} . Thus

$$V_{ab} = -\int_{b}^{a} \vec{E} \cdot \vec{dr}$$
$$C = \frac{q}{v_{ab}} = \frac{q}{-\int_{b}^{a} \vec{E} \cdot \vec{dr}}$$

HEAT GENERATED:

(1) Work done by battery

W = QV

 $\mathbf{Q}=\mathbf{charge}$ flow in the battery

V = EMF of battery

(2) W = +Ve (When Battery discharging) $W = \tilde{n}Ve$ (When Battery charging)

(3)
$$\Theta Q = CV (C = equivalent capacitance)$$

so $W = CV \times V = CV^2$

Now energy on the capacitor $=\frac{1}{2}CV^2$

Energy dissipated in form of heat (due to resistance)

H = Work done by battery \tilde{n} {final energy of capacitor - initial energy of capacitor}

Ex. At any time S1 switch is opened and S2 is closed then find out heat generated in Circuit.



Sol.





Charge flow through battery = $Q_f - Q_i = 2CV - CV = CV$

$$H = (CV \times 2V) - \left\{ \frac{1}{2}C(2V)^2 - \frac{1}{2}CV^2 \right\}$$
$$= 2CV^2 - \left\{ 2CV^2 - \frac{1}{2}CV^2 \right\}$$
$$H = \frac{1}{2}CV^2$$

CLASS 12

Ex. (a) Find the final charge on each capacitor if they are connected as shown in the



0c 0c

C

10µC

=10μC

+ 100µC

–100µC

Sol. Initially

Finally let q charge flows clockwise then Now applying KVL

$$\frac{+q}{C_{1}} + \frac{(10+q)}{C_{2}} - \frac{(100-q)}{C_{3}} = 0$$

$$\Rightarrow \frac{q}{2} + \frac{10+q}{2} - \frac{100-q}{5} = 0$$

$$5q + 50 + 5q - 200 + 2q = 0$$

$$12q - 150 = 0 \Rightarrow q = \frac{75}{6} \mu C$$

so final

(b) Find heat loss in the above circuit.

 $\Delta H = Energy$ [initially ñ finally] on capacitor

$$= \left[\left\{ \frac{1}{2} \times 5 \times (20)^{2} + \frac{1}{2} \times 2 \times (5)^{2} \right\} - \left\{ \frac{1}{2} \times \left(\frac{525}{6} \right)^{2} \times \frac{1}{5} + \frac{1}{2} \times \left(\frac{135}{6} \right)^{2} \times \frac{1}{2} \right\} \right] \times 10^{-6} J$$