


## CURRENT ELECTRICITY

### COMBINATION OF RESISTORS – SERIES AND PARALLEL

#### COMBINATION OF RESISTANCE:

A number of resistances can be connected in a circuit and any complicated combination can be, in general, reduced essentially to two different types, namely series and parallel combinations.

##### (a) Resistance in Series

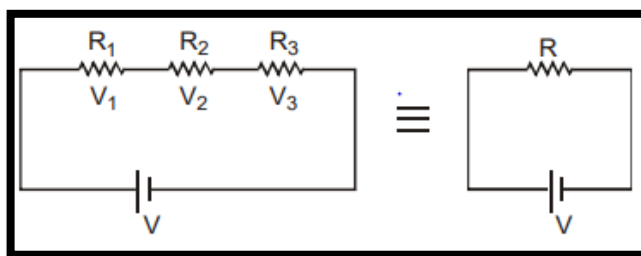

1. In this combination the resistances are joined end to end. The second end of each resistance is joined to the first end of the next resistance and so on. A cell is connected between the first end of the first resistance and the second end of the last resistance. Figure shows three resistances  $R_1$ ,  $R_2$  and  $R_3$  connected in this way.  
Let  $V_1$ ,  $V_2$  and  $V_3$  be the potential differences across these resistances.
2. In this combination the current flowing through each resistance will be the same and will be equal to the current supplied by the battery.
3. As resistances are different and the current flowing through them is the same, hence the potential differences across them will be different. The applied potential difference will be distributed among the three resistances directly in their ratio. As  $i$  is constant, hence  $V \propto R$   
i.e.,  
$$V_1 = iR_1, V_2 = iR_2, V_3 = iR_3$$

4. If the potential difference between the points A and D is V, then

$$V = V_1 + V_2 + V_3 = i (R_1 + R_2 + R_3)$$

5. If the combination of resistances between two points is replaced by a single resistance R such that there is no change in the current of the circuit in the potential difference between those two points, then the single resistance R will be equivalent to combination and

$$V = i R \text{ i.e.,}$$

$$iR = i (R_1 + R_2 + R_3) \text{ or } R = R_1 + R_2 + R_3$$

6. Thus, in series combination of resistances, important conclusion are

- (a) Equivalent Resistance > highest individual resistance
- (b) Current supplied by source = Current in each resistance


$$\frac{V}{R_1 + R_2 + R_3} = \frac{V_1}{R_1} = \frac{V_2}{R_2} = \frac{V_3}{R_3}$$

- (c) The total potential difference V between points A and B is shared among

The three resistances directly in their ratio

$$V_1 : V_2 : V_3 = R_1 : R_2 : R_3$$

### (b) Resistance in Parallel

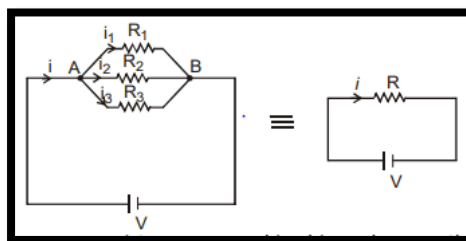

1. When two or more resistance are combined in such a way that their first ends are connected to one terminal of the battery while other ends are connected to other terminal, then they are said to be connected in parallel. Figure shows three resistances  $R_1$ ,  $R_2$  and  $R_3$  joined in parallel between two points A and B. Suppose the current flowing from the battery is  $i$ . This current gets divided into three parts at the junction A. Let the currents in three resistance  $R_1$ ,  $R_2$  and  $R_3$ , are  $i_1$ ,  $i_2$ ,  $i_3$  respectively.

2. Suppose potential difference between points A and B is V. Because each resistance is connected between same two points A and B, hence potential difference across Each resistance will be same and will be equal to applied potential difference V.

3. Since potential difference across each resistance is same, hence current approaching the junction A is divided among three resistances reciprocally in their ratio.

As V is constant, hence  $i \propto (1/R)$  i.e.,

$$i_1 = \frac{V}{R_1} \quad i_2 = \frac{V}{R_2} \quad \text{or} \quad i_3 = \frac{V}{R_3}$$

4. Because i the main current which is divided into three parts  $i_1$ ,  $i_2$  and  $i_3$  at the junction A.

Hence 
$$i = i_1 + i_2 + i_3 = V \left[ \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right]$$

If the equivalent resistance between the points A and B is R, then  $i = \frac{V}{R}$

Thus, 
$$\frac{V}{R} = V \left[ \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right] \quad \text{or} \quad \frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

5. Thus, in parallel combination of resistance important conclusion are:

(a) Equivalent resistance < lowest individual resistance

(b) Applied potential difference = Potential difference across each resistance.

or 
$$iR = i_1 R_1 = i_2 R_2 = i_3 R_3$$

(c) Current approaching the junction A = Current leaving the junction B and current is shared among the three resistances in the inverse ratio of resistances

$$i_1 : i_2 : i_3 = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$


(i) If two or more resistance are joined in parallel then  $i_1 R = i_2 R = i_3 R = \dots$  i.e.,  $iR =$  constant i.e., a low resistance joined in parallel always draws a higher current.

(ii) When two resistance  $R_1$  and  $R_2$  are joined in parallel, then

$$\frac{i_1 R_1}{i_2 R_2} = 0 \text{ or } \frac{i_1^2 R_1^2}{i_2^2 R_2^2} = 1 \text{ or } \frac{i_1^2 R_1^2}{i_2^2 R_2^2} = \frac{R_2}{R_1} \text{ or } \frac{H_1}{H_2} = \frac{R_2}{R_1}$$

i.e., heat produced will be maximum in the lowest resistance.

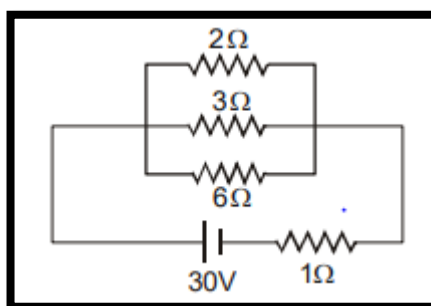**Ex.** Find current which is passing through battery




**Sol.** Here potential difference across each resistor is not 30 V  $\ominus$  battery has internal resistance here the concept of combination of resistors is useful.


$$R_{eq} = 1 + 1 = 2\Omega$$

$$i = \frac{30}{2} = 15A$$

**Ex.** Find equivalent Resistance

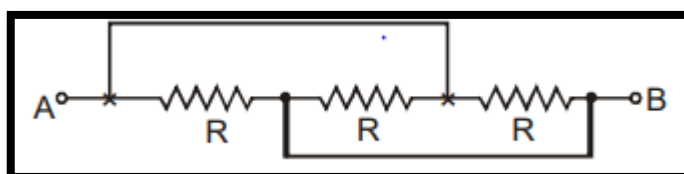


**Sol.**

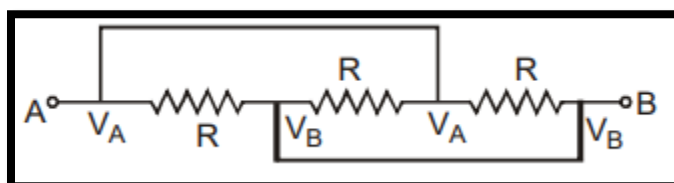


Here all the Resistance are connected between the terminals A and B. So, Modified circuit is

So  $R_{eq} = \frac{R}{3}$

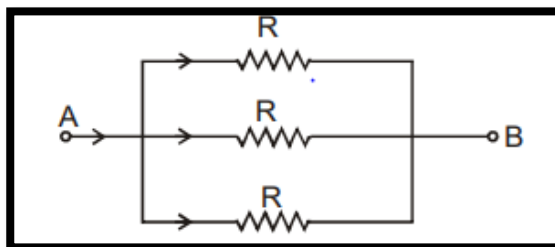


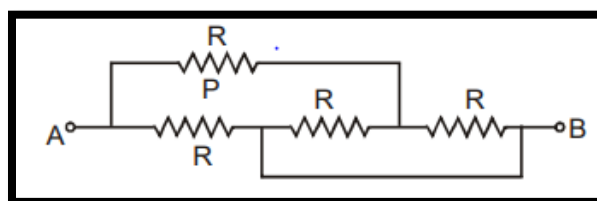**Ex.** Find the current in Resistance P if voltage supply between A and B is V volts




**Sol.**

$$R_{eq} = \frac{3R}{5}$$

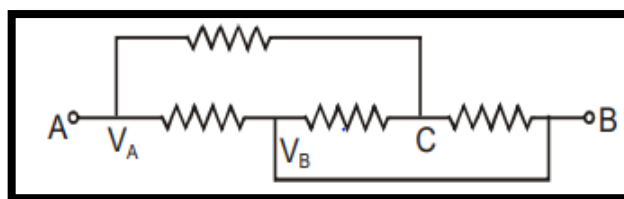

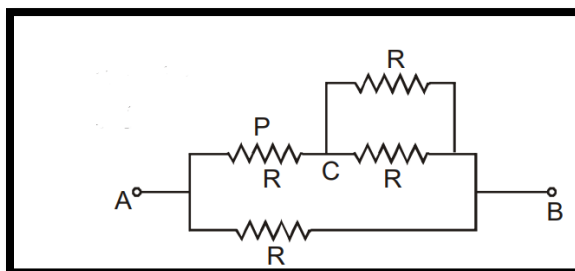
$$I = \frac{5V}{3R} \text{ Modified circuit}$$




Current in
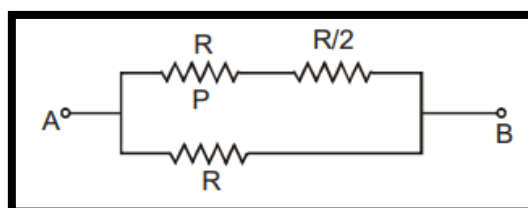
$$P = \frac{R \times \frac{5V}{3R}}{1.5R + R} = \frac{2V}{3R}$$



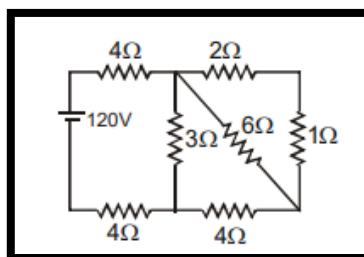Ex. Find the current in  $2\ \Omega$  resistance



Sol.  $2\ \Omega, 1\ \Omega$  in series  $= 3\ \Omega$

$$3\ \Omega, 6\ \Omega \quad \text{in parallel} = \frac{18}{9} = 2\ \Omega$$



$$2\ \Omega, 4\ \Omega \quad \text{in series} = 6\ \Omega$$

$$6\ \Omega, 3\ \Omega \quad \text{is parallel} = 2\ \Omega$$

$$R_{eq} = 4 + 4 + 2 = 10\ \Omega$$


$$i = \frac{120}{10} = 12\ A$$
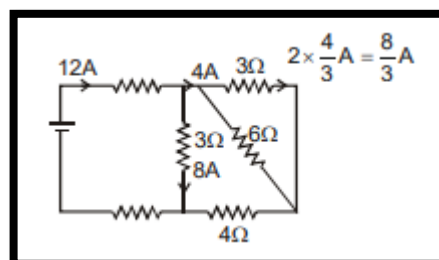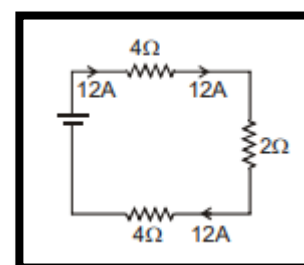
$$\text{So current in } 2\ \Omega \text{ Resistance} = \frac{8}{3}\ A$$



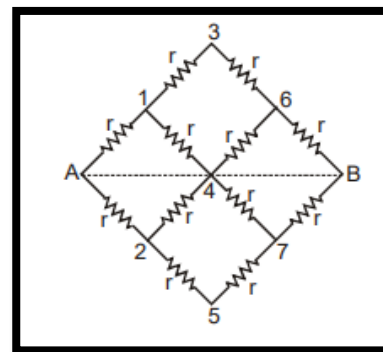
## SPECIAL PROBLEMS

We wish to determine equivalent resistance between A and B. In figure shown points (1,2) (3, 4, 5) and (6, 7) are at same potential. Equivalent circuit can be redrawn as in figure shown. The equivalent resistance of this series combination is




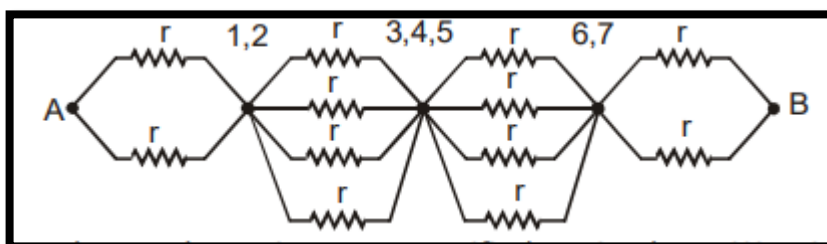
$$R_{eq} = \frac{r}{2} + \frac{r}{4} + \frac{r}{4} + \frac{r}{2} = \frac{3r}{2}$$





In the figure shown, the resistances specified are in ohms. We wish to determine the equivalent resistance between point A and D. Point B and C, E and F are the the same potential so the circuit can be redrawn as in figure shown.

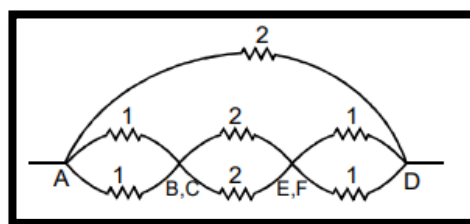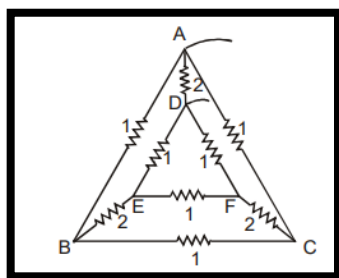Thus, the equivalent resistance is  $1 \Omega$ .



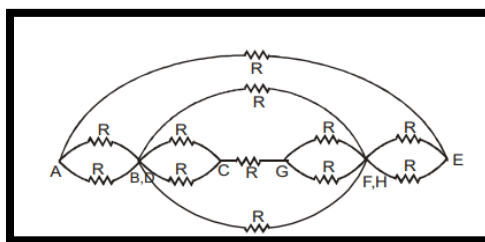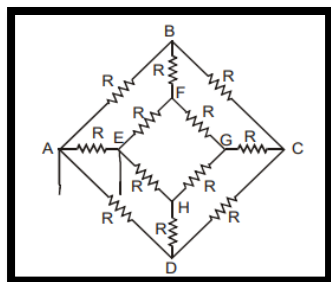In the network shown in figure shown all the resistances are equal, we wish to determine equivalent resistance between A and E. Point B and D have same potential, similarly F and H have same potential. The equivalent circuit is shown in figure shown. The equivalent resistance of network is  $7R/2$



**Ex.** In the circuit shown in figure. (a) find the current flowing through the  $100\ \Omega$  resistor connecting points U and S.

**Sol.** Figure (b) shows simplified circuit. The battery is directly attached to resistor  $90\ \Omega$  hence current in it is  $2\text{ A}$ , see figure (c), The total resistance of second branch is also  $90\ \Omega$ , hence current divides equally. Now current through  $45\ \Omega$  resistor is  $2\text{ A}$  and it is a combination of two equal  $90\ \Omega$  resistors. Once again current divides equally.  $90\ \Omega$  resistor is a series combination of  $40\ \Omega$  and  $50\ \Omega$ , hence current through them is equal, i.e.,

$1\text{ A}$ . As  $50\ \Omega$  resistor is a parallel combination of two equal  $100\ \Omega$  resistors, they must have the same current i.e.,  $0.5\text{ A}$

