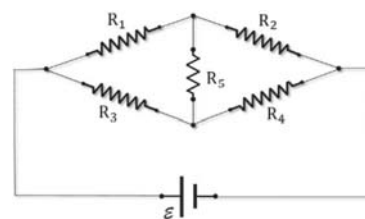


BALANCED AND UNBALANCED WHEATSTONE BRIDGE**Wheatstone Bridge**

A Wheatstone bridge connection comprises a specific arrangement of five resistors, where none of the resistors are directly in series or parallel with each other.

Typically, the majority of questions focus on balanced Wheatstone bridges.

**Balanced Wheatstone Bridge**

If there is no current through R_5 the bridge is said to be balanced.

The bridge is considered to be in a balanced state.

KVL between voltage V to x : $V - x = i_1 R_1 = i_2 R_3$... (1)

KVL between voltage x to O : $x - 0 = i_1 R_2 = i_2 R_4$... (2)

Dividing equation (1) by (2)

$$\frac{R_1}{R_2} = \frac{R_3}{R_4} \Rightarrow R_1 \times R_4 = R_3 \times R_2$$



$$\frac{R_1}{R_2} = \frac{R_3}{R_4} \text{ or } R_1 R_4 = R_3 R_2$$

If there is no current through R_5 , the bridge is balanced

As no current flows through R_5 in balanced WB, circuit can be shown as given figure

Equivalent resistance of balanced WB:
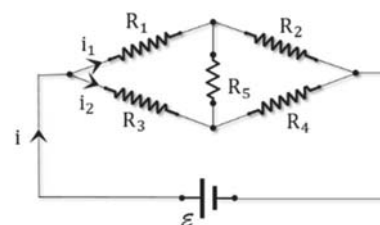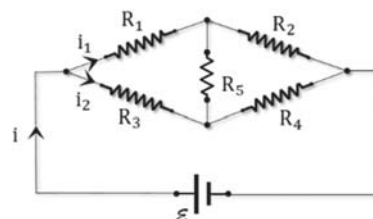
$$R_{eq} = \frac{(R_1 + R_2)(R_3 + R_4)}{R_1 + R_2 + R_3 + R_4}$$



Ex. Find the electric current through the segment BC in the circuit shown.

Sol. This is not a Wheatstone bridge. It would have been a Wheatstone bridge if battery had been connected between A and D.



This is a simple circuit with three branches in parallel connection. Equivalent circuit is shown below.

Thus, voltage at terminal B: $V_B = 10 \text{ V}$

Voltage at terminal C: $V_C = 0 \text{ V}$

Current through segment BC: $i_{BC} = \frac{10-0}{5} = 2 \text{ A}$

$$i = 2 \text{ A}$$

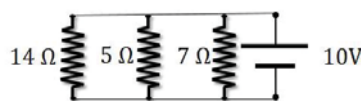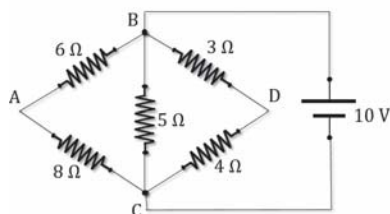

Ex. Find the equivalent resistance between the points A and D in the circuit shown.

Sol. Here $\frac{R_1}{R_2} = \frac{R_3}{R_4}$


Thus, this is a balanced Wheatstone bridge.

Equivalent resistance of balanced WB

$$R_{eq} = \frac{(R_1 + R_2)(R_3 + R_4)}{R_1 + R_2 + R_3 + R_4}$$


$$= \frac{(4+2) \times (6+3)}{4+2+6+3} = \frac{6 \times 9}{15} = \frac{18}{5} \Omega$$

$$R_{eq} = \frac{18}{5} \Omega$$

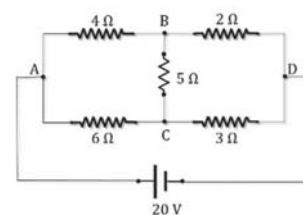

Ex. Find equivalent resistance between the points A and D in the circuit shown.

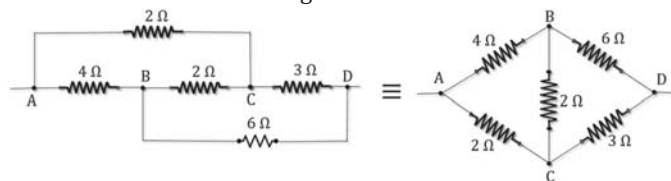- Sol.** This is a different representation of Wheatstone bridge. It can be reframed to usual form as shown in figure $\frac{R_1}{R_2} = \frac{R_3}{R_4}$
- Thus, this is a balanced Wheatstone bridge.



Equivalent resistance of balanced WB:

$$R_{eq} = \frac{(R_1 + R_2)(R_3 + R_4)}{R_1 + R_2 + R_3 + R_4}$$

$$R_{eq} = \frac{(4+6) \times (2+3)}{4+6+2+3}$$


$$= \frac{10 \times 5}{15}$$

$$= \frac{10}{3} \Omega$$

$$R_{eq} = \frac{10}{3} \Omega$$

- Ex.** Find equivalent resistance between the points A and D in the circuit shown.

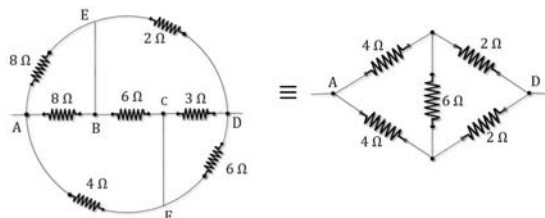Sol. Rearrange the given circuit as follows



Here,

$$\frac{R_1}{R_2} = \frac{R_3}{R_4}$$

Thus, this is a balanced Wheatstone bridge.

Equivalent resistance of balanced WB:

$$R_{eq} = \frac{(R_1 + R_2)(R_3 + R_4)}{R_1 + R_2 + R_3 + R_4}$$

$$= \frac{(4+2) \times (2+4)}{4+2+2+4}$$


$$= \frac{6 \times 6}{12} = 3 \Omega$$

$$R_{eq} = 3 \Omega$$

- Ex.** Find equivalent resistance between the points A and B in the circuit shown.

Sol. Rearrange the given circuit as follows:

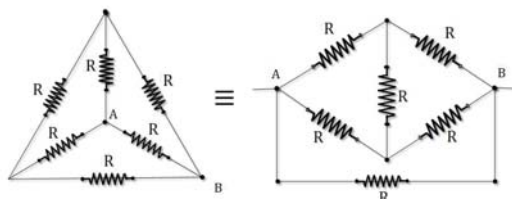Thus, circuit between point A and B is a Wheatstone bridge and one more resistance is connected parallel to it.



Equivalent resistance of balanced WB:

$$R_{AB} = \frac{(R_1 + R_2)(R_3 + R_4)}{R_1 + R_2 + R_3 + R_4}$$

$$= \frac{(R+R) \times (R+R)}{R+R+R+R} = R$$

Equivalent resistance of the circuit:

$$R_{eq} = \frac{R \times R}{R + R} = \frac{R}{2}$$

$$R_{eq} = \frac{R}{2}$$


Ex. Find current through $5\ \Omega$ resistance after interchanging position of $5\ \Omega$ resistance with the battery in the balanced Wheatstone bridge shown.

Sol. After interchanging the position of $5\ \Omega$ resistance, circuit becomes as shown in the figure. The resultant circuit is also a balanced Wheatstone bridge.

Here

$$\frac{R_1}{R_2} = \frac{R_3}{R_4}$$

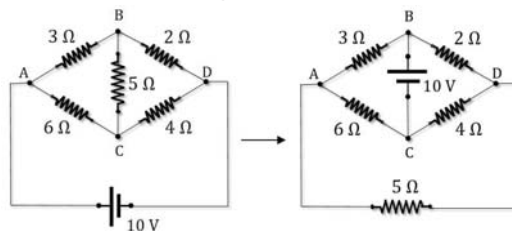Thus, this is a balanced Wheatstone bridge.



We know that the current through central resistance for balanced Wheatstone bridge is zero.

$$i = 0$$

Unbalanced Wheatstone Bridge

V – i method to determine the equivalent resistance of a circuit

Let's consider the potential at point B to be x and at point C to be y .

Current through branch BD: $i_1 = \frac{x}{2}$

Current through branch CD: $i_2 = \frac{y}{2}$

Applying KCL at point B,

$$\frac{x-V}{2} + \frac{x-y}{2} + \frac{x-0}{2} = 0$$

$$3x - V = y$$

... (1)


Applying KCL at point C,

$$\frac{y-v}{1} + \frac{y-x}{2} + \frac{y-0}{2} = 0$$

$$2y - 2v + y - x + y = 0$$

$$4y - x = 2v$$

... (2)

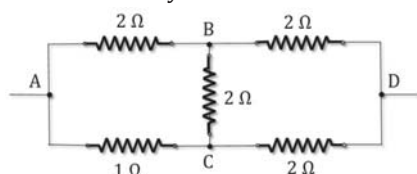

Putting value of y from equation (1) in equation (2),

$$4(3x - v) - x = 2v$$

$$12x - 4v - x = 2v$$

$$11x = 6v$$

$$x = \frac{6v}{11}$$

Putting value of x in equation (1),

$$\frac{18v}{11} - v = y$$

$$\frac{7v}{11} = y$$

Equivalent resistance of the circuit,

$$R_{eq} = \frac{V}{i} = \frac{V}{i_1 + i_2} = \frac{V}{\frac{x}{2} + y}$$

$$= \frac{2v}{x+y} = \frac{2v}{\frac{6v}{11} + \frac{7v}{11}} = \frac{22\Omega}{13}$$

$$R_{eq} = \frac{22}{13}\Omega$$

Ex. Find the equivalent resistance between A and B for the given circuit diagram.


Sol. Assume the potential at point B and C be x and y respectively

Current through branch BD: $i_1 = \frac{x}{1}$

Current through branch CD: $i_2 = \frac{y}{2}$

Applying KCL at point B,
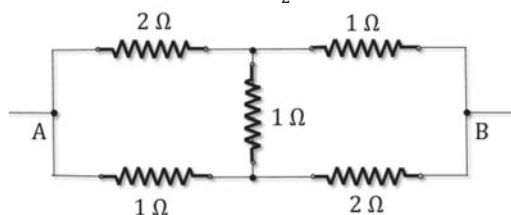
$$\begin{aligned}\frac{x-v}{2} + \frac{x-y}{1} + \frac{x-0}{1} &= 0 \\ x - v + 2x - 2y + 2x &= 0 \\ 5x - v &= 2y \\ y &= \frac{5x-v}{2}\end{aligned}\quad \dots (1)$$



Applying KCL at point C,

$$\begin{aligned}\frac{y-v}{1} + \frac{y-x}{1} + \frac{y-0}{2} &= 0 \\ 2y - 2v + 2y - 2x + y &= 0 \\ 5y - 2x &= 2v\end{aligned}\quad \dots (2)$$

Solving equation (1) and (2),

$$\begin{aligned}y &= \frac{5(\frac{5x-v}{2}) - v}{2} \\ &= \frac{8v}{14} = \frac{4v}{7}\end{aligned}$$

Putting value of y in equation (2),

$$\begin{aligned}5\left(\frac{5x-v}{2}\right) - 2x &= 2v \\ 5(5x - v) - 4x &= 4v \\ 25x - 5v - 4x &= 4v \\ 21x &= 9v \\ x &= \frac{9v}{21} = \frac{3v}{7}\end{aligned}$$

Equivalent resistance of the circuit,

$$\begin{aligned}R_{eq} &= \frac{v}{i_1 + i_2} = \frac{v}{x + yi_2} \\ &= \frac{v}{\frac{3v}{7} + \frac{2v}{7}} = \frac{7}{5} \Omega \\ R_{eq} &= \frac{7}{5} \Omega\end{aligned}$$